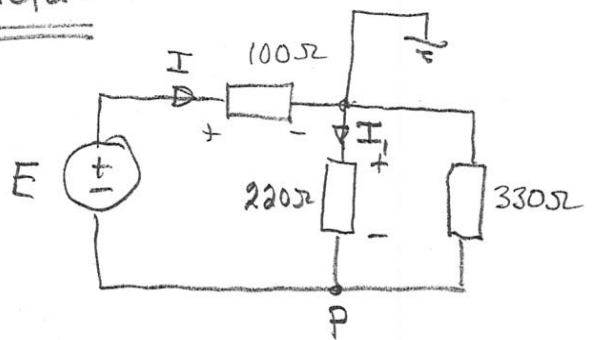


Lösningar Elektriska kretsar dec 2010

1a) $V_P = 0 - 220\Omega \cdot I_1 = \underline{\underline{-13,2V}}$

1b) $E = 100\Omega \cdot I + 220\Omega \cdot I_1$
$$I_1 = \frac{\frac{1}{220\Omega}}{\frac{1}{220\Omega} + \frac{1}{330\Omega}} \cdot I$$



$I_1 = 60\text{mA} \Rightarrow I = 100\text{mA} \Rightarrow$

$E = 100\Omega \cdot 100\text{mA} + 220\Omega \cdot 60\text{mA} = \underline{\underline{23,2V}}$

2a) $\cdot U_{CE} = E - R_C I_C = 5V - 1,8k\Omega \cdot I_C$

$\cdot I_C = h_{FE} \cdot I_B ; I_B = \frac{U - 0,7V}{R_b} = \frac{1,5V - 0,7V}{47k} = 17,02\mu A$

$\Rightarrow I_C = 120 \cdot 17,02\mu A = 2,04\text{mA} \Rightarrow$

$U_{CE} = 5V - 1,8k\Omega \cdot 2,04\text{mA} = \underline{\underline{1,32V}}$

2b) Räkna på $h_{FE} = h_{FE \text{ min}} = 50$!

$\cdot R_b = \frac{U - U_{BE}}{I_b} = \frac{4,5V - 0,7V}{I_B} = \frac{3,8V}{I_B}$

$\cdot I_B = \frac{I_C}{h_{FE}} = \frac{I_C}{50} ; I_C = \frac{E - U_{CE}}{R_C} = \frac{5V - 0,1V}{1,8k\Omega} = 2,72\text{mA}$

$\Rightarrow I_B = \frac{2,72\text{mA}}{50} = 54,4\mu A \Rightarrow$

$R_b = \frac{3,8V}{54,4\mu A} = \underline{\underline{69,8k\Omega}}$

Transistorerna böttnar säkert för $R_b < 69,8k\Omega$


③ Inverterande förstärkarkoppling!

⇒

$$\frac{U_2}{U_1} = - \frac{91 \text{ k}\Omega}{12 \text{ k}\Omega} = -7,583$$

$$\Rightarrow U_1 = \frac{U_2}{-7,583} = \frac{-10,5 \text{ V}}{-7,583} = \underline{\underline{1,385 \text{ V}}}$$
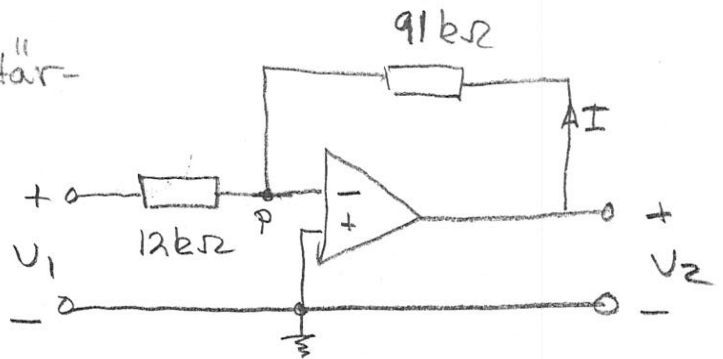
$$U_p = 0 \Rightarrow I = \frac{U_2}{91 \text{ k}\Omega} = \frac{10,5 \text{ V}}{91 \text{ k}\Omega} = \underline{\underline{115,4 \mu\text{A}}}$$




④ Komplekt: $u(t) \leftrightarrow U = 10 e^{j(3000t - 20^\circ)}$

$$i(t) \leftrightarrow I = |I| e^{j(3000t + \beta)}$$

$$R = 330 \Omega \leftrightarrow 330, C = 820 \text{ nF} \leftrightarrow \frac{1}{j\omega C} = -j406,5$$

Beräkningsschema

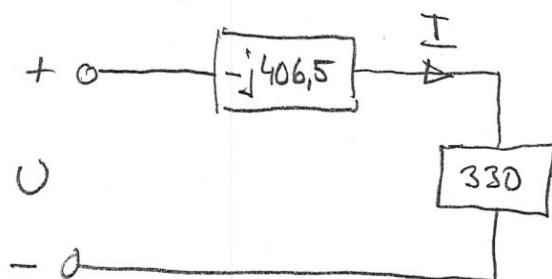

$$I = \frac{U}{Z_{\text{tot}}}$$

$$Z_{\text{tot}} = 330 - j406,5 =$$

$$= 523,6 \cdot e^{-j50,9^\circ} \Rightarrow$$

$$I = \frac{10 e^{j(3000t - 20^\circ)}}{523,6 e^{-j50,9^\circ}} = 19,1 e^{j(3000t + 30,9^\circ)} \Rightarrow$$

$$|I| = 19,1 \text{ mA} \quad \beta = 30,9^\circ \Rightarrow$$

$$\underline{\underline{i(t) = 19,1 \sin(3000t + 30,9^\circ) \text{ mA}}}$$

5a. $E = 2,5V \Rightarrow$ höger diod spärrar. Leder vänstra dioden? Tag bort den och beräkna spänningen över $12k\Omega$:aren.

$$U_{12} = \frac{12k\Omega}{12k\Omega + 2,7k\Omega} \cdot 2,5V = 2,04V > 0,7V \Rightarrow$$

dioden leder $\Rightarrow I = \frac{2,5V - 0,7V}{2,7k\Omega} = \underline{\underline{0,667mA}}$

5b. $E = -2,5V$. Vänster diod spärrar. Leder den högra? Tag bort den och beräkna spänningen över $2,7k\Omega$:aren.

$$U_{2,7} = \frac{2,7k\Omega}{2,7k\Omega + 12k\Omega} \cdot 2,5V = 0,46V < 0,7V \Rightarrow$$

ingen diod leder $\Rightarrow I = - \frac{2,5V}{2,7k\Omega + 12k\Omega} = \underline{\underline{-0,17mA}}$

$$(6a) \quad P = U_e \cdot I_e \cdot \cos \phi$$

$$U_e = \frac{|U|}{\sqrt{2}} = \frac{0,8V}{\sqrt{2}} ; \quad I_e = \frac{|I|}{\sqrt{2}} = \frac{1,2mA}{\sqrt{2}}$$

$$\phi = \frac{1}{3} \cdot 180^\circ = 60^\circ \Rightarrow P = \frac{0,8V}{\sqrt{2}} \cdot \frac{1,2mA}{\sqrt{2}} \cdot \cos 60^\circ = \underline{\underline{0,24mW}}$$

$$(6b) \quad T = 0,6ms \Rightarrow f = \frac{1}{0,6ms} = \underline{\underline{1,67kHz}} \Rightarrow$$

$$\omega = 2\pi f = \underline{\underline{10,47krad/s}}$$

(6c) Strömmen ligger före spänningen.

(6d) Kapacitiv seriekrets $\Rightarrow$

$$Z = R + \frac{1}{j\omega C} = R - j \frac{1}{\omega C} =$$

$$= |Z| \cos \phi - j |Z| \sin \phi$$

$$|Z| = \frac{|U|}{|I|} = \frac{0,8V}{1,2mA} = 666,7\Omega ; \quad \phi = \frac{1}{3} \cdot 180^\circ = 60^\circ \Rightarrow$$

$$R = |Z| \cdot \cos \phi = 666,7\Omega \cdot \cos 60^\circ \approx \underline{\underline{333\Omega}}$$


$$\frac{1}{\omega C} = |Z| \cdot \sin \phi \Rightarrow C = \frac{1}{\omega \cdot |Z| \cdot \sin \phi} =$$

$$= \frac{1}{10,47 \cdot 10^3 \cdot 666,7 \cdot \sin 60^\circ} F = \underline{\underline{165,4nF}}$$

$$\textcircled{7} \quad F(\omega) = 10^4 \cdot \frac{j\omega \cdot (1 + j \frac{\omega}{10^5})}{(1 + j \frac{\omega}{10}) \cdot 1000 \cdot (1 + j \frac{\omega}{1000})} =$$

$$= 10 \cdot \frac{j\omega \cdot (1 + j \frac{\omega}{10^5})}{(1 + j \frac{\omega}{10}) \cdot (1 + j \frac{\omega}{1000})}$$

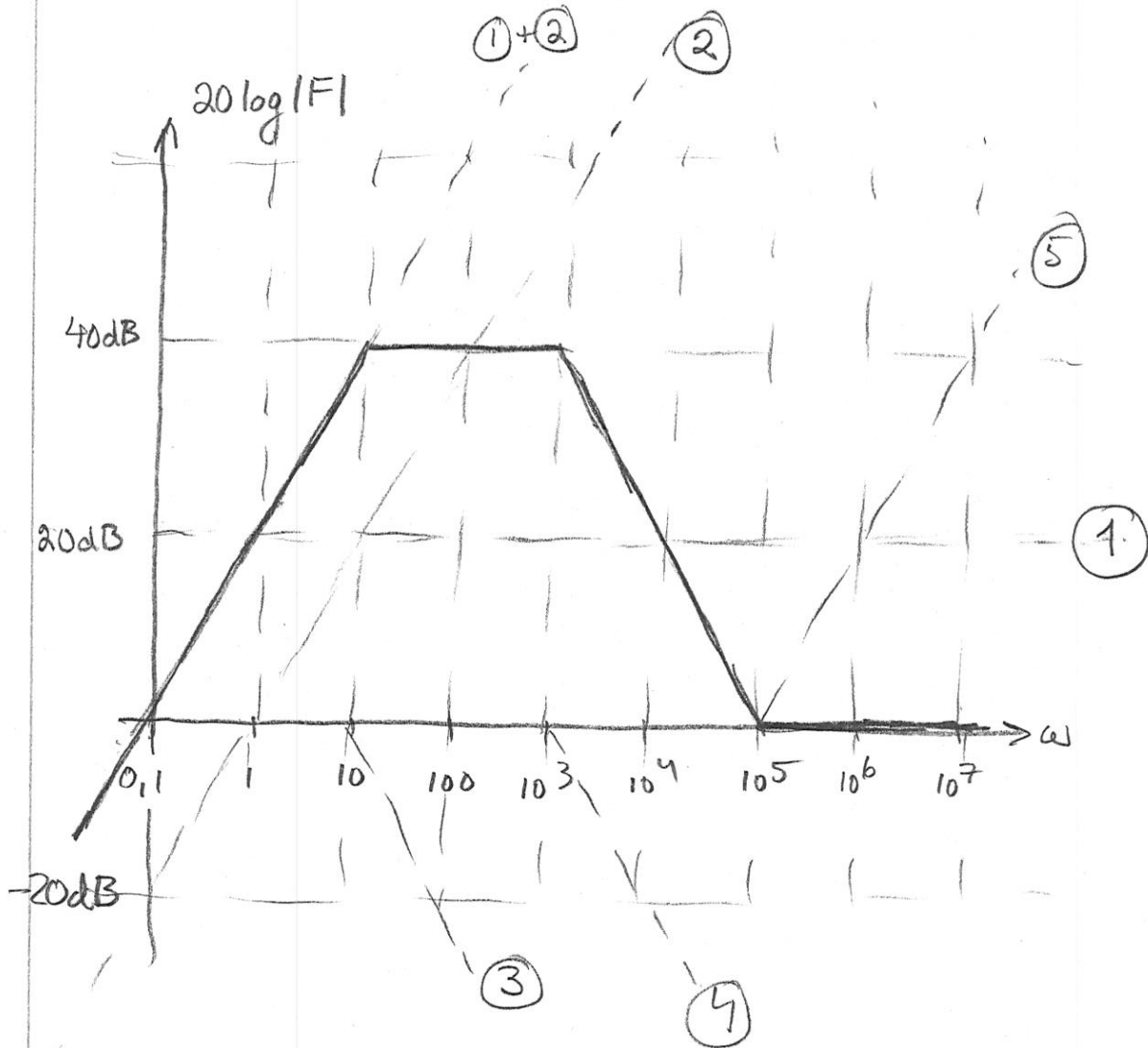$\textcircled{1}$ $\textcircled{2}$ $\textcircled{3}$ $\textcircled{4}$ $\textcircled{5}$



8. Inverterande förstärkarkoppling.

Låga frekvenser: $C = \text{öppn} \Rightarrow$

$$A_M = - \frac{82k + 330k}{2,2k} = \underline{\underline{-187,3}}$$

Höga frekvenser: $C = \text{kortslutning} \Rightarrow$

$$A_M = - \frac{82k}{2,2k} = \underline{\underline{-37,3}}$$

$$F(\omega) = - \frac{Z_2}{R_1} \quad (1)$$


$$Z_2 = R_2 + R_3 \parallel \frac{1}{j\omega C}$$

$$R_3 \parallel \frac{1}{j\omega C} = \frac{R_3 \cdot \frac{1}{j\omega C}}{R_3 + \frac{1}{j\omega C}} =$$

$$= \frac{R_3}{1 + j\omega R_3 C} \Rightarrow Z_2 = R_2 + \frac{R_3}{1 + j\omega R_3 C} = \frac{R_2 + R_3 + j\omega R_2 R_3 C}{1 + j\omega R_3 C} =$$

$$= (R_2 + R_3) \cdot \frac{1 + j\omega \frac{R_2 R_3}{R_2 + R_3} C}{1 + j\omega R_3 C} \quad \text{Sätt in i (1):}$$
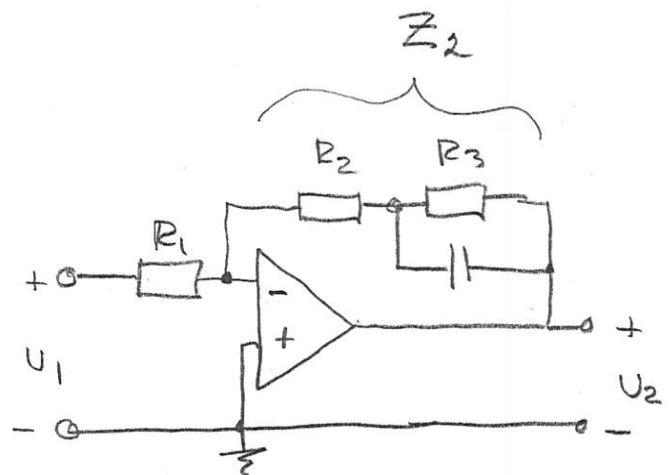
$$F(\omega) = - \frac{R_2 + R_3}{R_1} \cdot \frac{1 + j\omega \frac{R_2 R_3}{R_2 + R_3} C}{1 + j\omega R_3 C} = \underline{\underline{-187 \cdot \frac{1 + j \frac{\omega}{324}}{1 + j \frac{\omega}{64,5}}}}$$



$$R_1 = 2,2k\Omega \quad R_2 = 82k\Omega \quad R_3 = 330k\Omega \quad C = 47nF$$


9. Summerkoppling $\Rightarrow$

$$u_2 = -\frac{68k\Omega}{10k\Omega} \cdot 0,6V - \frac{68k\Omega}{4,7k\Omega} \cdot u_1 =$$

$$= -4,08V - \overbrace{14,47 \cdot u_1}^{u_1(t)} = -4,08V - u_1$$

Vi beräknar först $\hat{u}_{\max}$.

Figur.

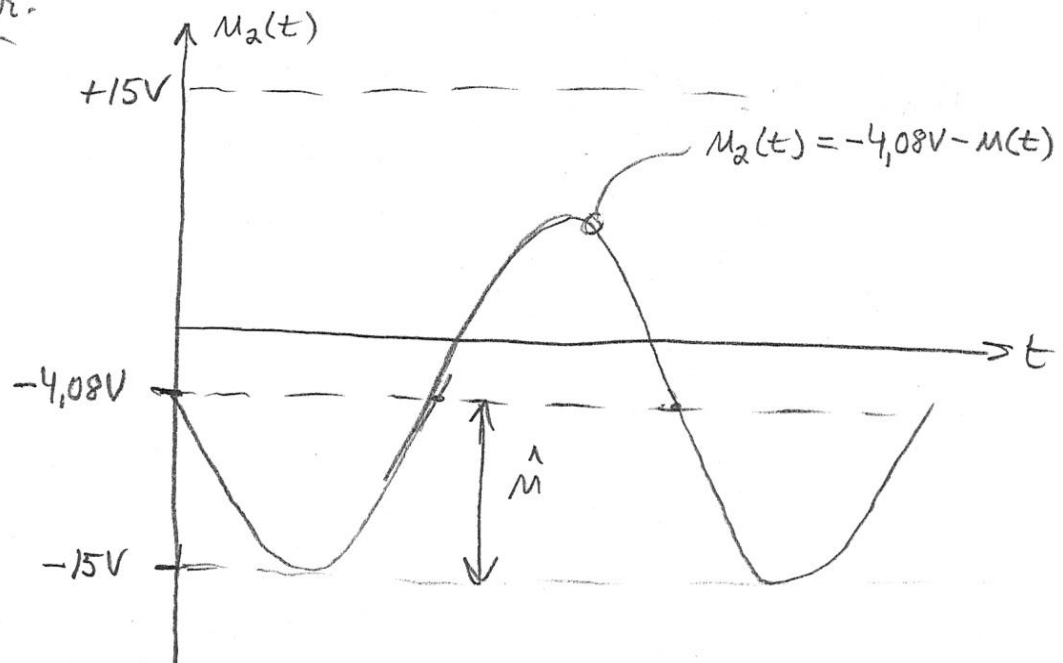

$$\Rightarrow \hat{M} = -4,08V - (-15V) = 10,92V \Rightarrow$$

$$\hat{M}_{\max} = \frac{10,92V}{14,47} = \underline{\underline{0,7547V}}$$