

Kortfattade lösningar Elektriska kretsar dec 2012

$$\underline{1.} \quad I = \frac{15V - 9V}{200\Omega + 200\Omega + 100\Omega} = \underline{12mA}$$

$$\cdot U = 200\Omega \cdot 12mA = \underline{2,4V}$$

$$\cdot V_A = 0 + 100\Omega \cdot 12mA + 9V = \underline{10,2V}$$

2a. Läge 2. Då blir $U_{BE} = 0$. Transistorn strypt!

$$\underline{2b.} \quad R_B = \frac{16V - 0,7V}{I_B} - 560\Omega, \quad I_B = \frac{I_C}{45}$$

$$I_C = \frac{9W}{16V} = 562,5mA \Rightarrow I_B = 12,5mA \Rightarrow$$

$$R_B \leq \frac{15,3V}{12,5mA} - 560\Omega = \underline{664\Omega}$$

3. Summerkoppling $\Rightarrow U$

$$U_2 = - \frac{100k\Omega}{5k\Omega} \cdot (-0,175V) - \frac{100k\Omega}{20k\Omega} \cdot E = \underline{3,5V - 5 \cdot E}$$

$$\underline{a.} \quad E = 1,5V \Rightarrow U_2 = 3,5V - 5 \cdot 1,5V = \underline{-4V}$$

$$\underline{b.} \quad -15V \leq U_2 \leq 15V \Rightarrow$$

$$-15V \leq 3,5V - 5 \cdot E \leq 15V \Leftrightarrow$$

$$-11,5V \leq 5E \leq 18,5V$$

$$\underline{-2,3V \leq E \leq 3,7V}$$

4a. Komplex:

$$u(t) = 10 \sin(\omega t + 23^\circ) \text{ V} \leftrightarrow U = 10 e^{j(\omega t + 23^\circ)} \text{ V}$$

$$i(t) = |I| \sin(\omega t + \beta) \leftrightarrow I = |I| e^{j(\omega t + 23^\circ)}$$

$$R = 820 \Omega \leftrightarrow 820$$

$$C = 680 \text{ nF} \leftrightarrow \frac{1}{j\omega C} = -j \frac{1}{600 \cdot 680 \cdot 10^{-9}} = -j2451$$

$$I = \frac{U}{Z}; \quad Z = 820 - j2451 \Omega = 2585 \cdot e^{-j71,5^\circ} \Omega \Rightarrow$$

$$I = \frac{10 e^{j(\omega t + 23^\circ)} \text{ V}}{2585 e^{-j71,5^\circ} \Omega} = 3,87 e^{j(\omega t + 94,5^\circ)} \text{ mA} \Rightarrow$$

$$\underline{i(t) = 3,87 \cdot \sin(600t + 94,5^\circ) \text{ mA}}$$

4b. $Z = R + \frac{1}{j\omega C} = R - j \frac{1}{\omega C}$

$$i(t) \text{ } 30^\circ \text{ före } u(t) \Rightarrow \arg Z = -30^\circ \Rightarrow$$

$$\frac{\frac{1}{\omega C}}{R} = \tan 30^\circ \Rightarrow \underline{\underline{\omega = \frac{1}{R \cdot \tan 30^\circ} =}}$$

$$= \frac{1}{820 \cdot 680 \cdot 10^{-9} \cdot \tan 30^\circ} \text{ rad/s} = \underline{\underline{3106 \text{ rad/s}}}$$

5. Max-effekt om $R = 20\Omega$. Då blir strömmen genom R $1A \Rightarrow$

$$P_{\max} = 20\Omega \cdot (1A)^2 = \underline{\underline{20W}}$$

6a $P = U_e \cdot I_e \cdot \cos \phi$

$$U_e = \frac{100V}{\sqrt{2}} ; I_e = \frac{15A}{\sqrt{2}} ; \phi = \frac{1}{3} \cdot 180^\circ = 60^\circ \Rightarrow$$

$$P = \frac{100V}{\sqrt{2}} \cdot \frac{15A}{\sqrt{2}} \cdot \cos 60^\circ = \underline{\underline{375W}}$$

6b. $T = 20ms \Rightarrow f = \frac{1}{T} = \underline{\underline{50Hz}} \Rightarrow \omega = 2\pi f = \underline{\underline{314rad/s}}$

6c. Strömmen ligger efter spänningen.

6d. $|Z| = \frac{|U|}{|I|} = \frac{100V}{15A} = 6,67\Omega ; \phi = 60^\circ \Rightarrow$

$$Z = 6,67 \cdot e^{j60^\circ} \Omega = 3,33\Omega + j5,77\Omega = R + j\omega L \Rightarrow$$

$$\underline{\underline{R = 3,33\Omega}} \quad \omega L = 5,77\Omega \Rightarrow$$



$$L = \frac{5,77\Omega}{314rad/s} = \underline{\underline{18,4mH}}$$

7.

$$F(\omega) = 10 \cdot \frac{j\omega \cdot (1 + j \frac{\omega}{10^6})}{10(1 + j \frac{\omega}{100}) \cdot 10(1 + j \frac{\omega}{10^4})} =$$

$$= \frac{100}{10} \cdot \frac{j \frac{\omega}{100} (1 + j \frac{\omega}{10^6})}{(1 + j \frac{\omega}{100})(1 + j \frac{\omega}{10^4})} = 10 \cdot \frac{j \frac{\omega}{100} (1 + j \frac{\omega}{10^6})}{(1 + j \frac{\omega}{100})(1 + j \frac{\omega}{10^4})}$$

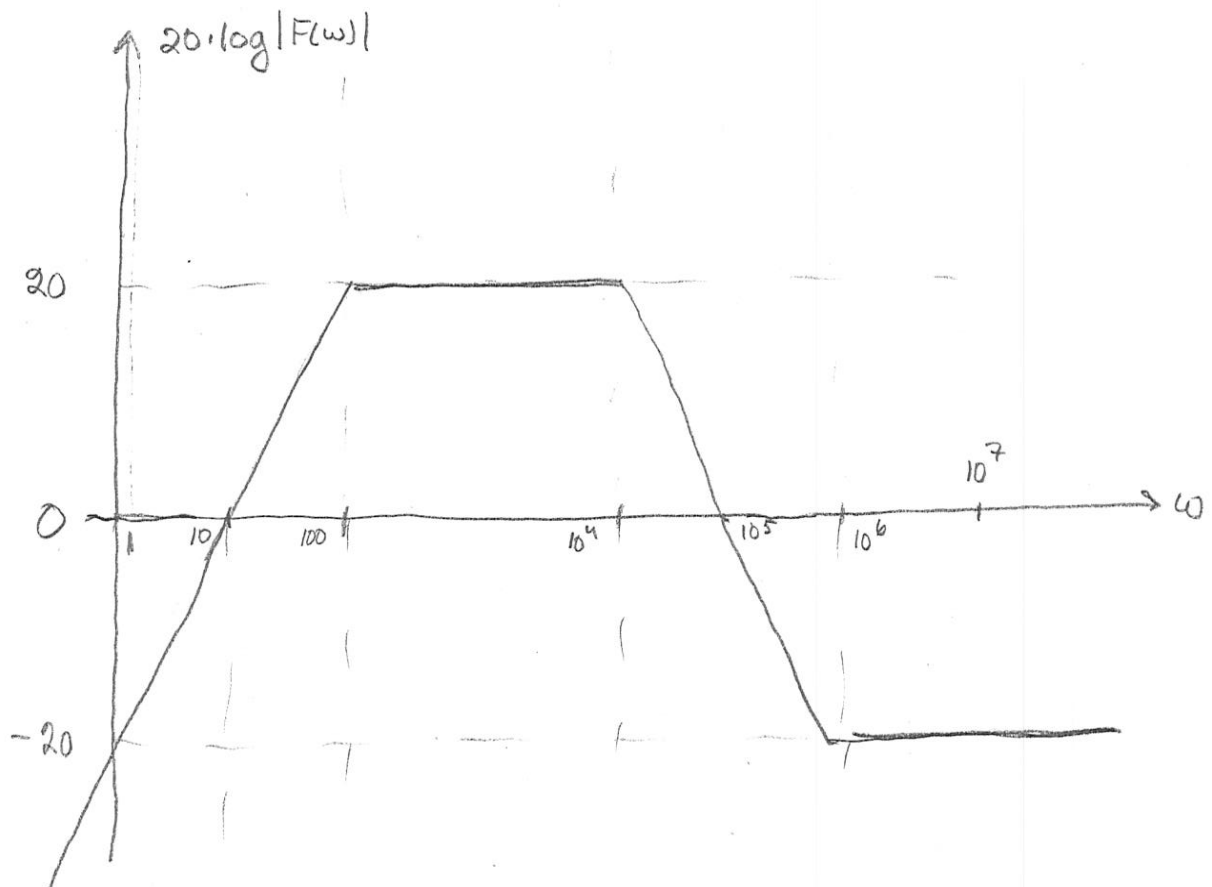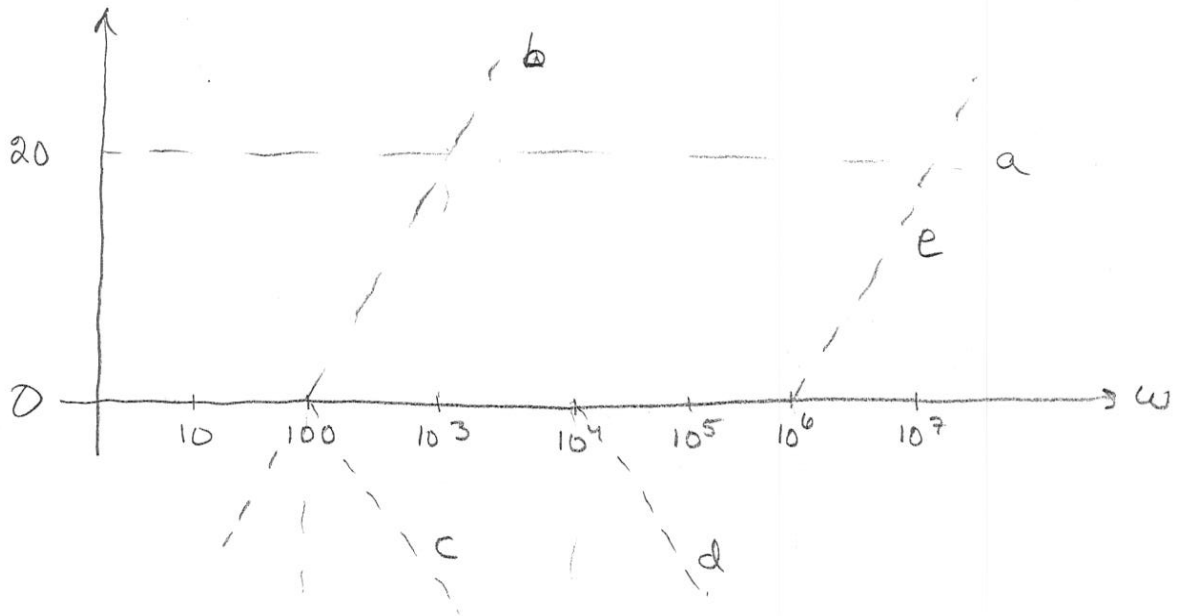$\begin{matrix} b \\ c \end{matrix}$
 $\begin{matrix} e \\ d \end{matrix}$



8. Icke-invertierende Kopplung $\Rightarrow$

$$\bullet F(\omega) = \frac{R_1 + Z}{R_1}$$

$$\bullet Z = R_2 \parallel \frac{1}{j\omega C_2} = \frac{R_2 \cdot \frac{1}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}} = \frac{R_2}{1 + j\omega R_2 C_2} \Rightarrow$$

$$F(\omega) = \frac{R_1 + \frac{R_2}{1 + j\omega R_2 C_2}}{R_1} = \frac{R_1 + R_2 + j\omega R_1 R_2 C_2}{R_1 (1 + j\omega R_2 C_2)} =$$

$$= \frac{R_1 + R_2}{R_1} \cdot \frac{1 + j\omega \frac{R_1 R_2}{R_1 + R_2} \cdot C_2}{1 + j\omega R_2 C_2} =$$


$$= 101 \cdot \frac{1 + j \frac{\omega}{55101}}{1 + j \frac{\omega}{546}} \Rightarrow$$

$$\underline{K = 101}$$

$$\underline{\omega_1 = 55,1 \text{ krad/s}}$$

$$\underline{\omega_2 = 546 \text{ rad/s}}$$

9.

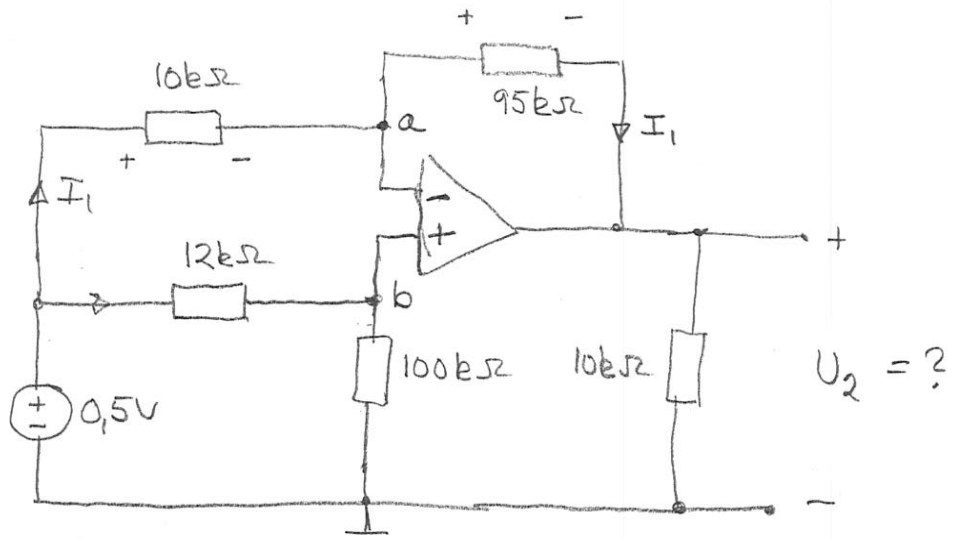

Ideal motkopplad OP $\Rightarrow V_a = V_b$

• instömmar = 0

• $U_2 = V_a - 95k\Omega \cdot I_1$


• $I_1 = \frac{0,5V - V_a}{10k\Omega}$

• $V_a = V_b = \frac{100k\Omega}{100k\Omega + 12k\Omega} \cdot 0,5V = 0,4464V$ (spänningsdelning)

$\Rightarrow I_1 = \frac{0,5V - 0,4464V}{10k\Omega} = 5,357\mu A \Rightarrow$

$U_2 = 0,4464V - 95k\Omega \cdot 5,357\mu A = \underline{\underline{-62,5mV}}$

10a

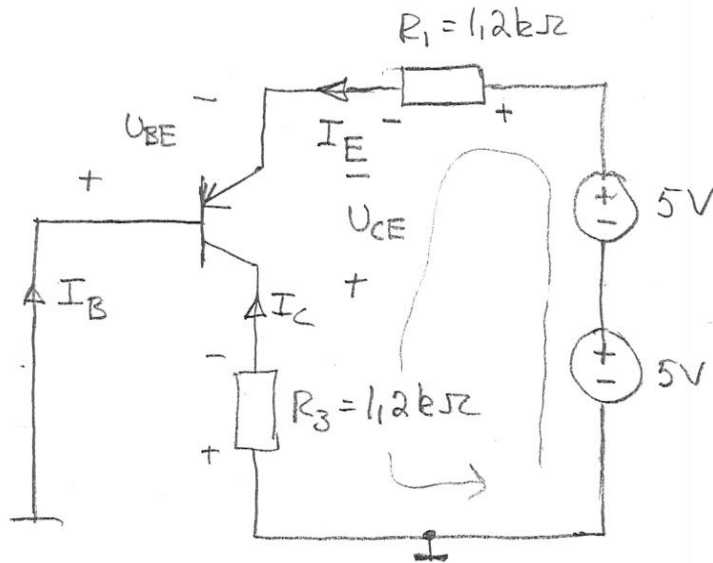

$$h_{FE} = 20$$

$$U_{BE} = -0,7V$$

$$I_C = h_{FE} \cdot I_B = 20 I_B \Rightarrow I_E = -21 I_B$$

$$KVL : +5V + 5V - 1,2k\Omega \cdot I_E + U_{CE} + 1,2k\Omega \cdot I_C = 0 \Rightarrow$$

$$U_{CE} = -10V + 1,2k\Omega (I_E - I_C)$$


$$KVL \text{ ger } I_E : -10V - 1,2k\Omega \cdot I_E + U_{BE} = 0 \Rightarrow$$

$$I_E = \frac{10V + (-0,7V)}{1,2k\Omega} = 7,75mA \Rightarrow I_B = -0,37mA \Rightarrow I_C = -7,38mA$$

$$\Rightarrow U_{CE} = -10V + 1,2k\Omega (7,75mA + 7,38mA) = 8,16V$$

$$U_{CE} > -0,1V \Rightarrow \text{bottnad}$$

10b.

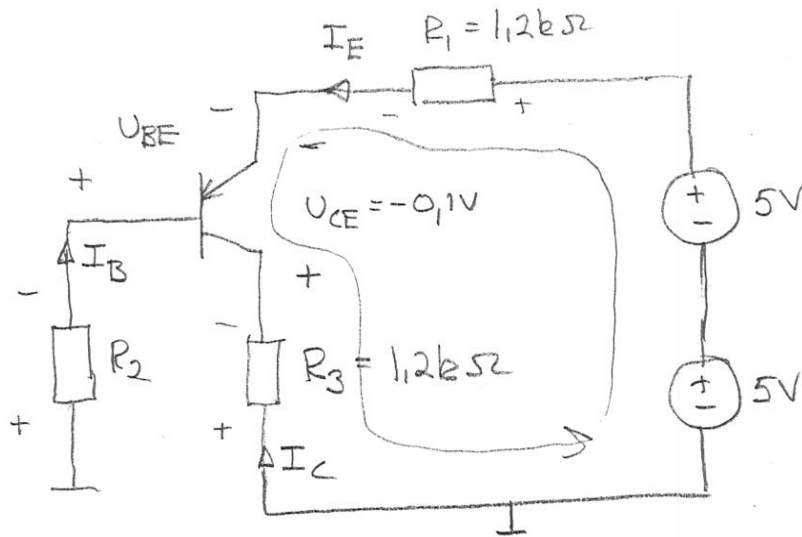

$$I_C = 20 I_B ; I_E = -21 I_B \Rightarrow I_E = -\frac{21}{20} I_C$$

$$KVL: +5V + 5V - 1.2k\Omega \cdot I_E + U_{CE} + 1.2k\Omega \cdot I_C = 0 \Rightarrow$$

$$1.2k\Omega (I_C - I_E) = -10V - U_{CE} = -9.9V \Rightarrow$$

$$1.2k\Omega (I_C + \frac{21}{20} I_C) = -9.9V \Rightarrow I_C = -4.02mA$$

$$\Rightarrow I_E = 4.23mA ; I_B = -0.201mA$$

KVL i basbrettens ger

$$+10V - 1.2k\Omega \cdot I_E + U_{BE} + R_2 I_B = 0 \Rightarrow$$

$$10V - 1.2k\Omega \cdot 4.23mA - 0.7V + R_2 \cdot (-0.201mA) = 0 \Rightarrow$$

$$R_2 = \frac{10V - 1.2k\Omega \cdot 4.23mA - 0.7V}{0.201mA} = \underline{\underline{21k\Omega}}$$

Detta är gränsvärdet $\Rightarrow$

Transistorn bottenad för $R_2 < 21k\Omega$

11a Komplex

$$e(t) = 10 \sin(10^4 t + 20^\circ) \text{ V} \leftrightarrow E = 10 e^{j(10^4 t + 20^\circ)} \text{ V}$$


$$u(t) = 10 \sin(10^4 t + \alpha) \leftrightarrow U = 10 e^{j(10^4 t + \alpha)}$$

$$L \leftrightarrow j\omega L = j10^4 \cdot 20 \cdot 10^{-3} = j200$$

$$C \leftrightarrow \frac{1}{j\omega C} = -j \frac{1}{10^4 \cdot 10^{-6}} = -j100$$

$$R_1 \leftrightarrow 20$$

$$R_2 \leftrightarrow 100$$

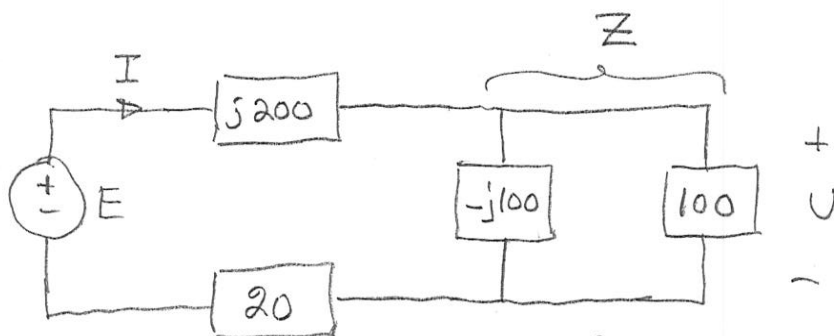

$$U = \frac{Z}{Z + j200 + 20} \cdot E; \quad Z = 100 \parallel -j100 = \frac{100 \cdot (-j100)}{100 - j100} =$$

$$= \frac{-j100}{1 - j} = 50 - j50 = 50\sqrt{2} \cdot e^{-j45^\circ} \Rightarrow$$

$$U = \frac{50\sqrt{2} e^{-j45^\circ}}{50 - j50 + j200 + 20} \cdot E = \frac{50\sqrt{2} e^{-j45^\circ}}{70 + j150} \cdot E =$$

$$= \frac{50\sqrt{2} e^{-j45^\circ}}{165,5 e^{j65^\circ}} \cdot 10 \cdot e^{j(10^4 t + 20^\circ)} \quad V = 4,27 \cdot e^{j(10^4 t - 90^\circ)} \quad V \Rightarrow$$

$$u(t) = 4,27 \cdot \sin(10^4 t - 90^\circ) \text{ V}$$

11b. Färförskjutning mellan $e(t)$ och $i(t)$ $20^\circ \Rightarrow$

$$\arg Z_{\text{Tot}} = \pm 20^\circ$$

$$Z_{\text{Tot}} = R_1 + j\omega L + Z = 20 + j10^4 L + 50 - j50 =$$

$$= 70 + j(10^4 L - 50) \Rightarrow$$

$$\frac{10^4 L - 50}{70} = \pm \tan 20^\circ = \pm 0,364 \Rightarrow$$

$$10^4 L - 50 = \pm 25,48 \Rightarrow$$

$$10^4 L = 50 \pm 25,48 = \begin{cases} 75,48 \\ 24,52 \end{cases} \Rightarrow$$

$$\underline{L = 7,55 \text{ mH}} \quad \text{eller} \quad \underline{L = 2,45 \text{ mH}}$$

induktiv krets

$i(t)$ 20° efter $e(t)$

kapacitiv krets

$i(t)$ 20° före $e(t)$
