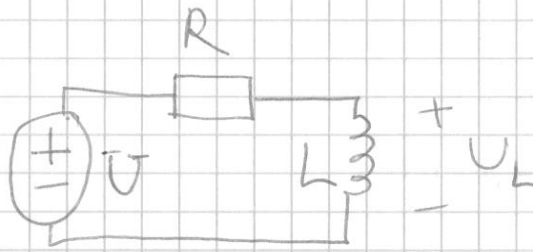


AC 1



$$U = 10 \text{ V}$$

$$R = 100 \, \Omega$$

$$L = 0,050 \text{ H}$$

$$\omega = 2000 \text{ rad/s}$$

Kompleksa spänningar:

$$U_L = U \cdot \frac{j\omega L}{R + j\omega L} = 10 \cdot \frac{j2000 \cdot 0,05}{100 + j2000 \cdot 0,05} =$$

$$= 10 \cdot \frac{j100}{100 + j100} = 10 \cdot \frac{j}{1 + j} =$$


$$= \frac{10 \cdot e^{j90^\circ}}{\sqrt{2} \cdot e^{j45^\circ}} \approx 7,07 \cdot e^{j45^\circ}$$

Tidsfunktion:

$$u_L(t) = \text{Im}(U_L \cdot e^{j\omega t}) = 7,07 \cdot \sin(\omega t + 45^\circ)$$

$$\approx 7,1 \cdot \sin(2000t + 45^\circ) \text{ volt}$$

AC4

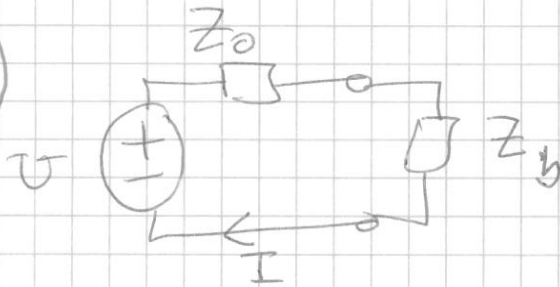

$$Z_0 = 50 - j20 \, \Omega$$

$$U = 5 \, \text{V}$$

$$\omega = 5000 \, \text{rad/s}$$

a)  $Z_b = Z_0^* = \underline{\underline{50 + j20 \, \Omega}}$

$\Rightarrow$  totala impedansen i kretsen blir

$$Z_{\text{tot}} = Z_0 + Z_b = 100 \, \Omega$$

$$I = \frac{U}{Z_{\text{tot}}} = 0,05 \, \text{A}$$

$$P_b = \frac{1}{2} |I|^2 \text{Re}\{Z_b\}$$

$$P_b = I^2 \cdot \text{Re}\{Z_b\} \cdot \frac{1}{2} = 0,05^2 \cdot 50 \cdot \frac{1}{2} = \underline{\underline{0,0625 \, \text{W}}}$$

$\uparrow$   
i detta fall  $\checkmark$  är strömmen reell


$$\approx \underline{\underline{0,062 \, \text{W}}}$$

b)  $Z_b = |Z_0| = \sqrt{50^2 + (-20)^2} \approx 53,85 \, \Omega$   
 $\approx \underline{\underline{54 \, \Omega}}$

$Z_b$  reell  
 $P_b = \frac{1}{2} |I|^2$

$$|I| = \left| \frac{U}{Z_{\text{tot}}} \right| = \frac{5}{|50 - j20 + 53,85|} \approx 0,0473$$
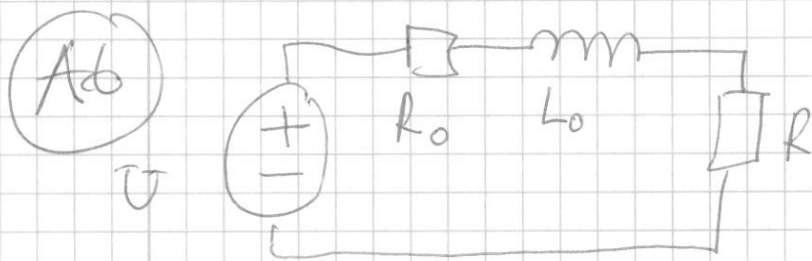
$$\Rightarrow P_b \approx 0,0602 \approx \underline{\underline{0,06 \, \text{W}}}$$



$$U = 15V$$

$$R_0 = 18\Omega$$

$$L_0 = 35 \cdot 10^{-3} H$$

$$\omega = 300 \text{ rad/s}$$

Se  $R$  som belastning och  $R_0, L_0$  som "impedans för källan".

Max. effekt i  $R$  om:

$$R = |R_0 + j\omega L_0| = \sqrt{18^2 + (300 \cdot 35 \cdot 10^{-3})^2}$$

$$\approx 20,84 \Omega \approx \underline{\underline{21 \Omega}}$$

$$P = \frac{1}{2} |I|^2 \cdot R = \frac{1}{2} \left| \frac{U}{Z_{tot}} \right|^2 \cdot R =$$

$$= \frac{1}{2} \left| \frac{15}{18 + j300 \cdot 35 \cdot 10^{-3} + 20,84} \right|^2 \cdot 20,84 \approx \underline{\underline{1,45 W}}$$