

 



Block diagram of measurement systems

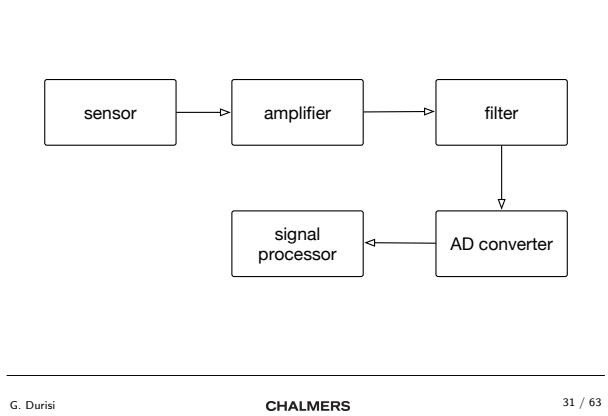


Sampling and aliasing

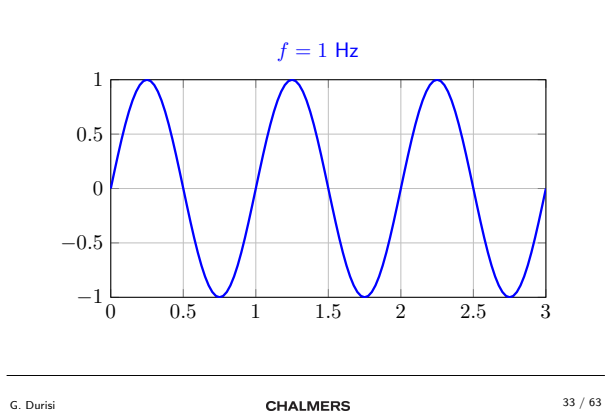


Sampling and aliasing

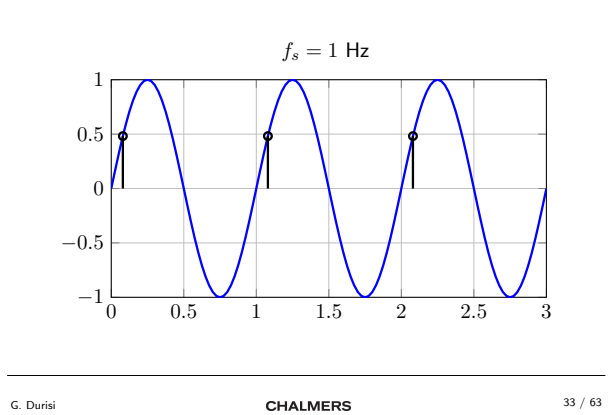


Sampling and aliasing

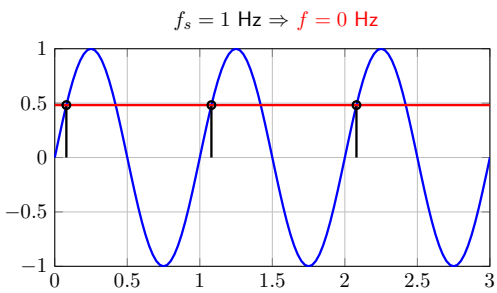


Sampling and aliasing

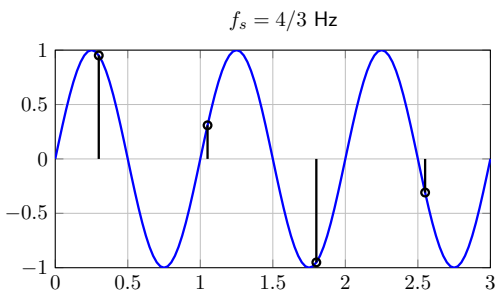


Sampling and aliasing

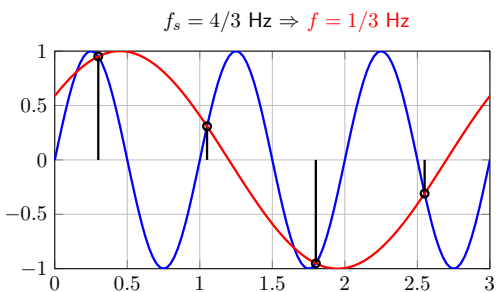


Sampling and aliasing

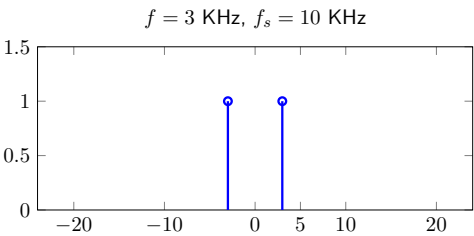


Sampling and aliasing

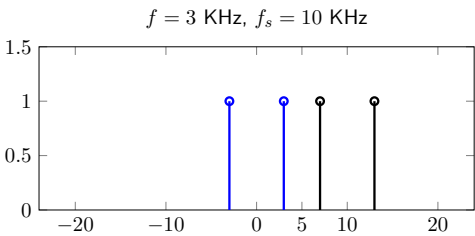


Sampling and aliasing

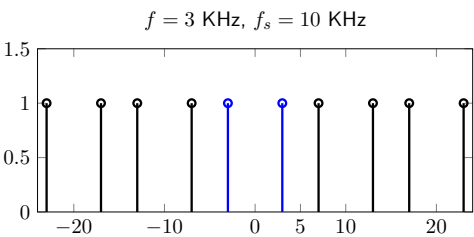


Sampling and aliasing

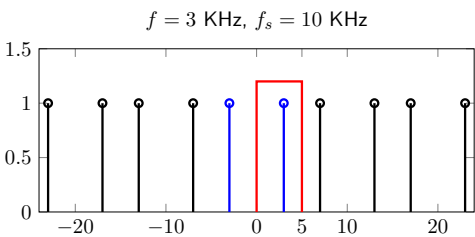


Sampling and aliasing

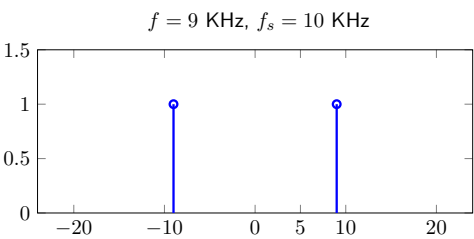



Sampling and aliasing

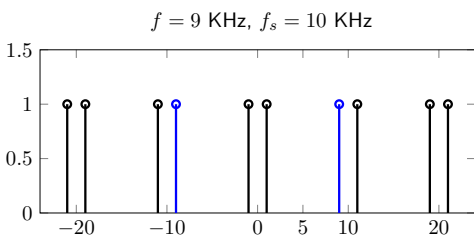


Sampling and aliasing

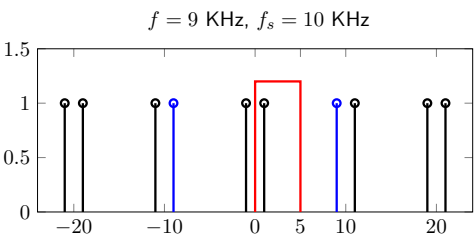

ADC: example

 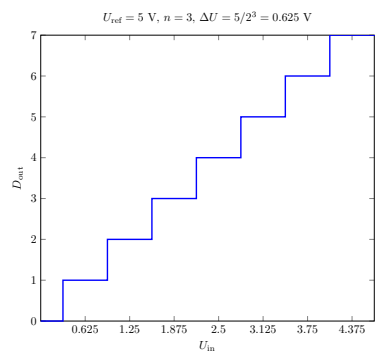

Successive approximation ADC

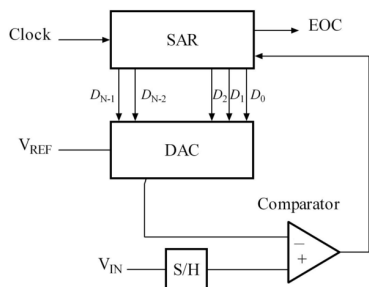

Successive approximation ADC

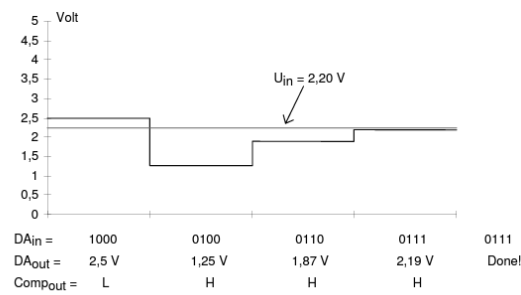


Fig 4.34 The DAC output successively approaches the analog input voltage

Flash ADC

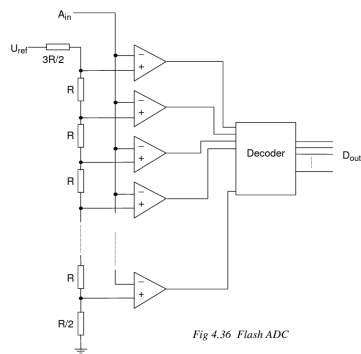


Fig 4.36 Flash ADC

3-Bit Flash ADC

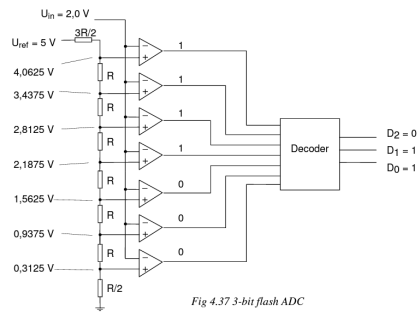


Fig 4.37 3-bit flash ADC

Dual-slope ADC

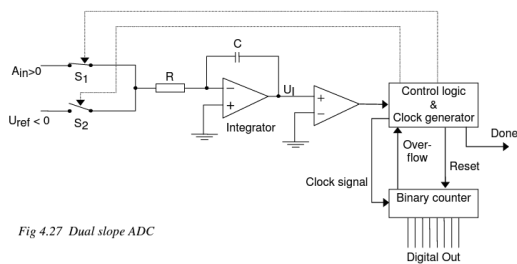


Fig 4.27 Dual slope ADC

Grounding: one end only

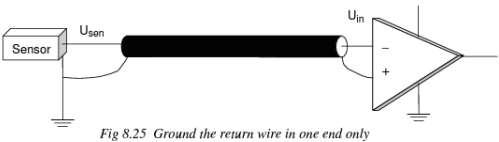


Fig 8.25 Ground the return wire in one end only

Grounding: shielded pair cable

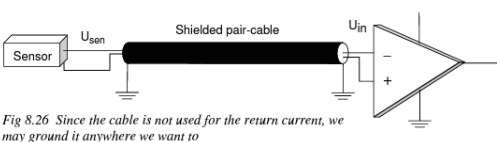


Fig 8.26 Since the cable is not used for the return current, we may ground it anywhere we want to

Grounding: differential signals

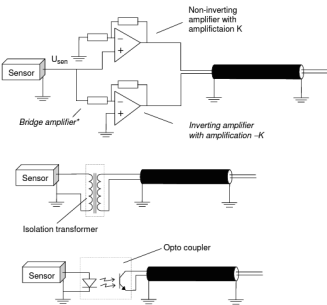


Fig 8.28 There are several ways to make the signal differential