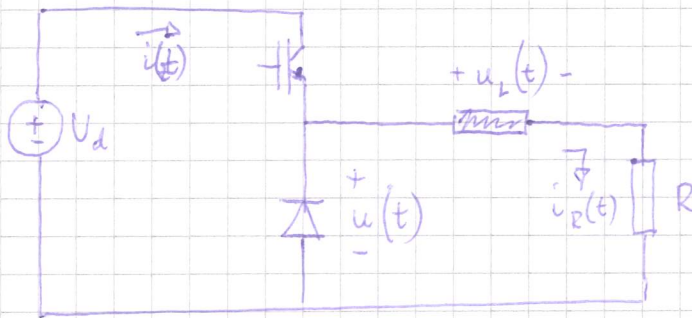


10.1

LS - omriktare

10.1switchfrekv.  $f = 4 \text{ kHz}$  ;  $V_d = 72 \text{ V}$  ;  $R = 4 \Omega$ 



a)  $I_R = 15 \text{ A}$  ;  $t_p = ?$



$$U_R = \frac{t_p}{T} V_d \quad ; \quad T = \frac{1}{f} = \frac{1}{4 \cdot 10^3} = 0,25 \text{ ms} - \text{modulations-period}$$



$$U_R = I_R \cdot R = 15 \cdot 4 = 60 \text{ V}$$
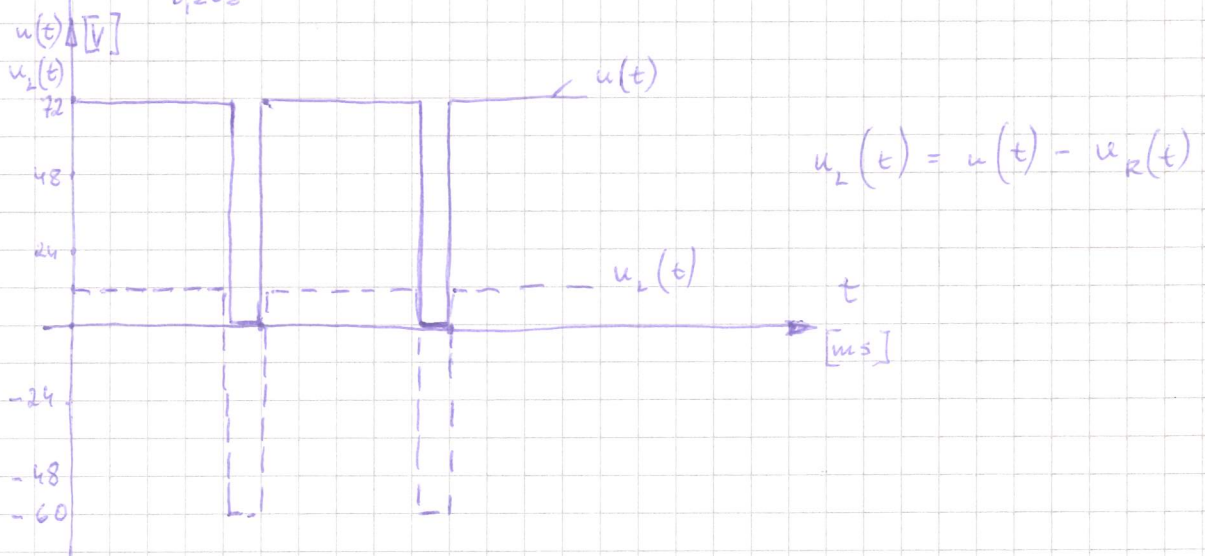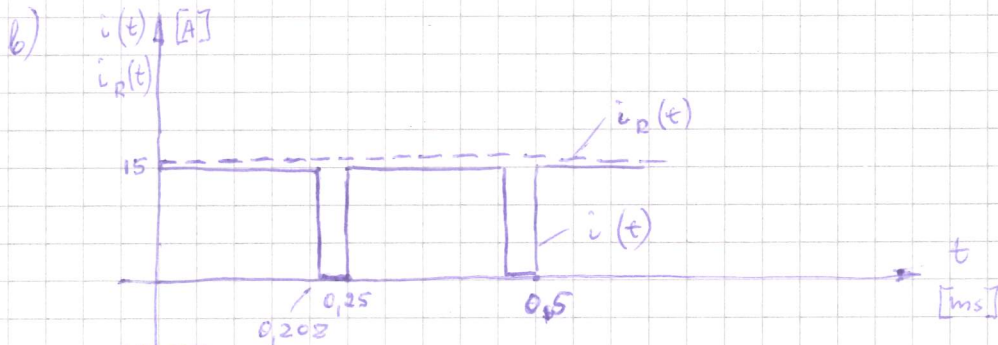
$$t_p = T \frac{U_R}{V_d} = 0,25 \cdot \frac{60}{72} = \underline{\underline{0,208 \text{ ms}}}$$



c)
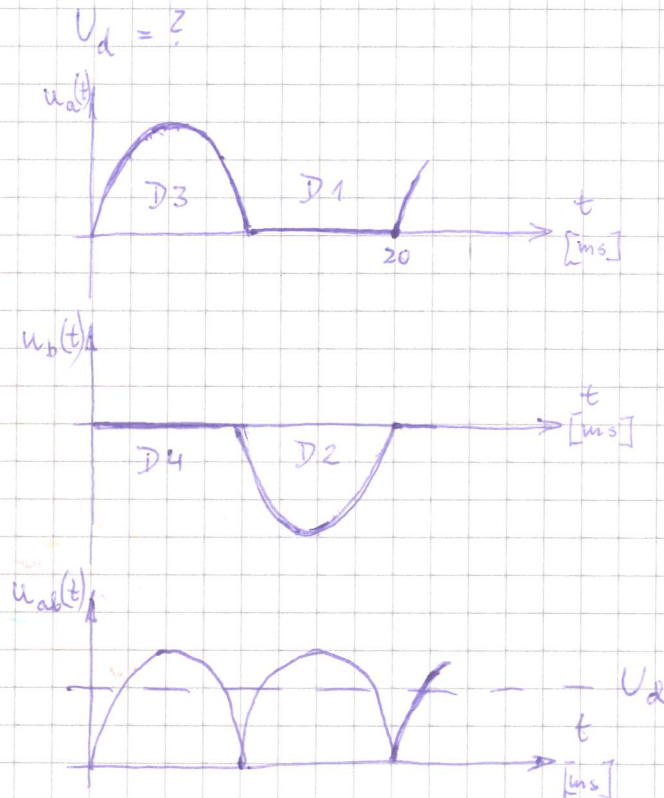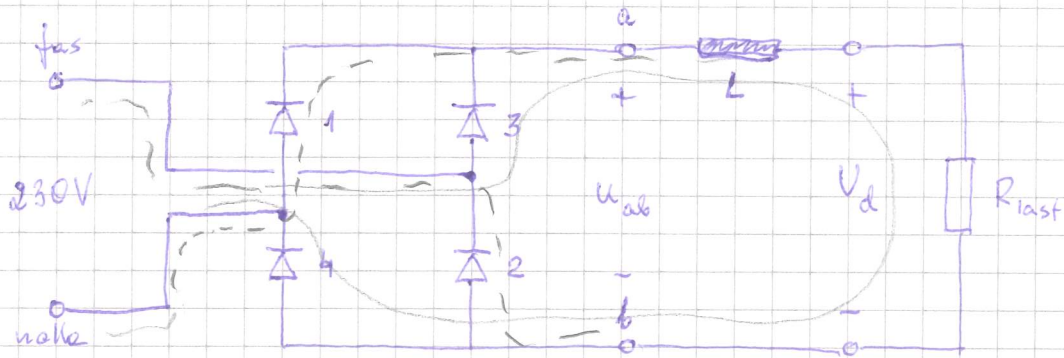
$$\underline{\underline{I_{Rmax} = \frac{72}{4} = 18 \text{ A}}} \quad \underline{\underline{\frac{t_p}{T} = 1}}$$



$U_d$  - medelvärde av  $u_{ab}$


$$\begin{aligned}
 U_d &= \frac{1}{T} \int_0^T u_{ab}(\omega t) d(\omega t) = \\
 &= \frac{1}{\pi} \int_0^\pi \sqrt{2} U_f \sin(\omega t) d(\omega t) = \\
 &= \frac{1}{\pi} \sqrt{2} U_f (-\cos(\omega t)) \Big|_0^\pi = \\
 &= \frac{1}{\pi} \sqrt{2} U_f (1+1) = \frac{2\sqrt{2}}{\pi} U_f = 0,9 U_f
 \end{aligned}$$

$$U_f = 230V \Rightarrow U_d = 0,9 \cdot 230 = \underline{\underline{207V}}$$

10.3

$$U_{\text{batt}} = 96 \text{ V}; \quad I = 10 \text{ A}; \quad U = 300 \text{ V}; \quad T = 0,1 \text{ ms}$$

L o C - mycket stora

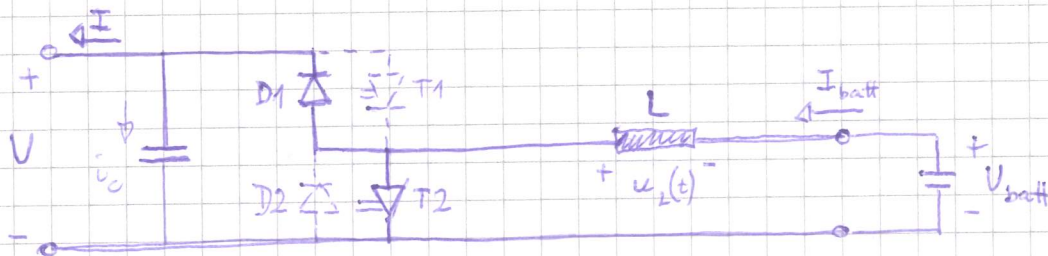

a)  $\frac{t_p}{T} = ?$

$$0 \leq t < t_p \quad D1$$


$$t_p < t < T \quad T2$$

$$U_{\text{batt}} = \frac{t_p}{T} U$$

$$\frac{t_p}{T} = \frac{96}{300} = 0,32$$

$$t_p = 0,32 \cdot 0,1 = \underline{\underline{0,032 \text{ ms}}}$$

b)  $[A] \quad i_c(t)$

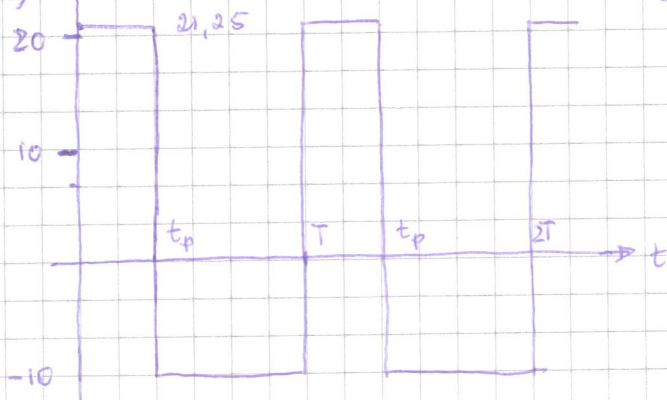


$$U_{\text{batt}} \cdot I_{\text{batt}} = U I$$

$$I_{\text{batt}} = \frac{300}{96} \cdot 10 = 31,25 \text{ A}$$

$$i_c(t) = 31,25 - 10 = 21,25 \text{ A}$$

$[V] \quad u_L(t)$

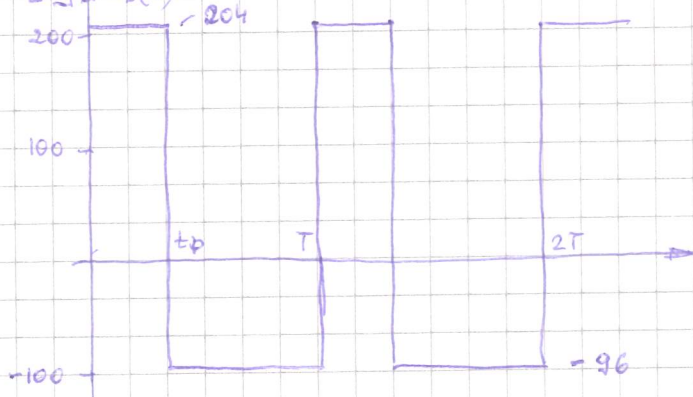

$$u_L = U - U_{\text{batt}} =$$

$$= 300 - 96 = 204 \text{ V} \rightarrow (t_p)$$

$$u_L = -96 \text{ V} \rightarrow (T - t_p)$$

c)  $I_{\text{batt}} = 31,25 \text{ A}$

F6


10.4

F6

LH's fältklingning matas från nätet via trafo och halvöglariknare.

$$U_1 = 230 \text{ V}, \quad U_f = 110 \text{ V}; \quad I_f = 4 \text{ A}; \quad L_f = \infty$$
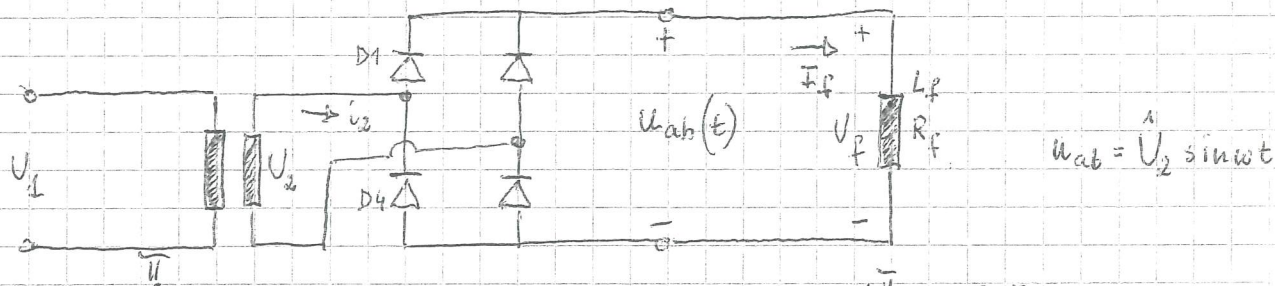
$$\frac{U_1}{U_2} = ?; \quad S_n = ? \quad (\text{sp. föll försummas}); \quad I_{\text{mv}} = ?; \quad U_{\text{back}} = ?$$



$$U_f = \frac{1}{\pi} \int_0^{\pi} \sqrt{2} U_2 \sin \omega t \, d(\omega t) = \frac{\sqrt{2} U_2}{\pi} [-\cos \omega t]_0^{\pi} = \frac{2\sqrt{2}}{\pi} U_2 = 110 \text{ V}$$



medel värde

$$U_2 = \frac{110 \pi}{2\sqrt{2}} = 122,2 \text{ V} \Rightarrow \frac{U_1}{U_2} = \frac{230}{122,2} = 1,88 \text{ trafo omvandling}$$

$$S_n = U_2 \cdot I_2 = U_2 \cdot I_f = 122,2 \cdot 4 = 488,8 \text{ VA}$$

$$I_{\text{mv}} = \frac{4}{2} = 2 \text{ A}$$
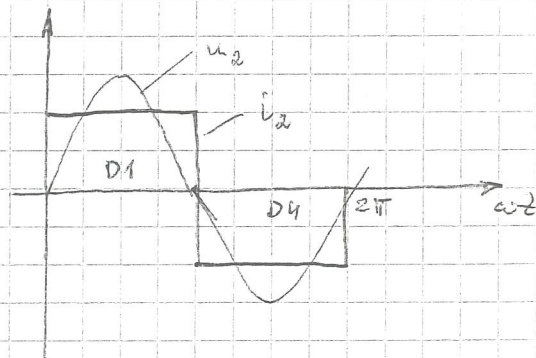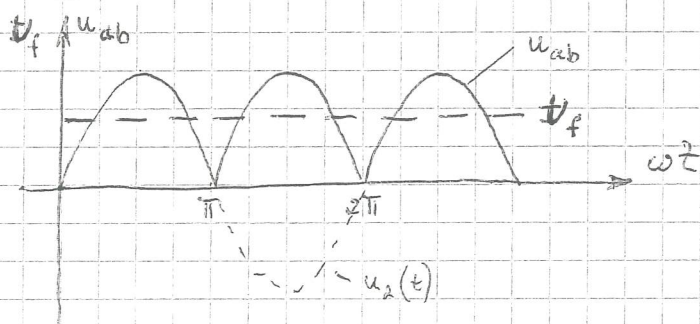
$$U_{\text{back}} = \hat{U}_2 = \frac{110 \pi}{2} = 172,8 \text{ V} \quad (\text{eller } 122,2 \cdot \sqrt{2})$$



$$I_f = I_{\text{mv}} = I_{\text{eff}}$$

Likriktade medelvärde

$$U_{\text{lm}} = \frac{1}{T} \int_0^T |u(t)| \, dt$$

störhetens  
belopp integreras

Effektivvärde


$$U_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T u(t)^2 \, dt}$$

10.5


$$U_b = 12 \text{ V} ; U_m = 24 \text{ V}$$

10.5

a) Upptröskelformerande LS-omriktare;

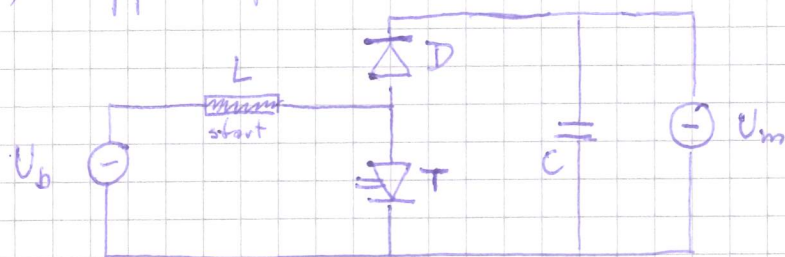

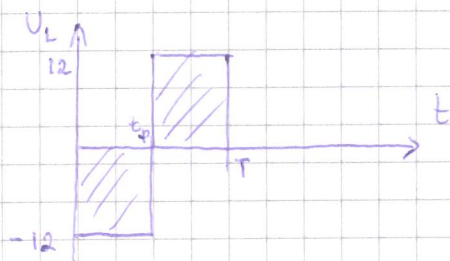b) då T är tänd  $U_L = U_b \rightarrow t_p$   
 T är släckt  $U_L = U_m - U_b \rightarrow T - t_p$




ytor lika

$$U_b \cdot t_p = (U_m - U_b) (T - t_p)$$

$$U_b \cdot t_p = U_m T - U_b T - U_m t_p + U_b t_p$$


$$U_m T - U_b T = U_m t_p$$
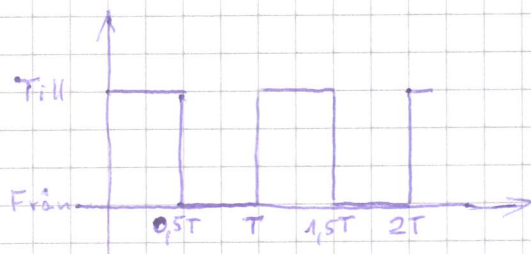
$$t_p = \frac{U_m - U_b}{U_m} T = \frac{12}{24} T = 0,5 T$$



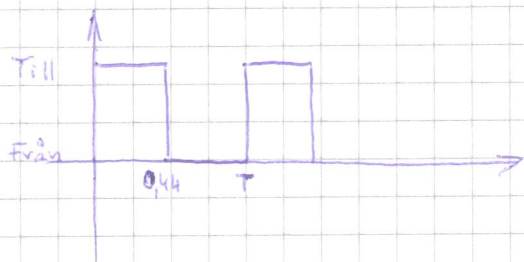
c)  $U_b = 13,5 \text{ V} ; U_m = 24 \text{ V}$

$$\underline{t_p = \frac{24 - 13,5}{24} T = \frac{10,5}{24} T = \underline{\underline{0,4375 T}}}$$



10.6


Varvtalsstyra 12V LM

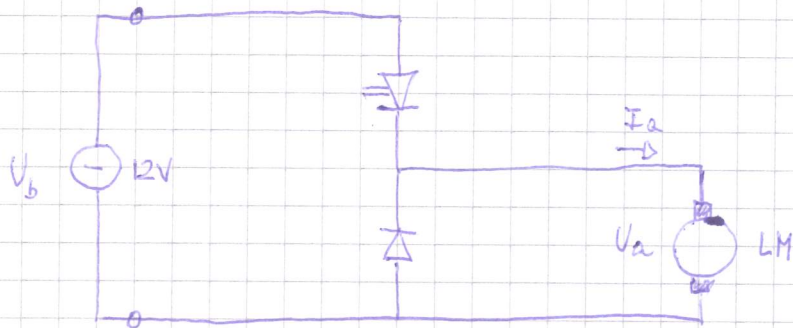10.6a) 12V batteri in  $\rightarrow$  0 ÷ 12V ut

$$V_a = \frac{t_p}{T} V_b$$




b) En enkvaldrant nedspänningshackare

c) En tvåkvaldrant " " "

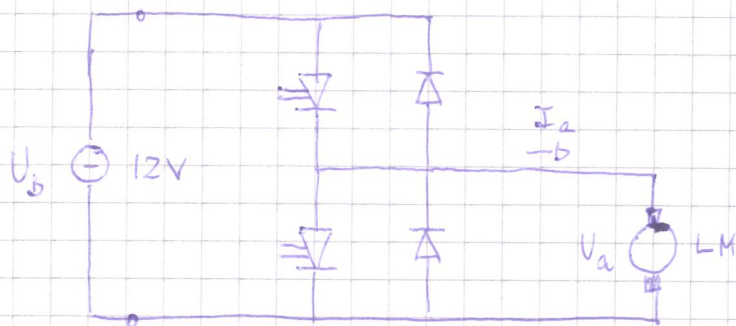

10.7

a) som 10.2  $\rightarrow 207V$

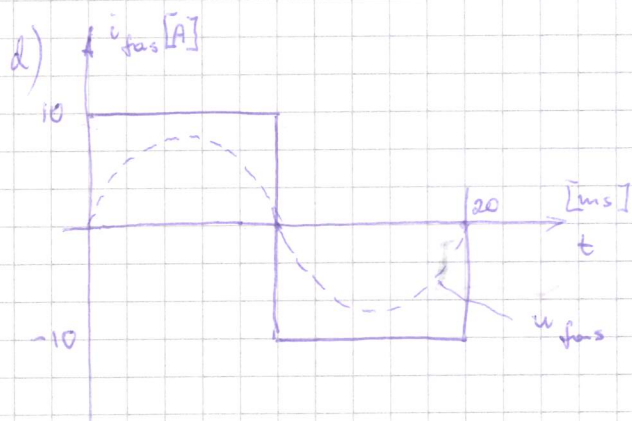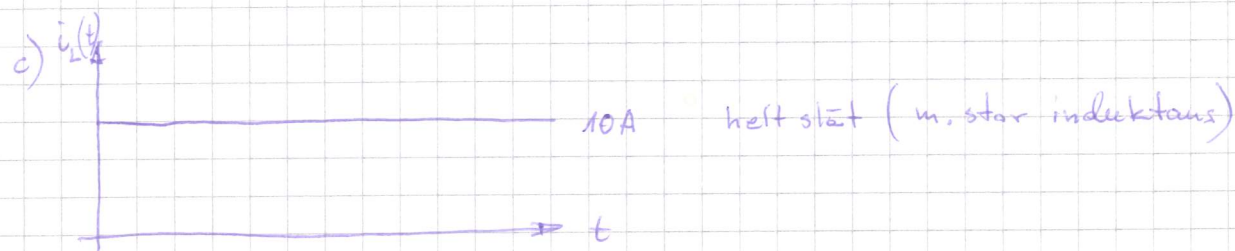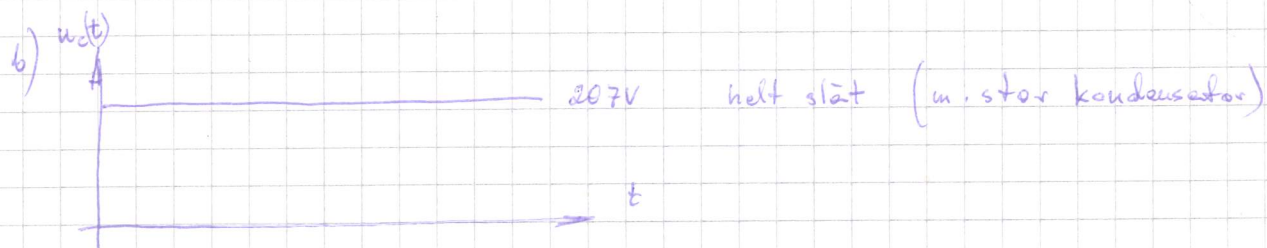

10.7

10.8

3-f. diodkviktere

$$U = 380 \text{ V}$$


a)  $U_{ab}$  - se bilden 5.10 i komp

$$U_d = 1,35 U = 513 \text{ V}$$

b) L - mycket stor

$$I = 10 \text{ A}$$

strömmen genom spolen hållt slät

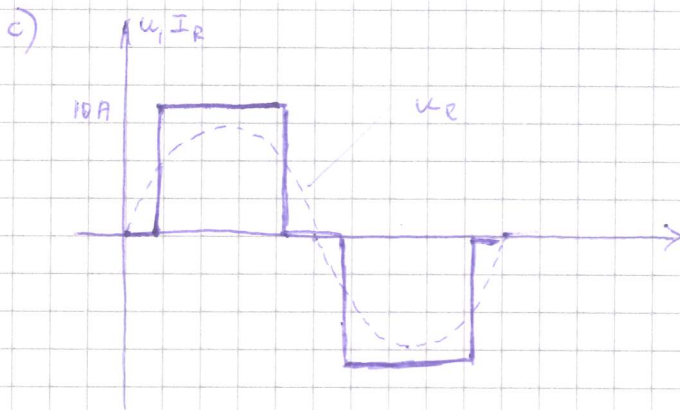

$$30^\circ - 1,67 \text{ ms}$$

$$150^\circ - 8,33 \text{ ms}$$


$$210^\circ - 11,67 \text{ ms}$$

$$330^\circ - 18,33 \text{ ms}$$

$$U_d = \frac{3}{\pi} \int_{-\frac{\pi}{6}}^{\frac{\pi}{6}} \sqrt{2} U \cos \omega t d(\omega t) = \frac{3}{\pi} \sqrt{2} U \sin \omega t \Big|_{-\frac{\pi}{6}}^{\frac{\pi}{6}} =$$
$$= \frac{3}{\pi} \sqrt{2} U (0,5 + 0,5) = \frac{3\sqrt{2}}{\pi} U = 1,35 U$$

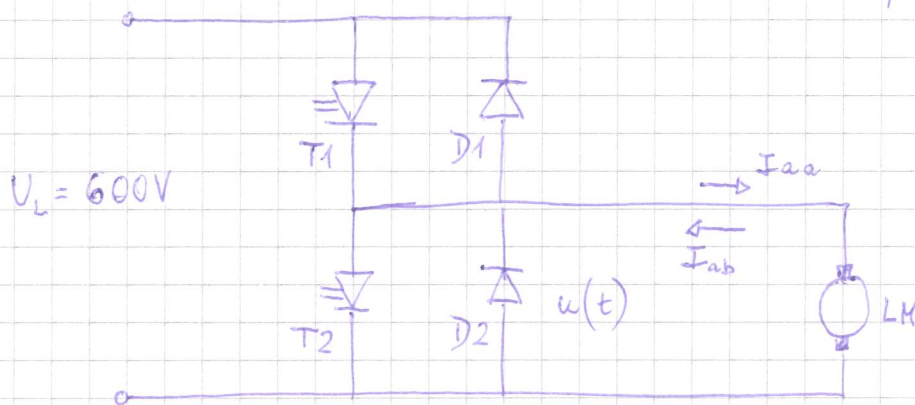10.910.9

$$E_a = 200 \text{ V} ; f = 1 \text{ kHz}$$



a)  $I_{aa} = 200 \text{ A}$   $T1 ; D2$


$T1$  leder  $\rightarrow u(t) = 600 \text{ V}$   $0 < t_p \leq t_p$

$$\frac{t_p}{T} = \frac{E_a}{U_L} \Rightarrow \frac{200}{600} = 0,33$$

nedsp.

$$T = \frac{1}{f} = \frac{1}{10^3} = 10^{-3} \text{ s} \Rightarrow t_p = 0,33 \text{ ms}$$

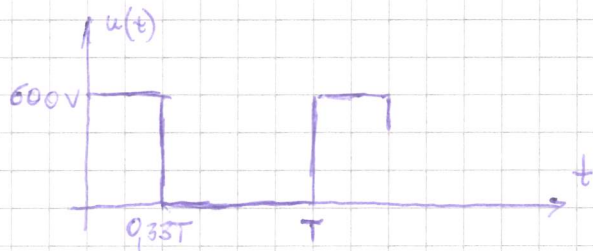$D2$  leder  $\rightarrow u(t) = 0$   $t_p < t < T$



b)  $I_{ab} = -200 \text{ A}$

$D1$  leder  $u(t) = 600 \text{ V}$

$T2$  leder  $u(t) = 0$

uppsp.

fig. som ovan

# F8 Tvåvägs-sexpulskoppling - laddning av batterier


F8

10.10

$$108 \leq U_B \leq 125 \text{ V} \quad I_{\text{lad max}} = 60 \text{ A}$$

$$U_1 = 400 \text{ V} \quad \Delta/\gamma - \text{trafo} \quad \Delta U_v = 0,7 \text{ V}$$
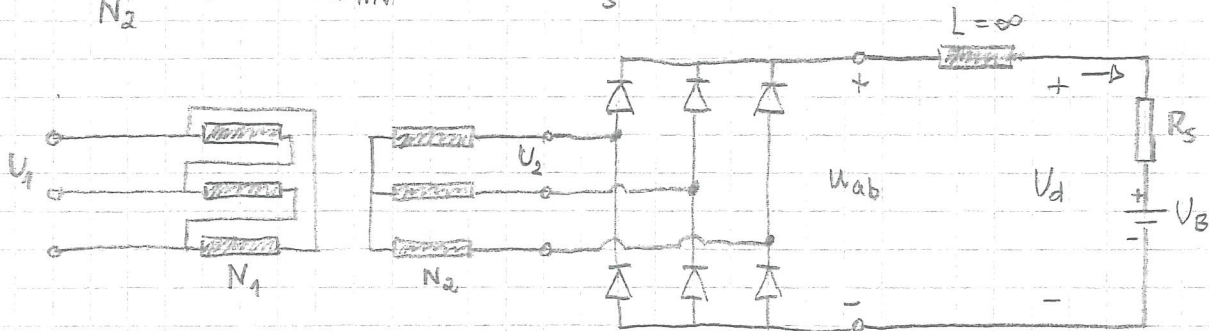
$$\frac{N_1}{N_2} = ? \quad I_{\text{mv}} = ? \quad R_s = ?$$



$$u_{ab}(t) = \sqrt{2} U_2 \cos \omega t$$

OH

$$U_d = \frac{1}{\frac{2\pi}{6}} \int_{-\pi/6}^{\pi/6} \sqrt{2} U_2 \cos \omega t d(\omega t) = \frac{3\sqrt{2}}{\pi} U_2 \left( \frac{1}{2} + \frac{1}{2} \right) \approx 1,35 U_2$$

$$U_d' = U_d + 2 \Delta U_v = U_{B\text{max}} + 2 \Delta U_v = 125 + 1,4 = 126,4 \text{ V}$$

$$U_2 = \frac{126,4}{1,35} = 93,6 \text{ V} \Rightarrow U_{2f} = 54,04 \text{ V}$$


$$\frac{N_1}{N_2} = \frac{U_1}{U_{2f}} = \frac{400}{54,04} = \underline{\underline{7,4}}$$

oms. mellan  
trafos lindningar

Varje ventil leder ström under  $1/3$  period

$$I_{\text{vmv}} = \frac{I_{\text{max}}}{3} = \frac{60}{3} = \underline{\underline{20 \text{ A}}}$$
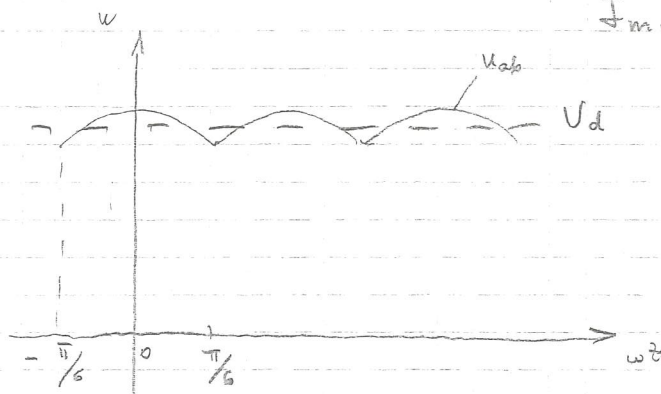
$$\text{Serierisistansen } R_s = \frac{U_{B\text{max}} - U_{B\text{min}}}{I_{\text{max}}} = \frac{125 - 108}{60} = \underline{\underline{0,283 \Omega}}$$



10.11


$$U = 100 \text{ V}$$

10.11

a) som 10.9

b)  $R_a = 1,3 \Omega$  ;  $E_{a0} = 75 \text{ V}$  ;  $n = 1000 \text{ rpm}$  ;  $I_a = 10 \text{ A}$

$$\frac{t_p}{T} = ?$$

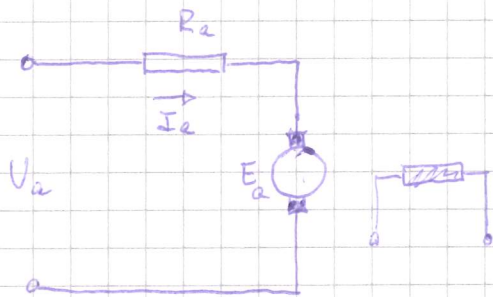

$$U_a = E_a + R_a I_a$$

$$U_a = 75 + 10 \cdot 1,3 = 88 \text{ V}$$

$$\frac{t_p}{T} = \frac{88}{100} = 0,88$$

c)  $I_a = -30 \text{ A}$

$$n = 1000 \text{ rpm}$$

$$U_a = 75 - 30 \cdot 1,3 = 75 - 39 = 36 \text{ V}$$

$$\frac{t_p}{T} = 0,36$$