



# ENM061 - Power Electronic Converters

## 7.5 ECTS, 2017

Mebtu Beza

[mebtu.beza@chalmers.se](mailto:mebtu.beza@chalmers.se)

Chalmers University of Technology  
Department of Electrical Engineering  
Division of Electric Power Engineering



## Lecture outline


### **The flyback converter**

- DC/DC converters with electrical isolation
- The fly back converter
  - ❖ Continuous conduction mode (CCM)
  - ❖ Discontinuous conduction mode (DCM)
  - ❖ Load voltage limitation and purpose of a third winding
- Alternative fly back converter configurations
- Brief description of the Tutorial, PSpice and Practical exercises
- Summary

## Learning outcomes


- Fourier components and total harmonic distortion (THD) for basic waveforms.
- Operating principles of the most common active components (e.g. diode, thyristor, IGBT, and MOSFET) and passive components (e.g. capacitors, transformers and inductors).
- Operation of a pulse width modulation (PWM), the purpose of controlling the desired quantity and the need for a controller circuit within the power electronic converter.
- Analysis of ideal DC/DC converters (e.g. buck, boost, buck-boost, flyback, the forward, the push-pull, half-bridge and full-bridge converters) in CCM and DCM operation.**
- Operating principles of single-phase and three-phase AC/DC inverters with different modulation strategies (e.g. PWM and square wave operation).
- Operation of multilevel converters (e.g. NPC, flying capacitor and MMC topologies) using current and voltage waveform analysis. Pros and Cons of the converter in terms of harmonics and losses.
- Operation of single- and three-phase diode rectifiers operating with voltage-stiff and current-stiff DC-side. Investigating the impact of line impedance within the converter circuit for current commutation.
- Operation of single- and three-phase thyristor rectifiers operating with a current-stiff DC-side and the impact of line impedance for current commutation. Investigating the use of 6/12-pulse configurations.
- Identify simple power electronic converter schematics. Recognizing the different parts in a physical circuit on which basic wave-shape and efficiency measurements is performed.
- Loss calculation in passive and active components. Evaluating the temperature rise in the active components and choosing an appropriate heat-sink. Gaining a basic understanding of component life time.
- Utilizing the software Cadence PSpice to simulate basic power electronic circuits and the practical labs to have a firsthand experience of how real DC/DC converters operate.
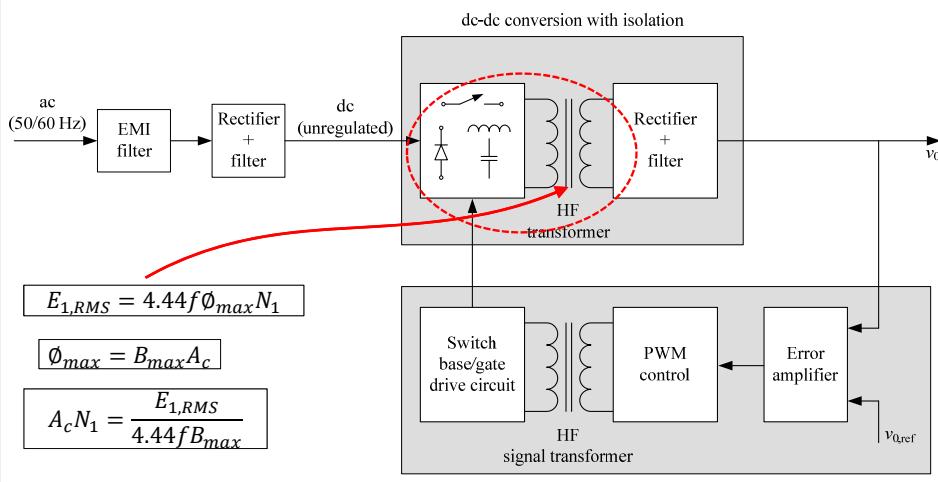
## Switch-mode power supply with electrical Isolation




## Electrical Isolation – The Reason for Isolated Converters

- Avoid circulating currents

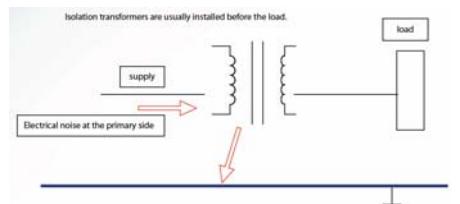


- Safety reasons

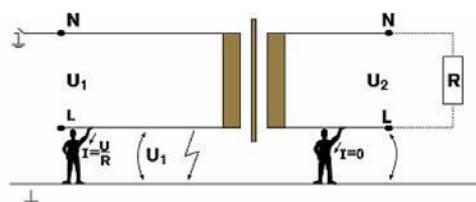

- Multiple outputs and the possibility to have different turns ratios
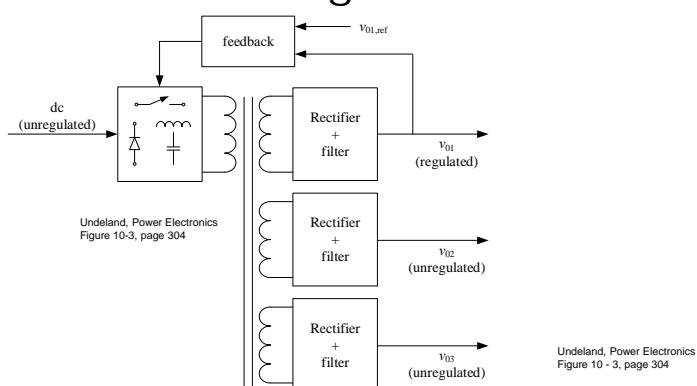
## Electrical Isolation – Power Supply Block Diagram




Undeland, Power Electronics

Figure 10-3, page 304

- Possible to implement multiple electrically isolated outputs from one converter. Only one output can be controlled though.
- Different turns ratio on the secondary windings
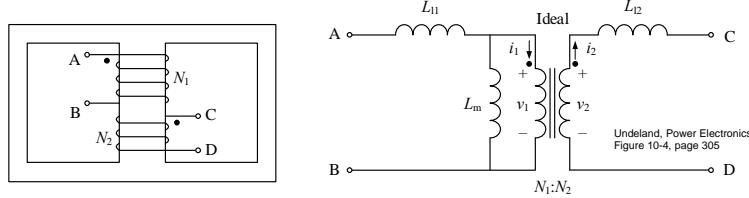
## Electrical Isolation – Transformer Implementation


- For converter applications, a high frequency transformer is used which reduces size and weight compared with a 50Hz transformer



- Desirable to minimize the leakage inductance to reduce unwanted oscillations and therefore the need for snubber circuits
- In general it is desirable to maximize the magnetizing inductance to reduce the magnetizing current (except for the flyback)
- The core excitation can be either unidirectional or bidirectional
- When the current flows into the dot on the primary side – the current flows out of the dot on the secondary side

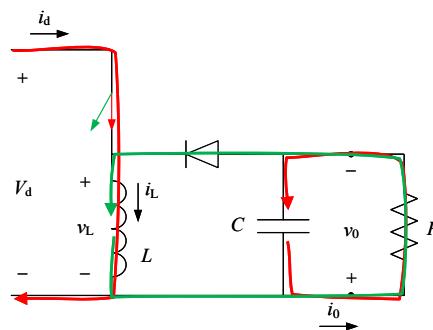
## The Flyback – Derivation From the Buck/Boost Converter

- On: Energy is stored in the inductor
- Off: The energy stored in the inductor is transferred to the load



## The Flyback – Derivation From the Buck/Boost Converter


- On: Energy is stored in the transformer
- Off: The energy stored in the transformer is transferred to the load

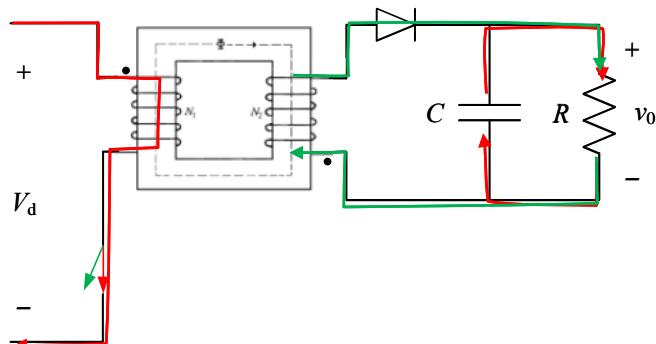

ENM061 – 2017

Lecture 6 – 8/19

## The Flyback – Current Paths with Equivalent Transformer Circuit

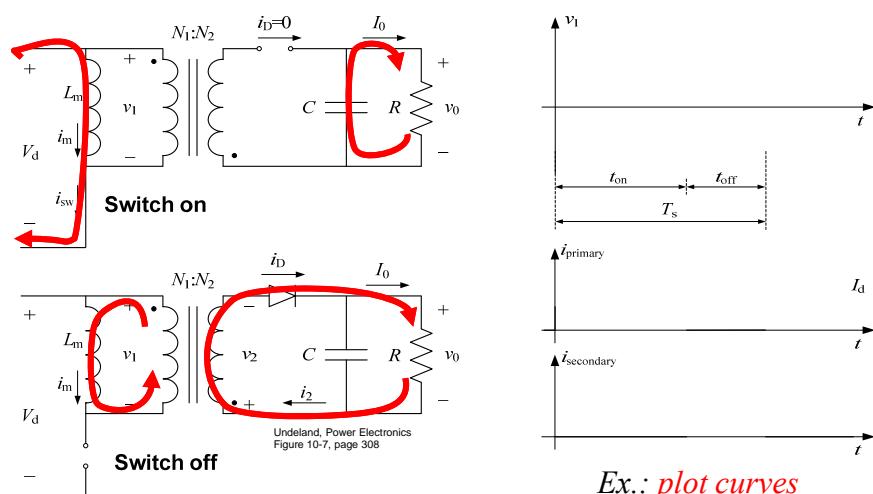


ENM061 – 2017


Lecture 6 – 9/19



## The Flyback – Waveforms in CCM


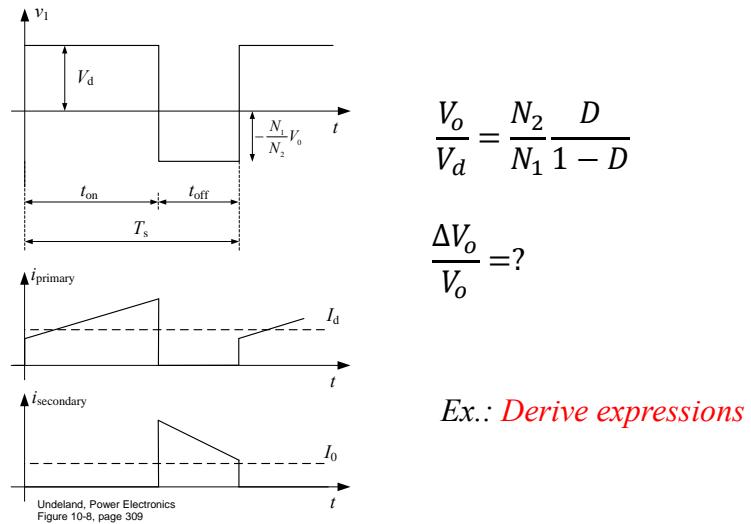


## The Flyback – Waveforms in DCM

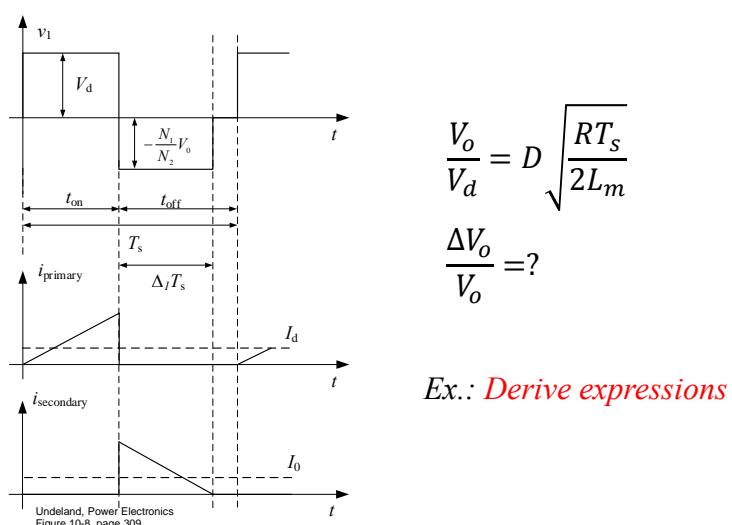

## The Flyback – Core Excitation

- Uses unidirectional core excitation
- An airgap is introduced as to avoid saturation of the core.
- The core is made of ferrite due to the high switching frequency.

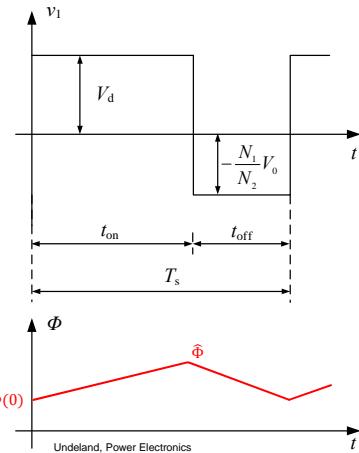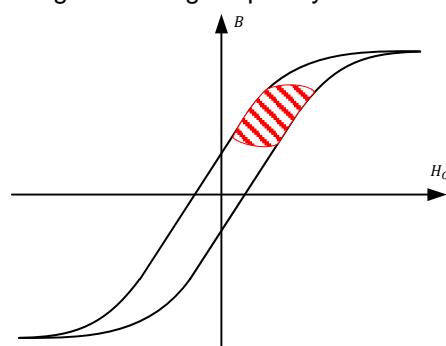


ENM061 – 2017

Lecture 6 – 12/19

## The Flyback – Load Voltage Limiting


- To avoid that the load voltage becomes very high at low load conditions, a third winding can be implemented that feeds energy back to the source

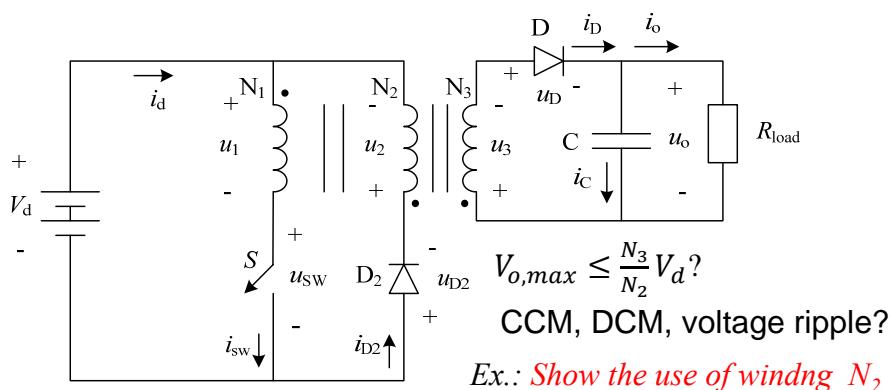

ENM061 – 2017


Lecture 6 – 13/19
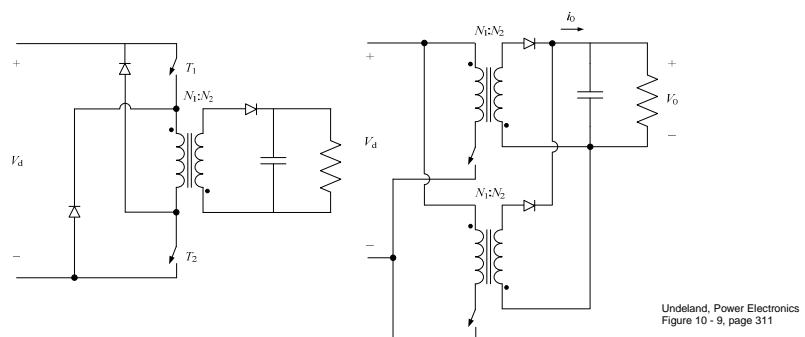
## Two-transistor and Parallelled Flyback Converters




- +L Increased power level and no snubber due to current path through diodes
- +R Increased power level and reliability (due to redundancy), increased effective switching frequency and lower current/voltage ripple
- L&R Increased cost and complexity

## Tutorial 5

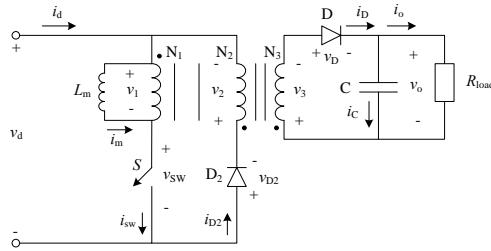


- Derivation of flyback from buck-boost converter
- For DCM, find voltage ratio  $V_o/V_d$  using  $R_{load}$ ,  $f_{sw}$ ,  $L_m$  and  $D$
- Waveforms during a no-load operation with  $D = 0.3$
- Explain how  $N_2$  and  $D_2$  can limit the maximum duty ratio
- When is the flyback operation changing from CCM to DCM

## PSpice 3

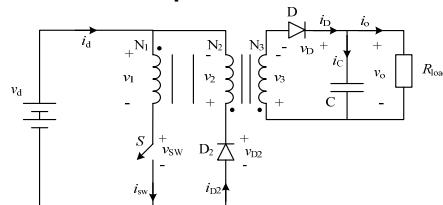

- For CCM and without  $N_2$ , plot waveforms and find  $V_o$ , average and peak-to-peak ripple in the magnetizing current
- Output to input voltage ratio for CCM and DCM and investigate the impact of  $R_{load}$  on the voltage ratio
- Maximum output voltage and the purpose of  $N_2$
- Purpose of a snubber circuit on the switch

## Laboratory 2

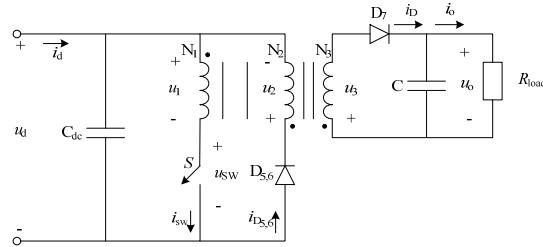

- Find  $L_m$  by calculation and measurement, purpose of  $N_2$
- Output to input voltage ratio for CCM and DCM
- Waveforms and impact of switching frequency on the mode of operation
- Waveforms for a no load operation
- Impact of a snubber circuit and a fast or slow diode ( $D_{5,6}$ )

## Summary

- What is the use of electrical isolation in power electronic converters?
- How do you decide if a flyback converter is operating in CCM or DCM operation?
- What is the purpose of the third winding in a flyback converter transformer and when will it be operational?
- Does the transformer in a flyback require an airgap and why?
- Learning outcome:
  - ❖ Analysis of a flyback DC/DC converter in CCM and DCM operation.