



ENM061 - Power Electronic Converters

7.5 ECTS, 2017

Mebtu Beza

mebtu.beza@chalmers.se

Chalmers University of Technology
Department of Electrical Engineering
Division of Electric Power Engineering



Lecture outline

Multilevel inverter

- Prerequisites for today's lecture
- The Two-level vs Multilevel Inverters
- Neutral Point (Diode) Clamped Inverter (three- and five-level)
- Flying Capacitor Inverter (three- and five-level)
- Modular Multilevel Inverter
- The Half-Bridge vs the Full-Bridge Modular Multilevel Inverter
- Control Strategies
- Summary

Reference:


http://web.eecs.utk.edu/~tolbert/publications/multilevel_book_chapter.pdf



Learning outcomes

- Fourier components and total harmonic distortion (THD) for basic waveforms.
- Operating principles of the most common active components (e.g. diode, thyristor, IGBT, and MOSFET) and passive components (e.g. capacitors, transformers and inductors).
- Operation of a pulse width modulation (PWM), the purpose of controlling the desired quantity and the need for a controller circuit within the power electronic converter.
- Analysis of ideal DC/DC converters (e.g. buck, boost, buck-boost, flyback, the forward, the push-pull, half-bridge and full-bridge converters) in CCM and DCM operation.
- Operating principles of single-phase and three-phase AC/DC inverters with different modulation strategies (e.g. PWM and square wave operation).
- Operation of multilevel inverters (e.g. NPC, flying capacitor and MMC topologies) using current and voltage waveform analysis. Pros and Cons of the converter in terms of harmonics and losses.**
- Operation of single- and three-phase diode rectifiers operating with voltage-stiff and current-stiff DC-side. Investigating the impact of line impedance within the converter circuit for current commutation.
- Operation of single- and three-phase thyristor rectifiers operating with a current-stiff DC-side and the impact of line impedance for current commutation. Investigating the use of 6/12-pulse configurations.
- Identify simple power electronic converter schematics. Recognizing the different parts in a physical circuit on which basic wave-shape and efficiency measurements is performed.
- Loss calculation in passive and active components. Evaluating the temperature rise in the active components and choosing an appropriate heat-sink. Gaining a basic understanding of component life time.
- Utilizing the software Cadence PSpice to simulate basic power electronic circuits and the practical labs to have a firsthand experience of how real DC/DC converters operate.

Single-Phase Inverter Square Wave Mode


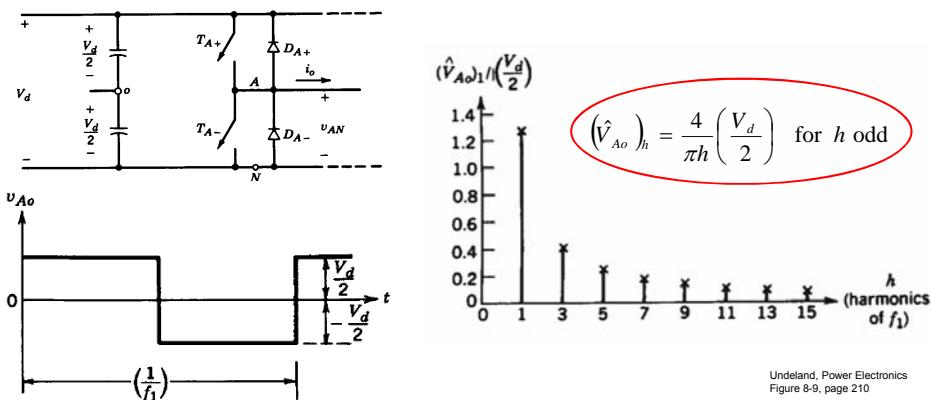
- The output voltage of an inverter operating in square-wave mode results in a high number of odd harmonics



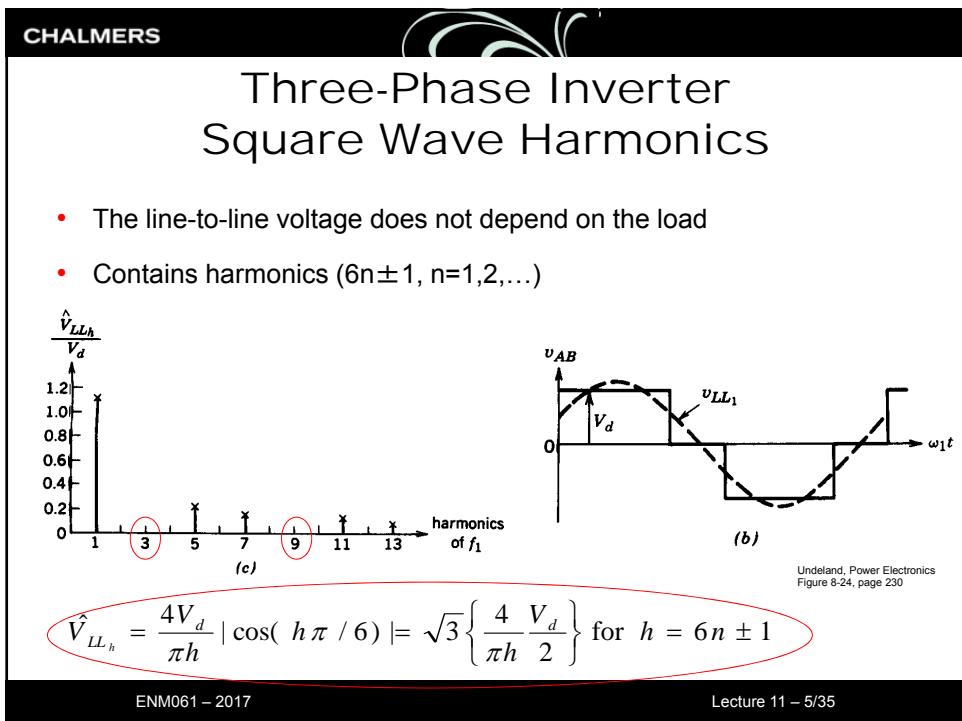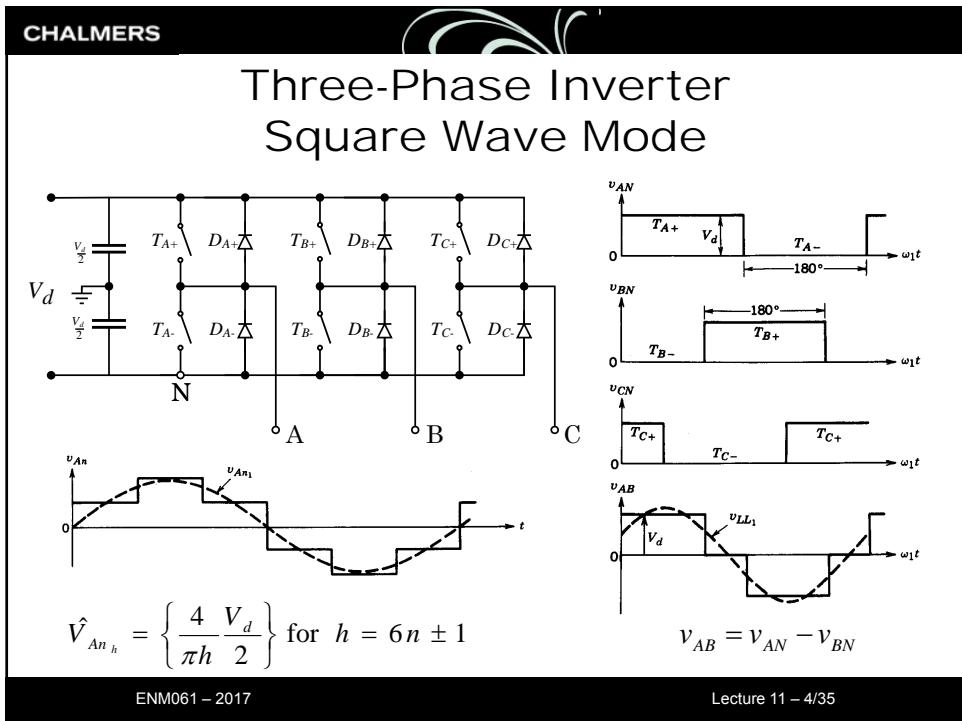

Single-Phase Inverter Bipolar Switching and Voltage Control

- Compare the reference voltage with a triangular voltage with much higher frequency – bipolar switching as for a H-bridge DC/DC-converter

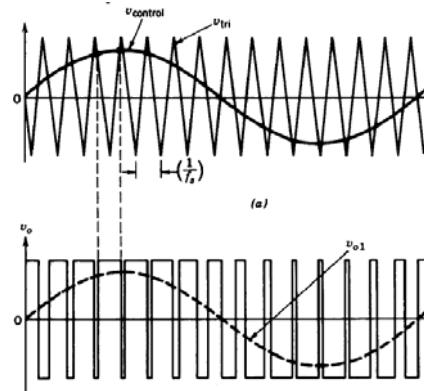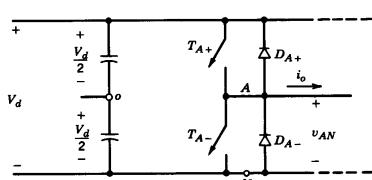


ENM061 – 2017

Lecture 11 – 6/35

Single-Phase Inverter Harmonics in Bipolar Switching


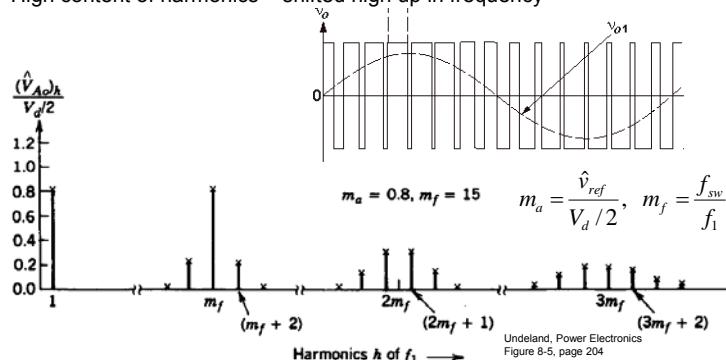
- High content of harmonics – shifted high up in frequency



- Synchronous PWM: when the control voltage and the carrier are synched (when $m_f \leq 21$).
- Asynchronous PWM: when m_f is not an integer. Creates unwanted subharmonics of the fundamental frequency component (OK when $m_f \geq 21$)

ENM061 – 2017

Lecture 11 – 7/35

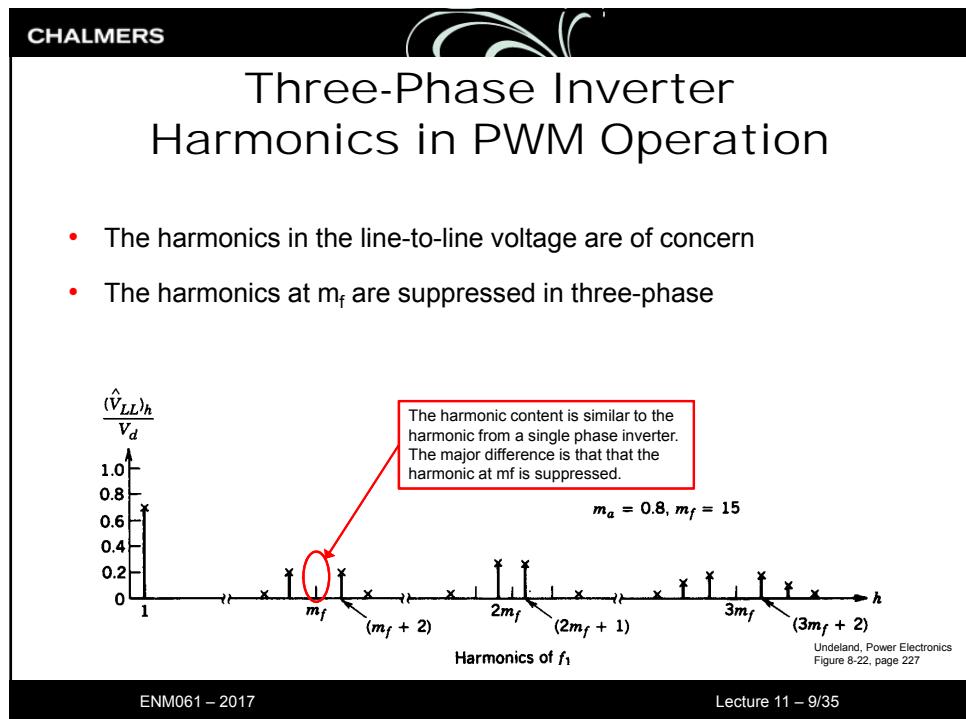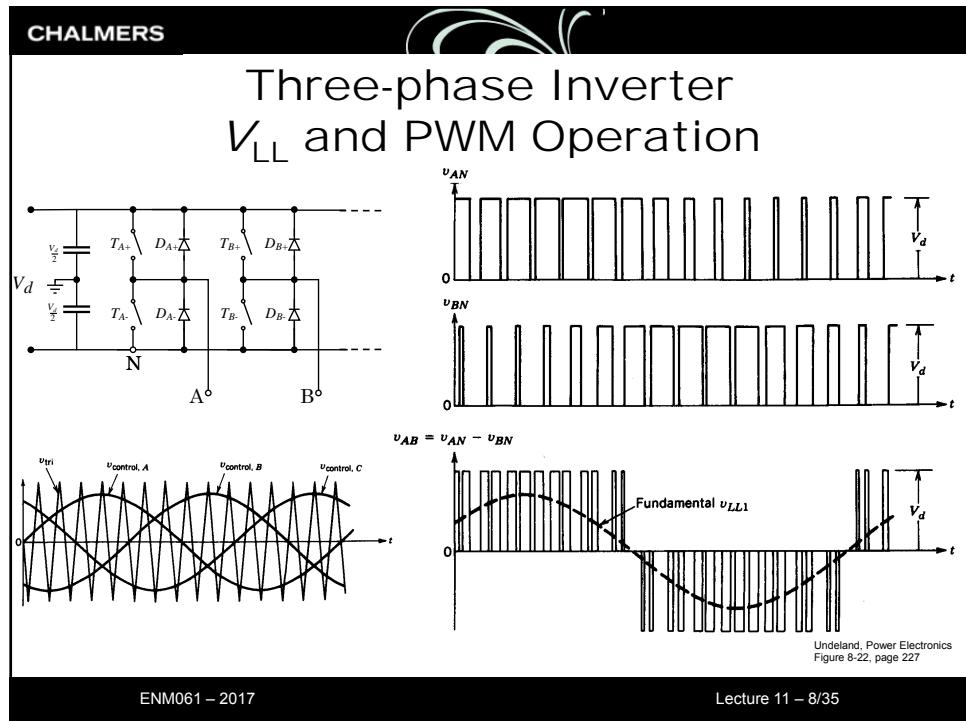

CHALMERS

Summary: Three-phase two-level inverter square wave operation

Line to line voltage
 $v_{AB} = v_{AN} - v_{BN}$

Phase (load) voltage
 $v_{AN} = \frac{2}{3}v_{AN} - \frac{1}{3}(v_{BN} + v_{CN})$

DC-link current

Phase current

Undeland, Power Electronics
Figure 8-24, page 230

- The resulting phase-to-ground voltage is a 2-level square wave
- The line-to-line voltage is a 3-level quasi-square wave
- The phase-to-neutral (load) voltage is a 4-level stair-case wave
- For an RL-load, there is a positive average input current and active power is consumed.

ENM061 – 2017

Lecture 11 – 10/35

CHALMERS

Summary: Three-phase two-level inverter PWM operation

Line to line voltage
 $v_{AB} = v_{AN} - v_{BN}$

Fundamental v_{LL1}

Undeland, Power Electr.
Figure 8-22, page 227

Phase (load) voltage
 $v_{AN} = \frac{2}{3}v_{AN} - \frac{1}{3}(v_{BN} + v_{CN})$

DC-link current

Phase current

- The resulting phase-to-ground voltage is pulse-width modulated and 2-level
- The line-to-line voltage is pulse-width modulated and 3-level
- The phase-to-neutral (load) voltage is pulse width modulated and 5-level
- For an RL-load, there is a positive average input current and active power is consumed.

ENM061 – 2017

Lecture 11 – 11/35




Why Multilevel Inverters?

- The phase-to-ground voltages can have more than 2-levels
- By increasing the number of levels, lower effective switching frequency (as low as the fundamental frequency) can be used. This increases the harmonic performance without increasing the switching losses.
- The output voltage swing is reduced – less insulation stress due to high voltage derivatives
- Typical applications are high power converters such as HVDC transmission or large drive systems




Why Multilevel Inverters?

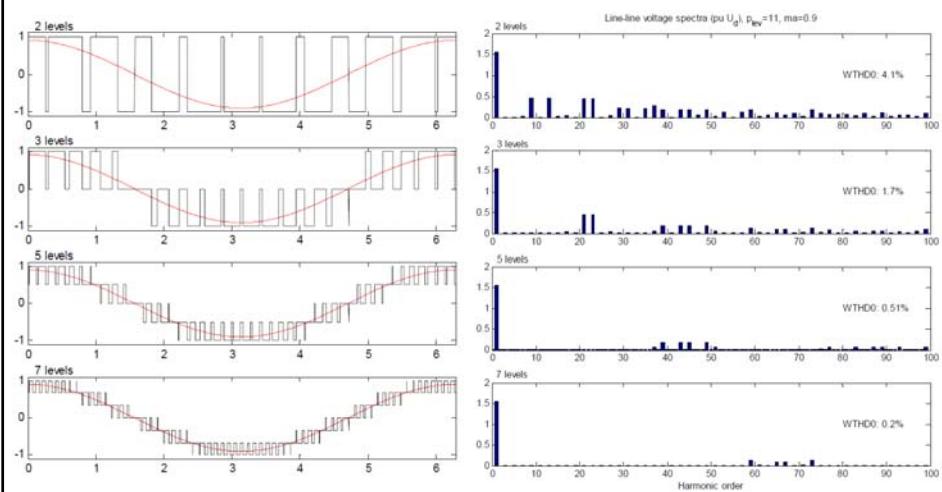

Neutral Point (Diode) Clamped Inverter (Three-Level)


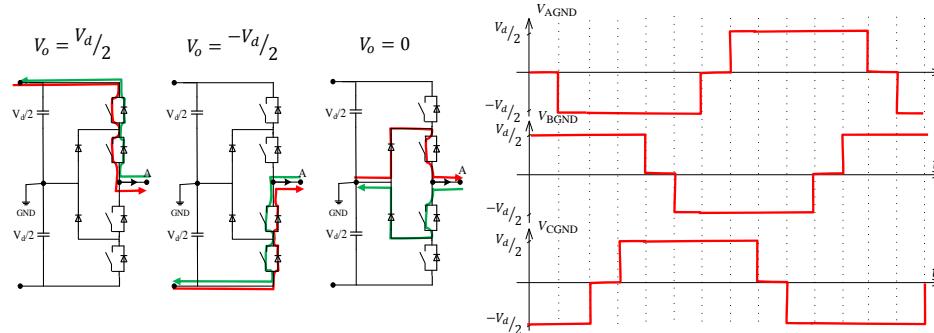
- Bus-splitting common DC-capacitor and diodes for clamping



Ex: Show current paths for the three voltage potentials

Neutral Point (Diode) Clamped Inverter (Three-Level)

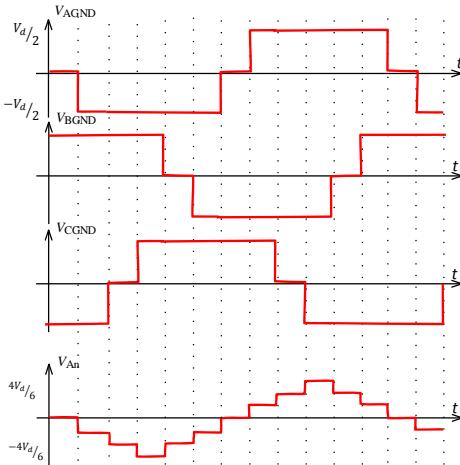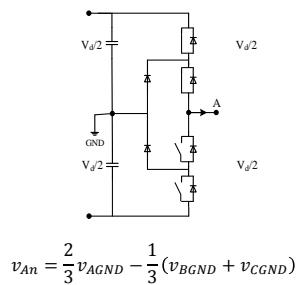- Bus-splitting common DC-capacitor and diodes for clamping
- The resulting phase voltage will have 7 levels (unlike 4 in two-level)
- V_n swings between 0 and $\pm V_d/6$



Neutral Point (Diode) Clamped Inverter (Three Level)

- NPC modules for drive systems (600V/75A)



product family overview

- **all generations**
- 1st - P90x 30BT
- 2nd - P96x 50BT

generation features

- High efficiency three-level topology (2 x 600V = 1200V)
- Dedicated designs for solar and UPS applications
- Ultra high switching frequency
- Compatible with FlowBOOST 0 symmetric
- Low voltage node through
- Available with Press-fit pins

Related Information:

- [Mounting Overview](#)
- [Press-fit technology](#)
- [Pre-Applied Thermal Interface Material](#)

Traditional module


conduction losses:	36W	conduction losses:	62W
switching losses:	118W	switching losses:	28W
total losses:	154W	total losses:	90W
efficiency:	96,65%	efficiency:	98,04%
total rating of Si:	720kVA	total rating of Si:	900kVA

NPC module

conduction losses:	62W
switching losses:	28W
total losses:	90W
efficiency:	98,04%
total rating of Si:	900kVA


ENM061 – 2017

Lecture 11 – 16/35

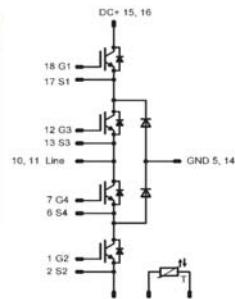


Neutral Point (Diode) Clamped Inverter (Three-Level)

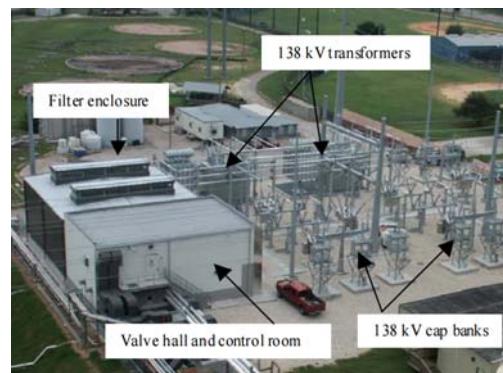- Static VAR Compensator (STATCOM) in Holly, USA.
- Provides $\pm 95 \text{MVA}$
- 32kV Converter Voltage
- Series connected IGBTs
- $m_f=21$
- Designed in 2004 by ABB



Neutral Point (Diode) Clamped Inverter (Five-Level)

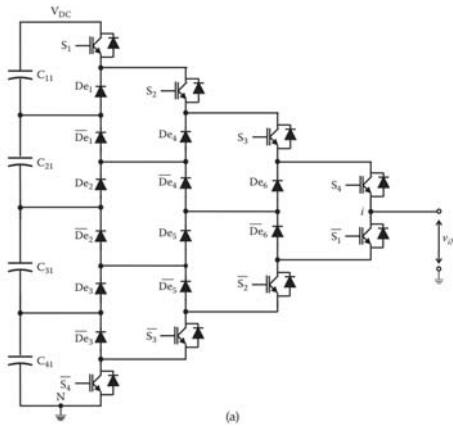
- Complicated design for higher number of voltage levels



[© Gonzalez, Fig 2.12](#)

Active Neutral Point Clamped Inverter (Three-Level)

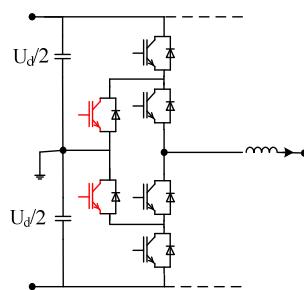- Active neutral point clamped topology – allows for more even distribution of semiconductor losses
- Gives alternatives for implementing the zero-voltage state
- Used in at least two HVDC projects (Murraylink, USA, and Cross Sound Cable Link, Australia) but difficult to scale up to higher voltages than $\pm 150\text{kV}$.



Neutral Point (Diode) Clamped Inverter Pros and Cons

Advantages:


- Any number of levels, but the number of diodes increases
- The capacitors can be pre-charged as a group
- Efficiency is high for the fundamental switching frequency
- Widespread use in MV drives and STATCOMS (mainly 3-level)

Disadvantages:



- The number of clamping diodes required is quadratic ally related to the number of voltage levels.
- For a high number of levels, the commutation mechanisms become complex with many interconnects
- Critical failure propagation with increasing number of levels
- The capacitors at the DC-bus are not minimized/eliminated

Flying Capacitor Inverter (Three-Level)

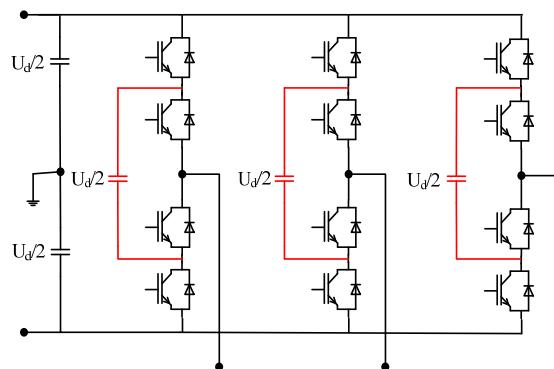
- Similar to the diode-clamped inverter but with capacitors instead
- Proven solutions for low number of voltage levels



Flying Capacitor Inverter (Three-Level)

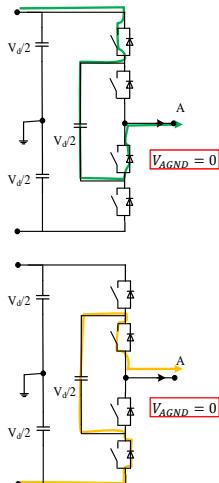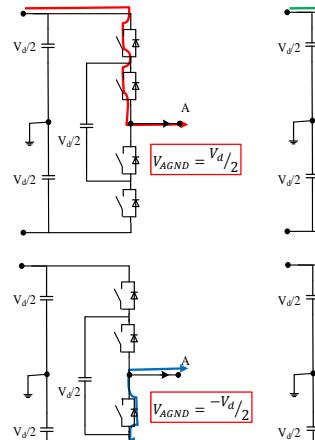


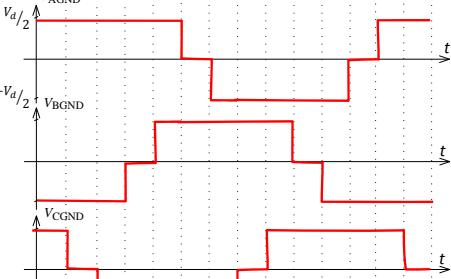Ex: Show current paths for the three voltage potentials



Flying Capacitor Inverter (Five-Level)

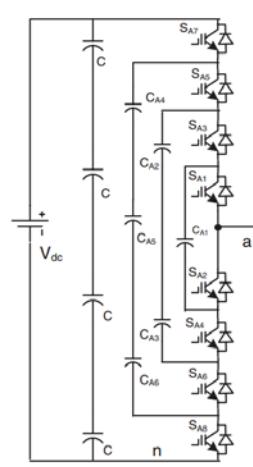- The voltage on each capacitor differs from that of the next capacitor.
- The voltage increment between two adjacent capacitor legs gives the size of the voltage steps in the output waveform.
- Becomes complicated as the number of voltage levels increases



The Flying Capacitor Inverter

Pros and Cons

Advantages:


- Redundant states in the phase voltages are available to balance the voltage levels over the capacitors
- Large number of capacitors enables the inverter to ride through voltage sags

Disadvantages:

- Large capacitors are needed since they must be able to handle the fundamental current
- Long commutation path
- Non scalable construction for higher number of voltage levels
- Requires pre-charging of the capacitors which is complicated
- Complicated control needed to track the voltage level over each capacitor
- More expensive and bulky compared to a diode clamped inverter


Modular Multilevel Inverter

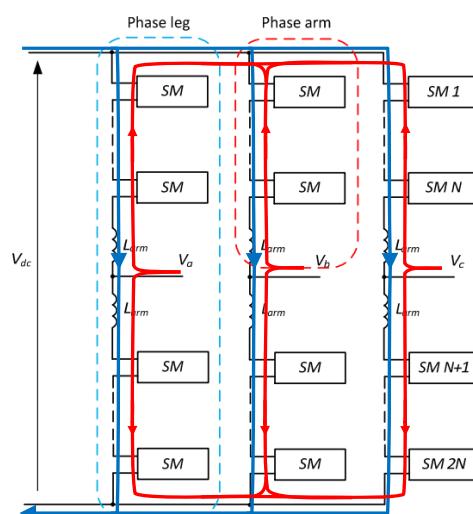- Series connection of identical SMs
- Inductors are placed in each phase arm to limit transient currents
- Scalable with regard to voltage levels, power and voltage rating
- Redundancy possible to replace failing cells
- The DC-side current is equally distributed between the legs
- The AC-current is divided equally in the upper and the lower arm in each leg




Modular Multilevel Inverter

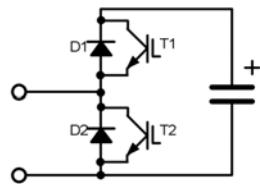- Simplest submodule topology for MMC
- Low semiconductor cost and minimized losses
- No possibility for electronic DC-current limitation
- High volume of installed capacitors




A half-bridge submodule (SM)

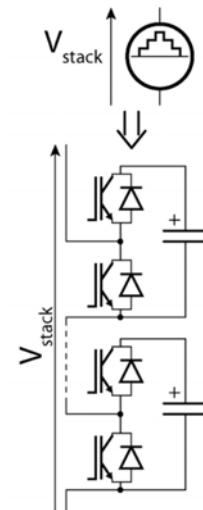


Modular Multilevel Inverter

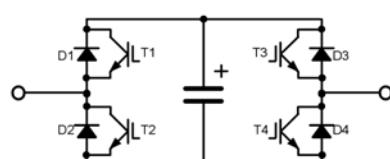- For a full-bridge configuration, AC/AC-conversion can be performed
- Double conduction losses in comparison to the half bridge
- Electronic DC-current limitation




A full-bridge submodule (SM)

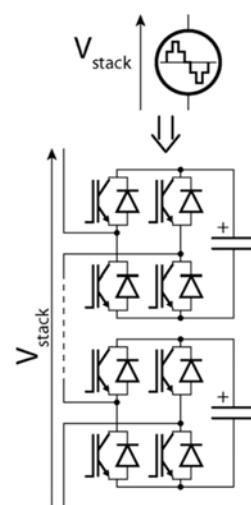


Control of the Modular Multilevel Inverter

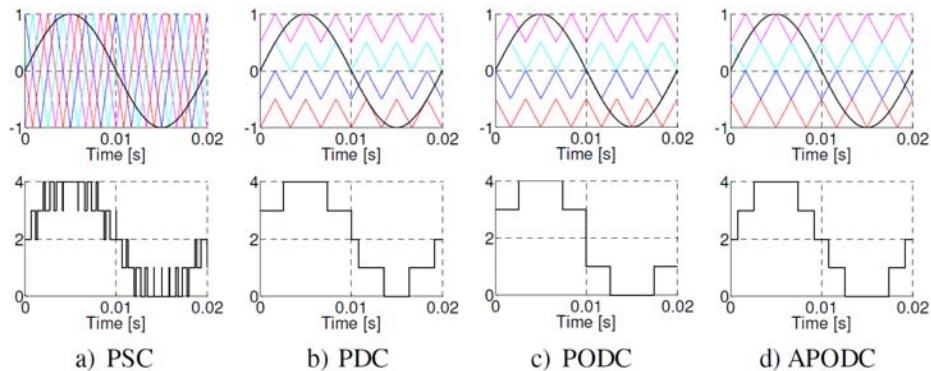- As for the previous topologies, carrier based modulation methods (PWM) can be used
- Different carriers gives various compromises between switching frequency and harmonics




Control of the Modular Multilevel Inverter

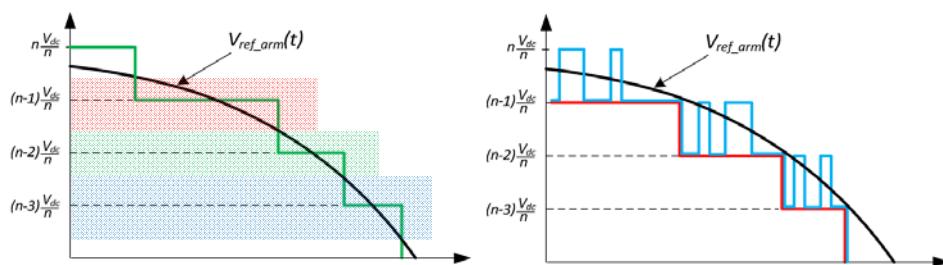- Nearest Level Modulation (NLM) is often used for high voltage applications
- For inverters with large number of cells, cells can be matched so that the output voltage matches the reference with fundamental switching frequency
- With a lower number of voltage levels, one cell in each arm can be modulated which lowers the harmonics



Modular Multilevel Inverters in Power System Applications

- HVDC Light by ABB
- DolWin in the north sea outside Hamburg, commissioned during 2016 (916MW, $\pm 320\text{kV}$, 45km + 90km cables)

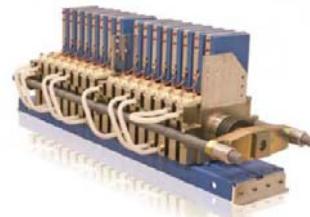


ENM061 – 2017

Lecture 11 – 30/35

Modular Multilevel Inverters in Power System Applications

- HVDC Plus by Siemens
- Baixas – Sta. Llogaia interconnection (65km, 2000MW, $\pm 320\text{kV}$)

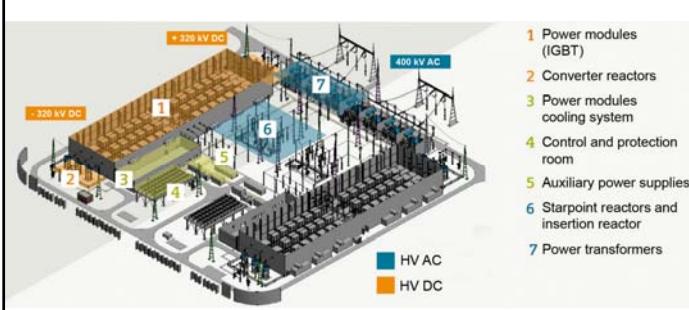


ENM061 – 2017

Lecture 11 – 31/35

Control of the Cascaded Full Bridge Inverter

- A typical modulation scheme is Selective Harmonic Elimination
- All switches operate with the fundamental frequency which gives low losses
- For each module, the switching angle (α) is controlled.
- For N switching angles, N independent equations and degrees of freedom can be obtained which can be used to eliminate $(N-1)$ harmonics and an adjustable amplitude modulation ratio (m_a)

[@ Guan, Song, Ye](#)

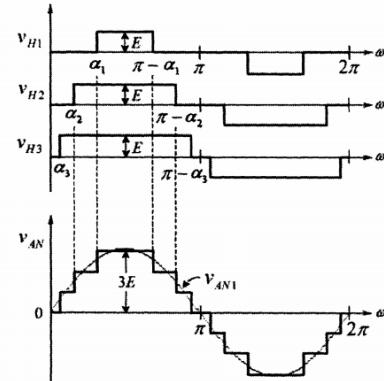

The Cascaded Full Bridge Inverter Pros and Cons


Advantages:

- The number of voltage levels is twice the number of DC-sources
- Modularized solution for each cell simplifies packaging and manufacturing
- For an electric vehicle application, the inverter losses can be reduced significantly if MOSFETs are used instead of IGBTs

Disadvantages:

- A separate DC-source is required for each cell
- A large pulsed current is drawn from each DC-source (battery) which gives increased losses and increases the need for filtering

Tutorial 9

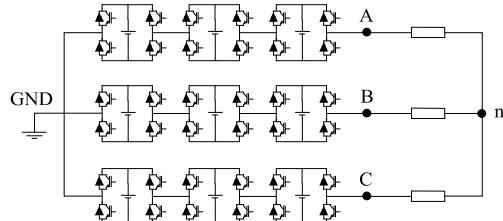

Assume 80°, 140° and 160° connection of the cells in a phase per half-cycle

- Plot phase to neutral and ground, the line-to-line and neutral to ground voltages
- THD of the phase to neutral voltage and comparison with two-level case in square-wave operation case
- Average and RMS value of the dc-current from the dc sources and its comparison to two-level square-wave operation case

Summary

- Pros and cons of the two-level vs multilevel inverters
- Pros and cons of the various multilevel inverters
- Basic operation of a Neutral Point (Diode) Clamped Inverter
- Basic operation of a Flying Capacitor Inverter
- Basic operation of a Modular Multi Level Inverter
- Pros and cons of the Cascaded Half- and Full-Bridge Inverters
- Learning outcome:
 - ❖ Operation of multilevel inverters (e.g. NPC, flying capacitor and MMC topologies) using current and voltage waveform analysis. Pros and Cons of the converter in terms of harmonics and losses.