



ENM061 - Power Electronic Converters

7.5 ECTS, 2017

Mebtu Beza

mebtu.beza@chalmers.se

Chalmers University of Technology
Department of Electrical Engineering
Division of Electric Power Engineering



Lecture outline

The three-phase thyristor rectifier


- Three-phase thyristor rectifiers without source inductance
- Source inductance and current commutation
- Three-phase thyristor rectifier as inverter
- Impact of thyristor loads
- Practical applications of three-phase thyristor rectifiers
- Summary



Learning outcomes

- Fourier components and total harmonic distortion (THD) for basic waveforms.
- Operating principles of the most common active components (e.g. diode, thyristor, IGBT, and MOSFET) and passive components (e.g. capacitors, transformers and inductors).
- Operation of a pulse width modulation (PWM), the purpose of controlling the desired quantity and the need for a controller circuit within the power electronic converter.
- Analysis of ideal DC/DC converters (e.g. buck, boost, buck-boost, flyback, the forward, the push-pull, half-bridge and full-bridge converters) in CCM and DCM operation.
- Operating principles of single-phase and three-phase AC/DC inverters with different modulation strategies (e.g. PWM and square wave operation).
- Operation of multilevel converters (e.g. NPC, flying capacitor and MMC topologies) using current and voltage waveform analysis. Pros and Cons of the converter in terms of harmonics and losses.
- Operation of single- and three-phase diode rectifiers operating with voltage-stiff and current-stiff DC-side. Investigating the impact of line impedance within the converter circuit for current commutation.
- Operation of single- and three-phase thyristor rectifiers operating with a current-stiff DC-side and the impact of line impedance for current commutation. Investigating the use of 6/12-pulse configurations.**
- Identify simple power electronic converter schematics. Recognizing the different parts in a physical circuit on which basic wave-shape and efficiency measurements is performed.
- Loss calculation in passive and active components. Evaluating the temperature rise in the active components and choosing an appropriate heat-sink. Gaining a basic understanding of component life time.
- Utilizing the software Cadence PSpice to simulate basic power electronic circuits and the practical labs to have a firsthand experience of how real DC/DC converters operate.

Three-Phase Thyristor Rectifier

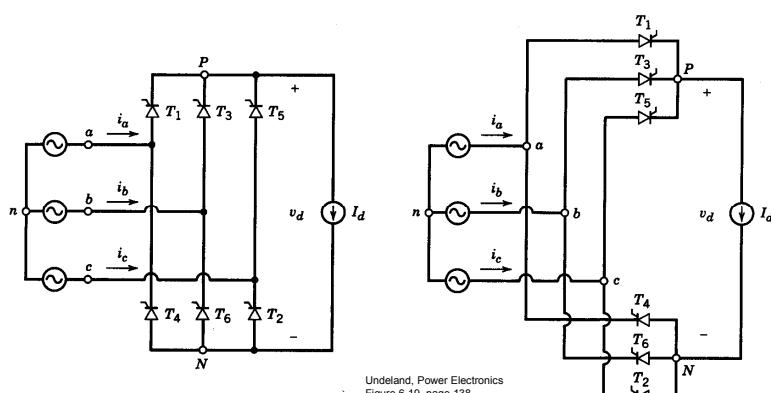- For most practical applications where higher powers are handled, a three-phase thyristor rectifier with constant DC-side current is used




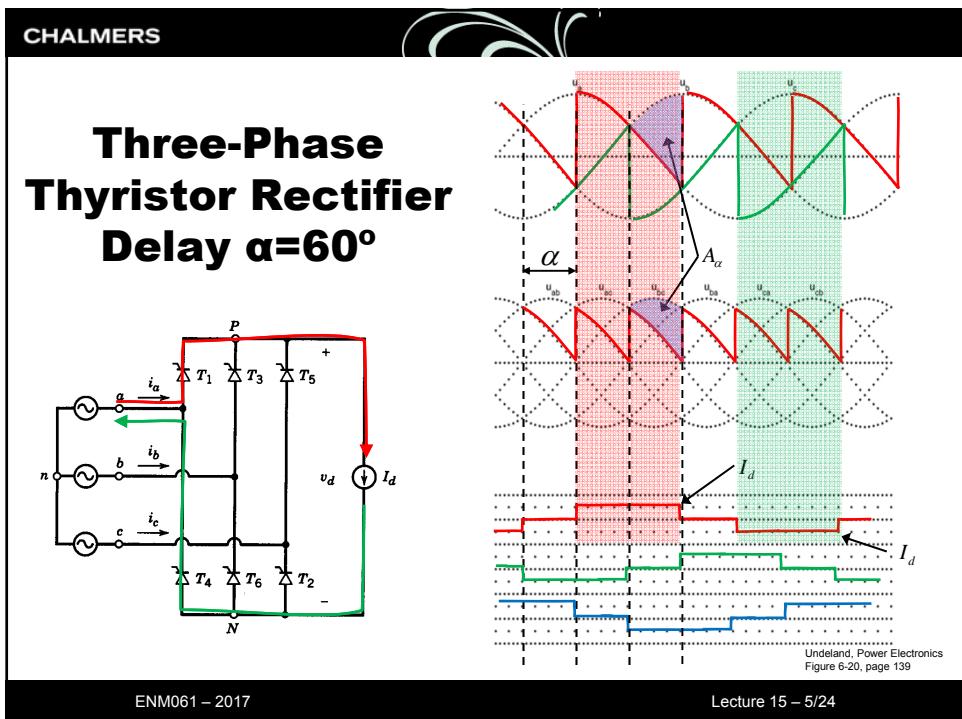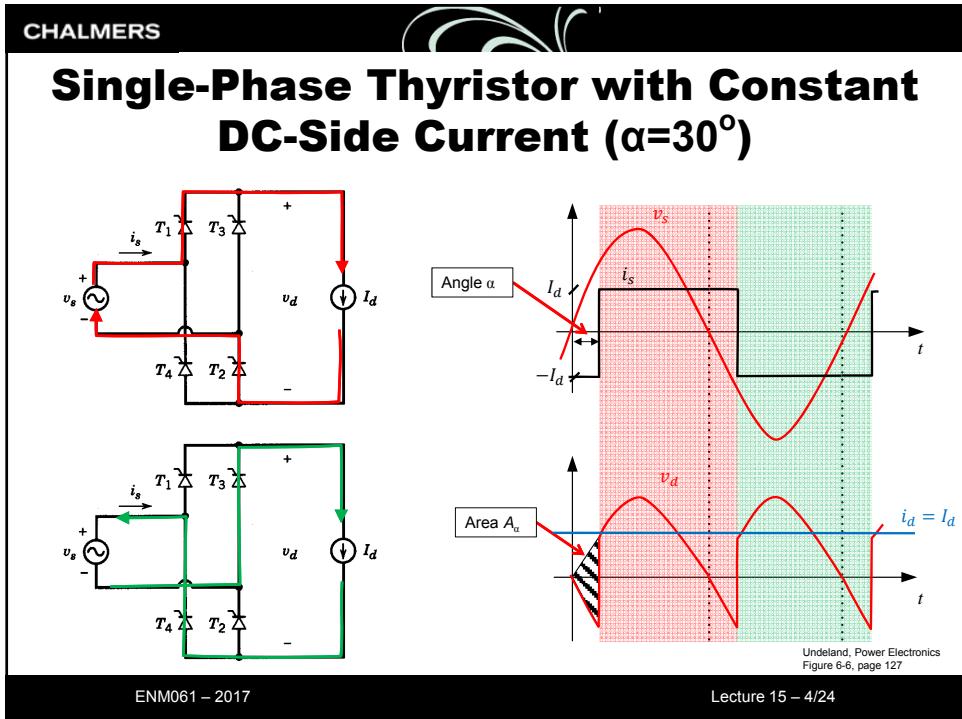



Three-Phase Thyristor Rectifier Delay $\alpha=60^\circ$

- Average DC-voltage
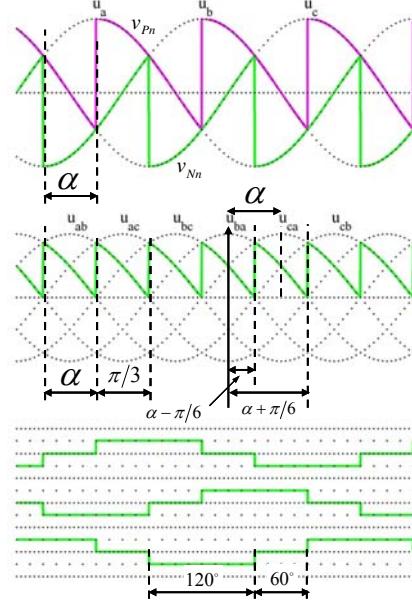
$$\begin{aligned}
 V_d &= \frac{1}{\pi/3} \int_{\alpha-\pi/6}^{\alpha+\pi/6} \sqrt{2}V_{LL} \cos(\gamma) d\gamma = \\
 &= \frac{3\sqrt{2}}{\pi} V_{LL} [\sin(\gamma)]_{\alpha-\pi/6}^{\alpha+\pi/6} = \\
 &= \frac{3\sqrt{2}}{\pi} V_{LL} \left(\sin\left(\alpha + \frac{\pi}{6}\right) - \sin\left(\alpha - \frac{\pi}{6}\right) \right) = \\
 &= \frac{3\sqrt{2}}{\pi} V_{LL} \cos(\alpha)
 \end{aligned}$$




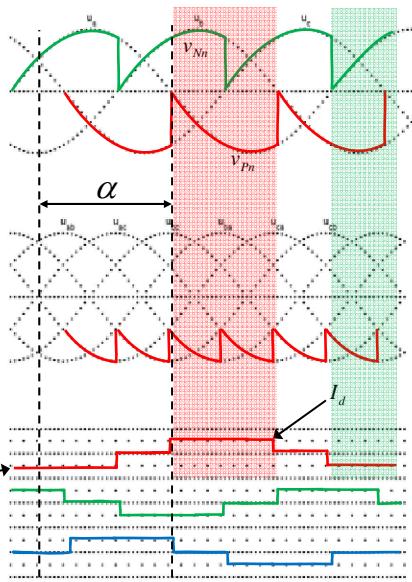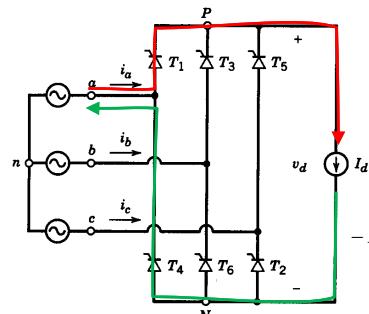Three-Phase Thyristor Rectifier Delay $\alpha=150^\circ$




Three-Phase Thyristor Rectifier Input Line Current Waveforms

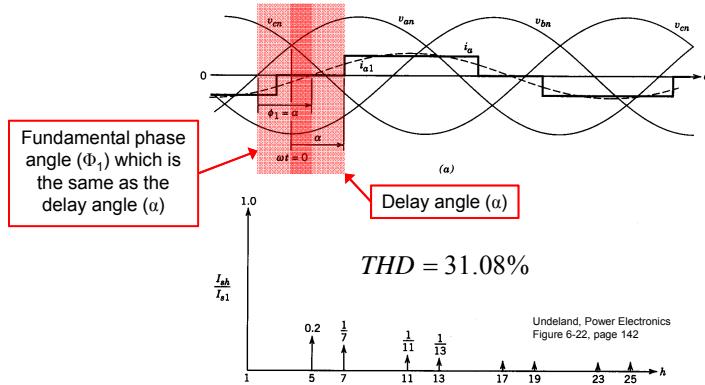- The current drawn from the source is quasi square-wave where the fundamental frequency is phase delayed with α



Three-Phase Thyristor Rectifier with AC-side Inductance

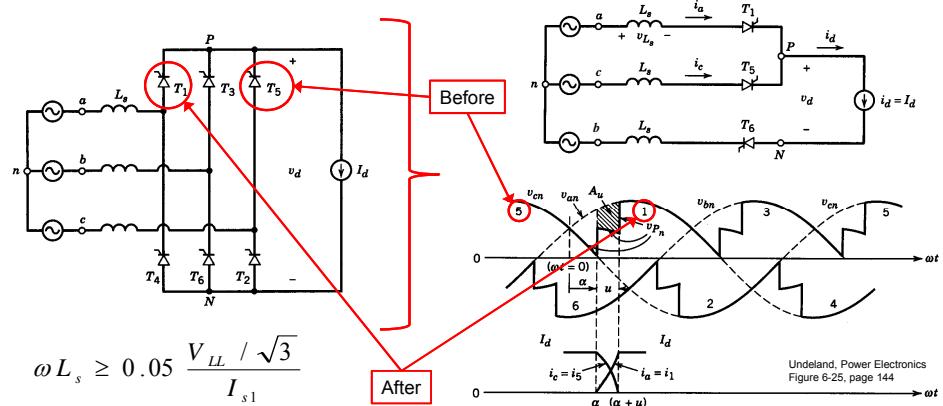- To study the current commutation, the circuit is redrawn so that the only commutation is included



Three-Phase Thyristor Rectifier with AC-side Inductance

Before commutation: $(\omega t < \alpha)$

$$i_c = I_d$$

$$i_b = -I_d$$

During commutation: $(\alpha \leq \omega t \leq \alpha + u)$

$$i_a = i_u$$


$$i_b = -I_d$$

$$i_c = I_d - i_u$$

After commutation: $(\omega t > \alpha + u)$

$$i_a = I_d$$

$$i_b = -I_d$$

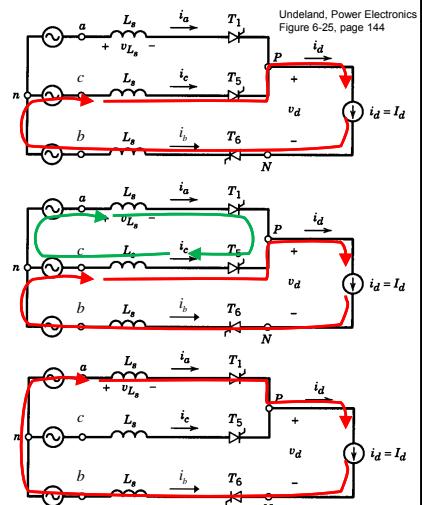

Three-Phase Thyristor Rectifier with AC-side Inductance


During commutation:

$$v_{pn} = v_c - v_{lc} = v_c - L_s \frac{d(I_d - i_u)}{dt} \Rightarrow$$

$$v_{pn} = v_c + L_s \frac{di_u}{dt}$$

$$v_{pn} = v_a - v_{la} = v_a - L_s \frac{di_u}{dt}$$

$$v_{pn} = \frac{v_c + v_a}{2}$$

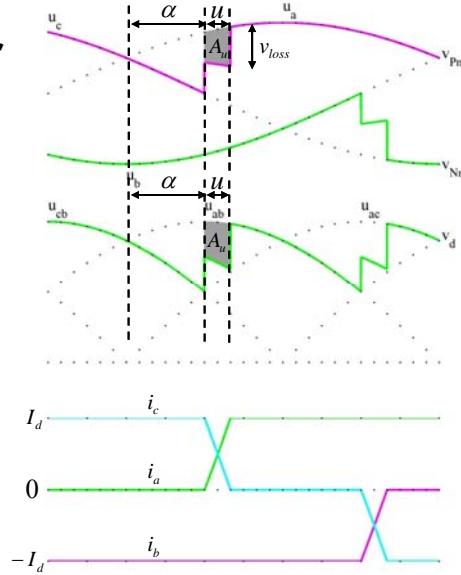

Three-Phase Thyristor Rectifier with AC-side Inductance

The commutation circuit gives:

$$v_{ac} = \sqrt{2}V_{LL} \sin(\gamma) = v_{La} - v_{Lc} = L_s \frac{di_u}{dt} - L_s \frac{d(I_d - i_u)}{dt} \Rightarrow$$

$$\sqrt{2}V_{LL} \sin(\gamma) = 2\omega L_s \frac{di_u}{d\gamma} \Rightarrow$$

$$\int_0^{I_d} 2\omega L_s di_u = 2\omega L_s I_d = \int_{\alpha}^{\alpha+u} \sqrt{2}V_{LL} \sin(\gamma) d\gamma = \sqrt{2}V_{LL} (\cos(\alpha) - \cos(\alpha+u)) \Rightarrow$$

$$\cos(\alpha+u) = \cos(\alpha) - \frac{2\omega L_s I_d}{\sqrt{2}V_{LL}}$$

Calculation of the average DC voltage:

$$v_{Pn} = v_a - v_{La} = v_a - v_{loss} \Rightarrow$$

Ideally: $v_{Pn} = v_a$

$$v_{loss} = v_{La} = L_s \frac{di_u}{dt} = \omega L_s \frac{di_u}{d\gamma} \Rightarrow$$

$$A_u = \int_{\alpha}^{\alpha+u} v_{loss} d\gamma = \int_0^{I_d} \omega L_s di_u = \omega L_s I_d$$

Ideal voltage-angle area without L_s

$$V_d = \frac{1}{\pi/3} \int_{\alpha-\pi/6}^{\alpha+\pi/6} v_d d\gamma = \frac{3}{\pi} \left(\int_{\alpha-\pi/6}^{\alpha+\pi/6} \sqrt{2}V_{LL} \cos(\gamma) d\gamma - A_u \right) =$$


$$= \frac{3\sqrt{2}}{\pi} V_{LL} \cos(\alpha) - \frac{3\omega L_s I_d}{\pi}$$

ENM061 – 2017

Lecture 15 – 12/24

Three-Phase Thyristor Rectifier with AC-side Inductance – Input Current

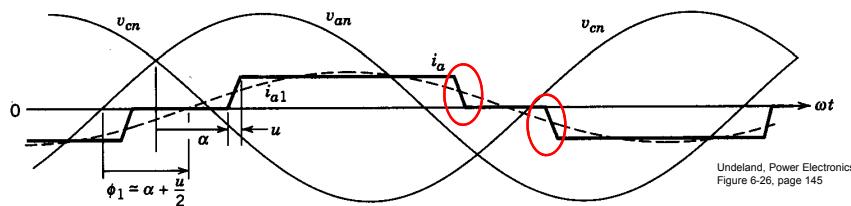- The current during the commutation has in the previous slides been idealized.



- The real current can be expressed as:


$$i_u(\theta) = \frac{1}{2\omega L_s} \int_{\alpha}^{\alpha+\theta} v_u d\theta \quad DPF = \cos(\alpha + u/2)$$

$$= \frac{1}{2\omega L_s} \int_{\alpha}^{\alpha+\theta} 2\sqrt{2}V_s \sin(\theta) d\theta = \frac{\sqrt{2}V_s}{\omega L_s} [-\cos(\theta)]_{\alpha}^{\theta} = \frac{\sqrt{2}V_s}{\omega L_s} (\cos(\alpha) - \cos(\alpha + \theta))$$

ENM061 – 2017

Lecture 15 – 13/24

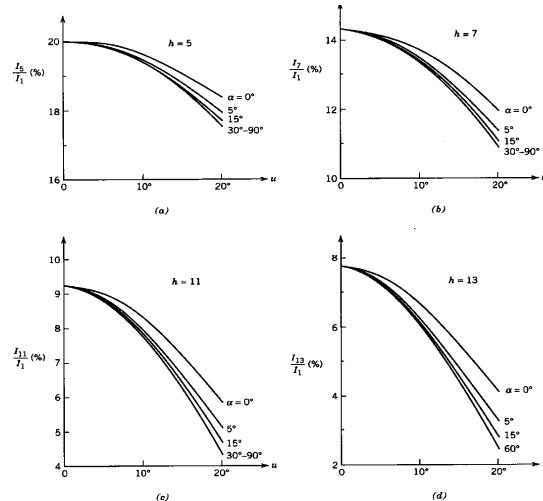Finite AC-side Inductance Input Current Harmonics




Undeland, Power Electronics
Figure 6-27, page 147

ENM061 – 2017

Lecture 15 – 14/24


Three-Phase Thyristor Rectifier Continuous DC-side Current

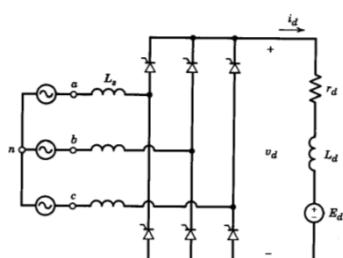- Practical application of a thyristor rectifier




Undeland, Power Electronics
Figure 6-28, page 148

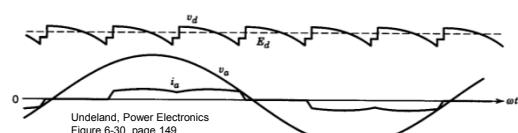- The current flowing on the DC-side can be continuous but not constant



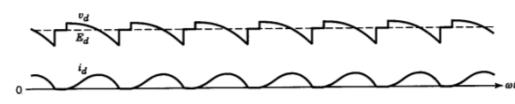- The DC-side current becomes discontinuous below a certain average value for a given delay angle.




Undeland, Power Electronics
Figure 6-29, page 148

ENM061 – 2017

Lecture 15 – 15/24

Three-Phase Thyristor Rectifier Inverter Mode

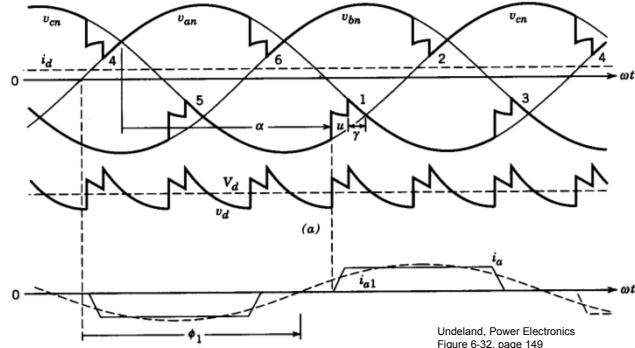
- For delay angles greater than 90° , the resulting output voltage (V_d) will become negative.



Undeland, Power Electronics

Figure 6-32, page 149

Thyristor inverter mode Importance of extinction angle γ

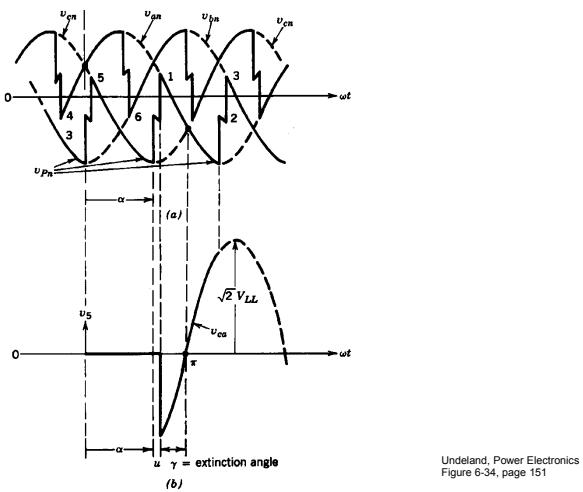Undeland, Power Electronics
Figure 6-34, page 151

Impact of thyristor loads PCC voltage Notching and harmonics

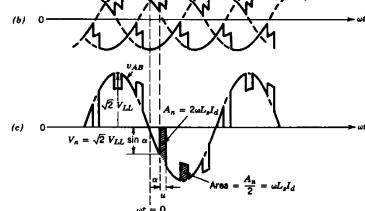
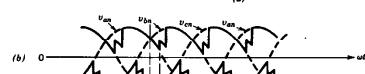
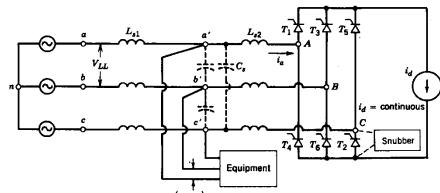


Figure 6-35 Line notching in other equipment voltage: (a) circuit, (b) phase voltages, (c) line-to-line voltage v_{AB} .

$$\text{Notch width } u = \frac{\text{Notch area } A_n}{\text{Notch depth } V_n}$$

Notch area and depth at PCC = $\rho A_n, \rho V_n$

$$\rho = \frac{L_{s1}}{L_{s1} + L_{s2}} \Rightarrow \omega L_s I_{s2} \geq 0.05 V_{LL} / \sqrt{3}$$

importance of the external inductance L_{s2}



Limits for 460 - V systems

Class	Line Notch Depth p(%)	Voltage Total	
		Line Notch Area (V·μs)	Harmonic Distortion (%)
Special applications	10	16,400	3
General system	20	22,800	5
Dedicated system	50	36,500	10

Undeland, Power Electronics
Figure 6-34/35/Table 6-2, page 151/152/153

Thyristor Applications – HVDC Converters and 12-Pulse Rectification

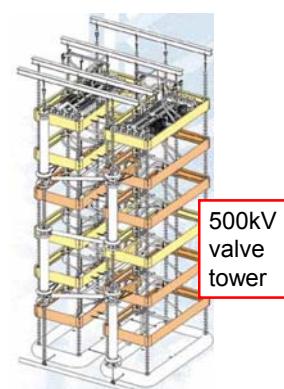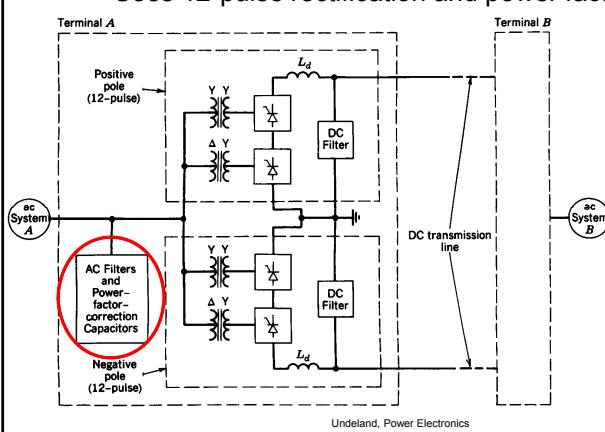
- Typical application of a thyristor rectifier is a HVDC Transmission
- Uses 12-pulse rectification and power factor correction capacitors



© Siemens

Thyristor Applications – HVDC Converters and 12-Pulse Rectification

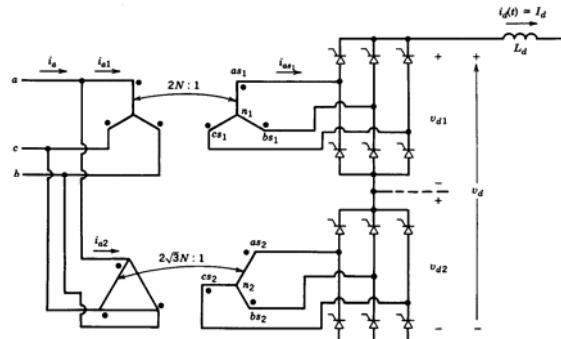
- A HVDC transmission is typically designed in a 12-pulse configuration



Undeland, Power Electronics
Figure 17-2, page 462


- To reduce line current THD
- To improve input power factor
- To avoid semiconductor devices in series.

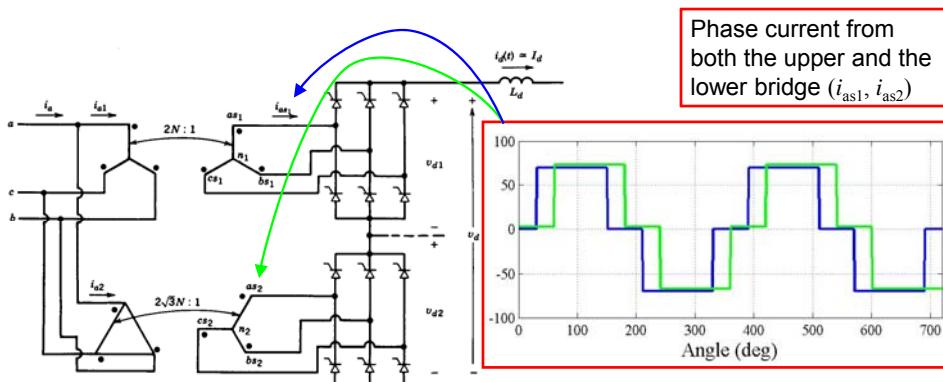Thyristor Applications – HVDC Converters and 12-Pulse Rectification




Phase current from
both the upper and the
lower bridge (i_{as1}, i_{as2})

Thyristor Applications – HVDC Converters and 12-Pulse Rectification

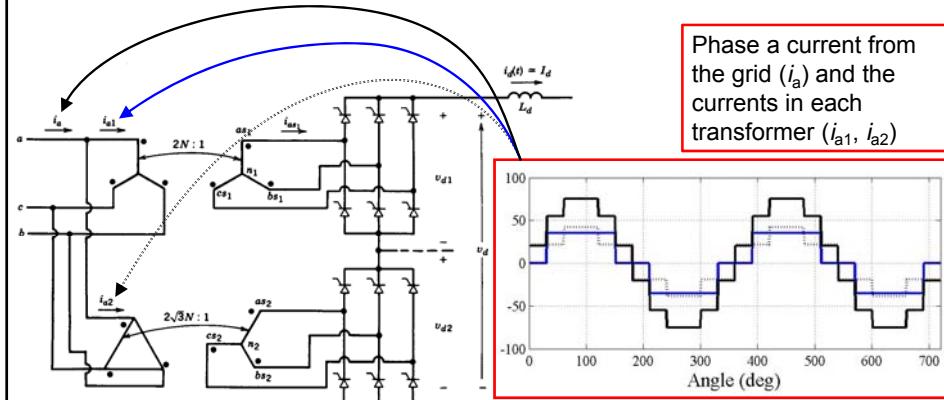

Tutorial 11

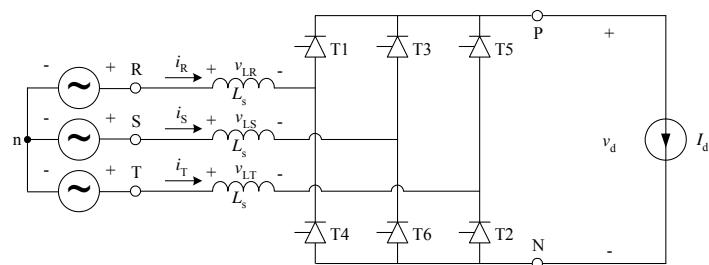

For $L_s = 25 \mu\text{H}$ and $V_{LL} = 460 \text{ V RMS}$ at 60 Hz

- Calculate the commutation angle u for $V_d = 525 \text{ V}$ and $P_d = 500 \text{ kW}$



Summary

- Three-phase thyristor rectifiers without source inductance
- Impact of source inductance on current commutation
- Thyristor converters in inverter mode of operation
- Impact of thyristor loads
- Applications of Thyristors
- Benefits of 12-pulse operation
- Learning outcome:
 - ❖ Operation of a three-phase thyristor rectifier operating with a current-stiff DC-side and the impact of line impedance for current commutation. Investigating the use of 6/12-pulse configurations.