

Demonstration 8

Equations used from previous lectures

Fourier analysis

$$g(\theta) = f(t), \theta = \omega t$$

$$g(\theta) = \frac{a_0}{2} + \sum_{n=1}^{\infty} [a_n \cos(n\theta) + b_n \sin(n\theta)]$$

$$a_n = \frac{1}{\pi} \int_{\theta_0}^{\theta_0+2\pi} g(\theta) \cos(n\theta) d\theta \quad n = 0, 1, 2, 3, \dots$$

$$b_n = \frac{1}{\pi} \int_{\theta_0}^{\theta_0+2\pi} g(\theta) \sin(n\theta) d\theta \quad n = 1, 2, 3, \dots$$

Table 3-1 Use of Symmetry in Fourier Analysis

Symmetry	Condition Required	a_h and b_h
Even	$f(-t) = f(t)$	$b_h = 0 \quad a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$
Odd	$f(-t) = -f(t)$	$a_h = 0 \quad b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$
Half-wave	$f(t) = -f(t + \frac{1}{2}T)$	$a_h = b_h = 0 \text{ for even } h$ $a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t) \text{ for odd } h$ $b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t) \text{ for odd } h$
Even quarter-wave	Even and half-wave	$b_h = 0 \text{ for all } h$ $a_h = \begin{cases} \frac{4}{\pi} \int_0^{\pi/2} f(t) \cos(h\omega t) d(\omega t) & \text{for odd } h \\ 0 & \text{for even } h \end{cases}$
Odd quarter-wave	Odd and half-wave	$a_h = 0 \text{ for all } h$ $b_h = \begin{cases} \frac{4}{\pi} \int_0^{\pi/2} f(t) \sin(h\omega t) d(\omega t) & \text{for odd } h \\ 0 & \text{for even } h \end{cases}$

Current ripple in a three-phase inverter when the load is a three-phase ac motor and the back-emf has the same amplitude and phase as the output fundamental voltage.

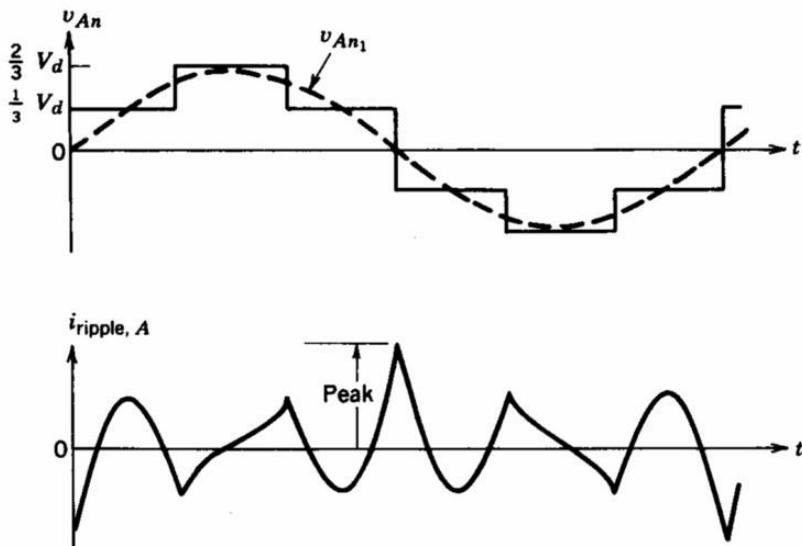



Fig.8.26a in Undeland book

Literature: Undeland book Chapter 8

Tutorial exercises

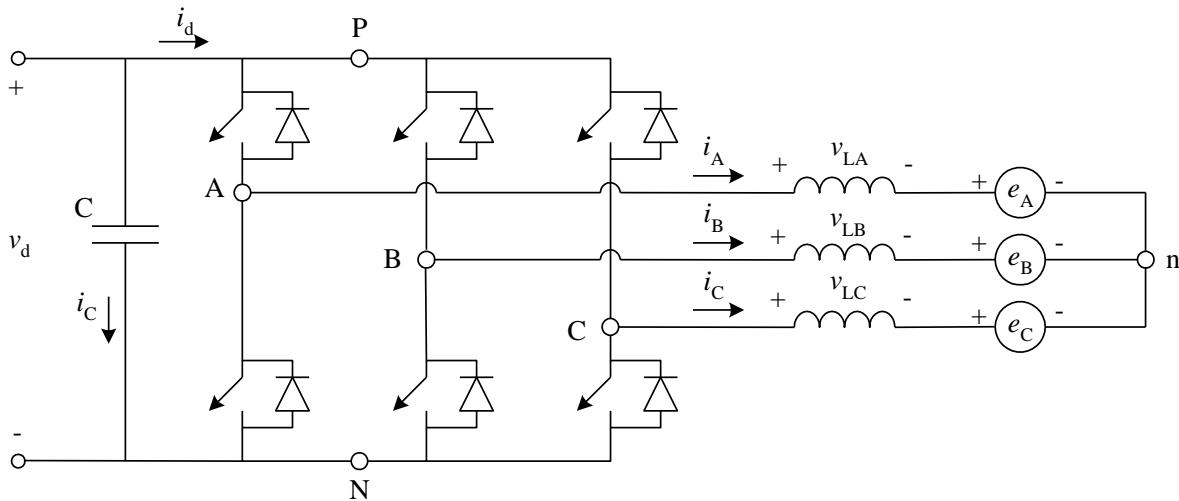Problem 1 (P8-7 in Undeland book)


Consider the problem of ripple in the output current of a three-phase square-wave inverter. $V_{LL(1)} = 200V$ at a frequency of 52Hz and the load is a three-phase ac motor with $L = 100mH$. Assume the back-emf has the same amplitude and phase as the output fundamental voltage.



Calculate the peak ripple current.

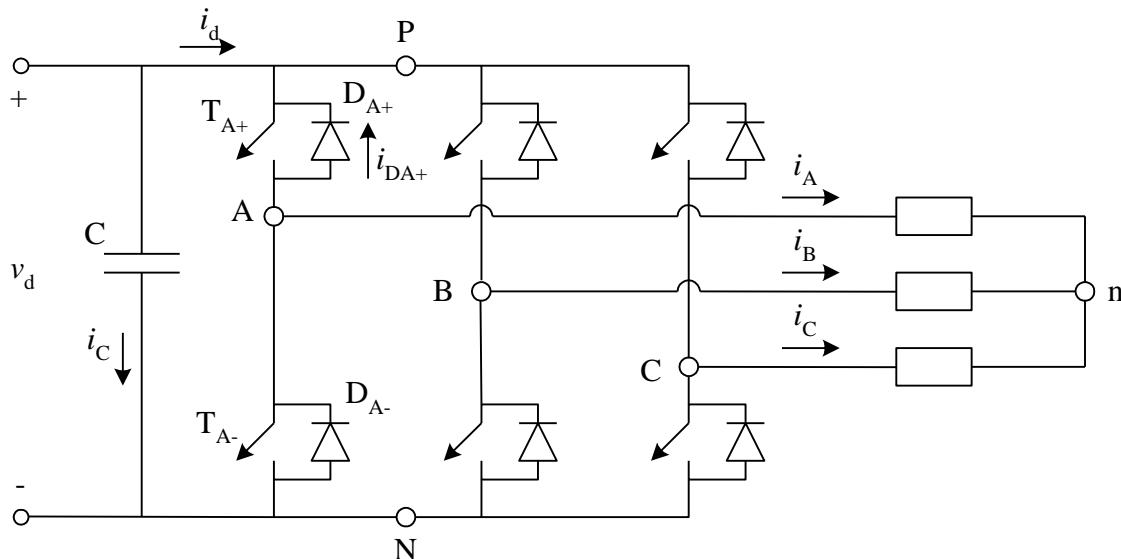Problem 2 (P8-10 in Undeland book)

In the three-phase, square-wave inverter (see Fig 8-24a in Undeland), consider the load to be balanced and purely resistive with a load-neutral point n .



Draw the steady state waveforms for v_{A_n} , i_A , $i_{D_{A+}}$ and i_d , where $i_{D_{A+}}$ is the current through diode D_{A+} .

Self-study exercises

From Undeland book:
P8-8, P8-11