




Demonstration 9

Tutorial exercises

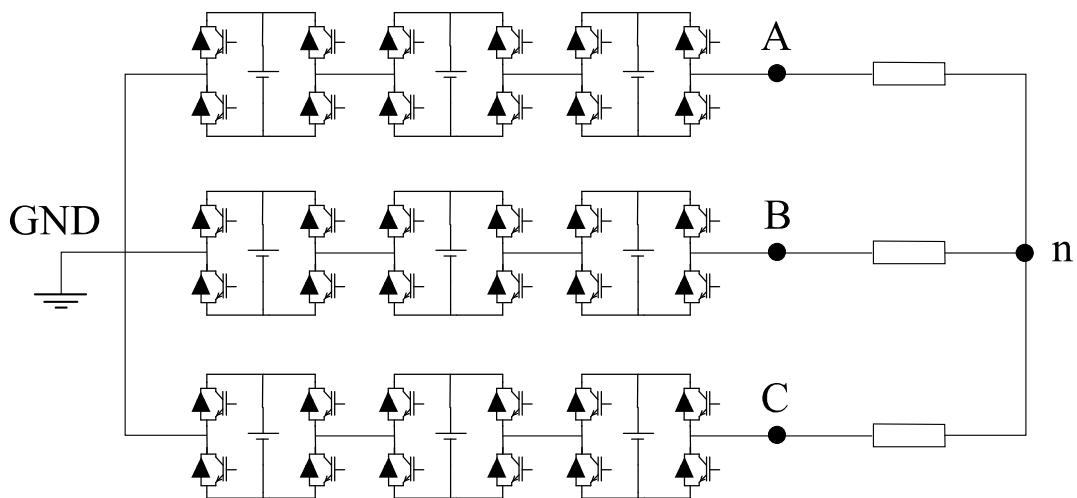Problem 1

Consider the cascaded three phase full bridge inverter with a purely resistive load below. Each H-bridge is connected to an ideal DC-source, V_d . The switching angle is 10° , 20° and 50° respectively.




a) Draw the waveform of voltages v_{AGND} , v_{AB} , v_{nGND} and v_{An} .

b) Calculate the THD of the phase voltage v_{An} .
Perform the same calculation for the phase voltage v_{An} in Problem 2 in Demonstration 8 (P8-9 in Undeland book).
Compare these two values.


c) Calculate the RMS value and average value of the DC-source currents in phase A.
Compare the RMS value and average value.
Perform the same calculation and comparison for the DC-source current in Problem 2 in demonstration 8 (P8-10 in Undeland book).




v_{AGND}


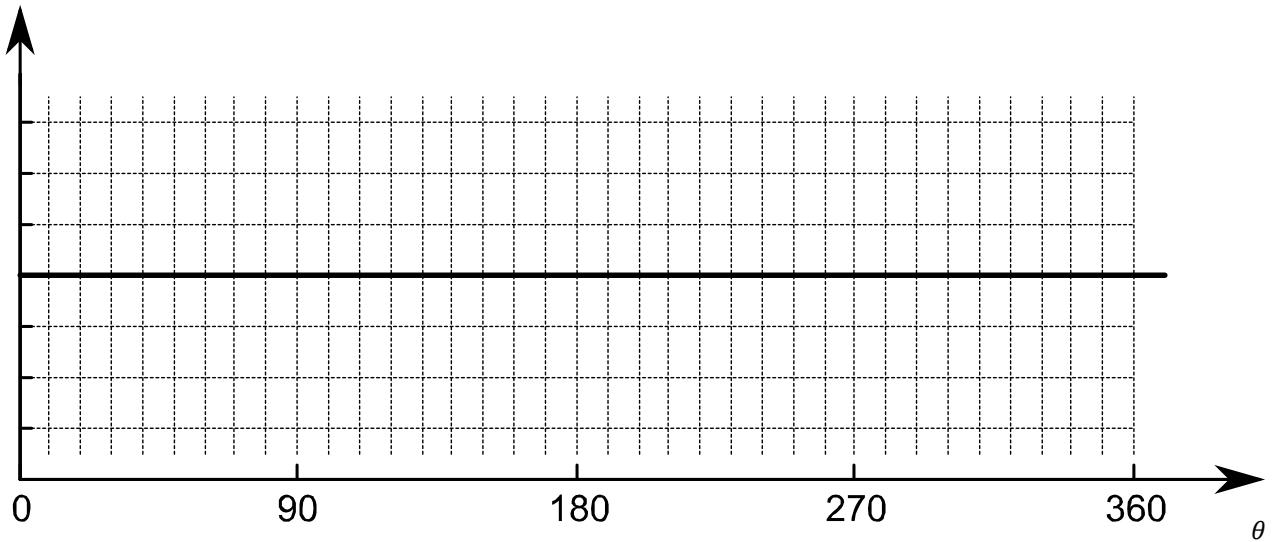


v_{AB}

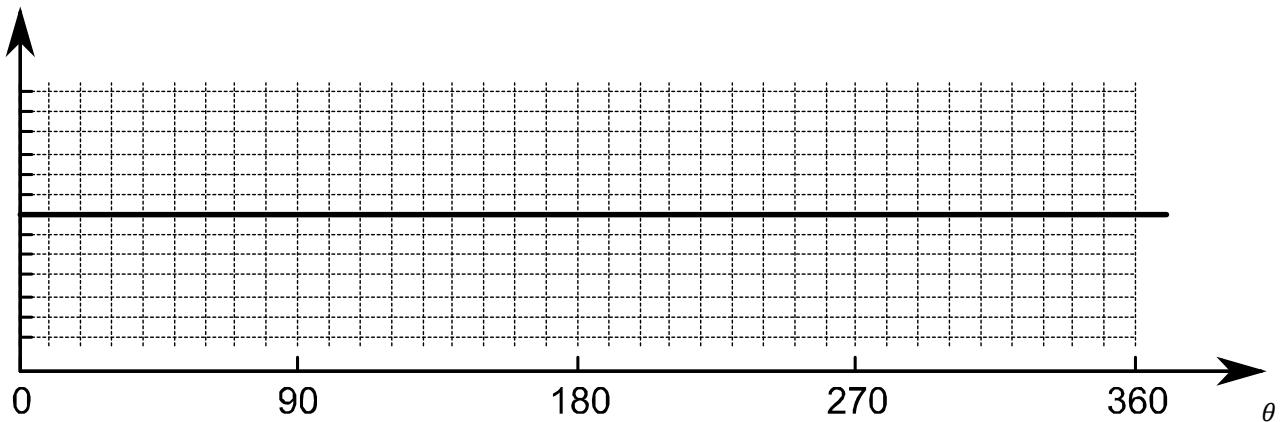

v_{nGND}

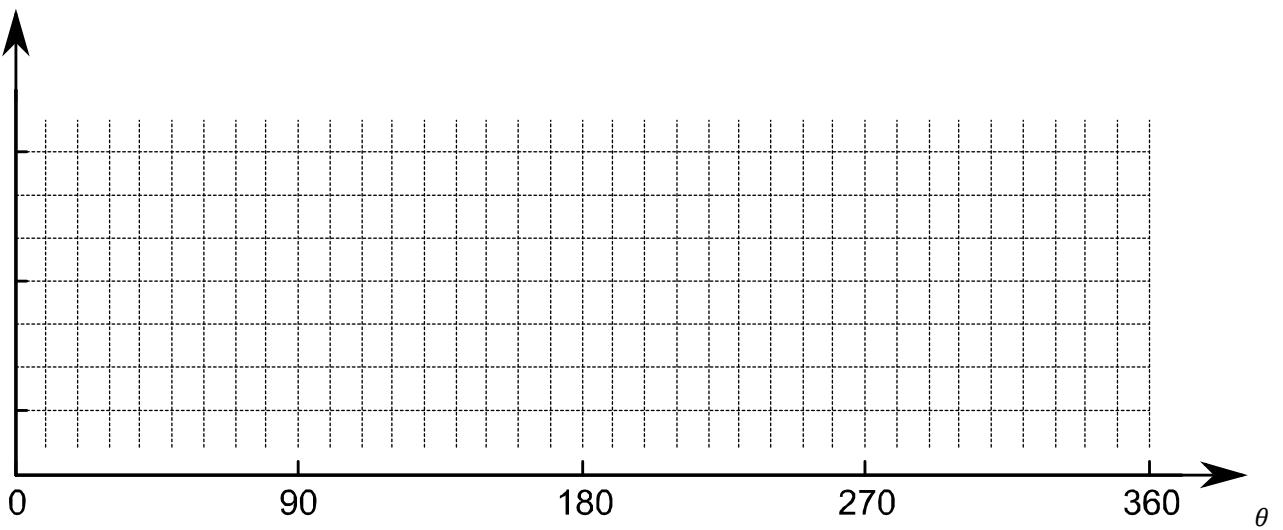

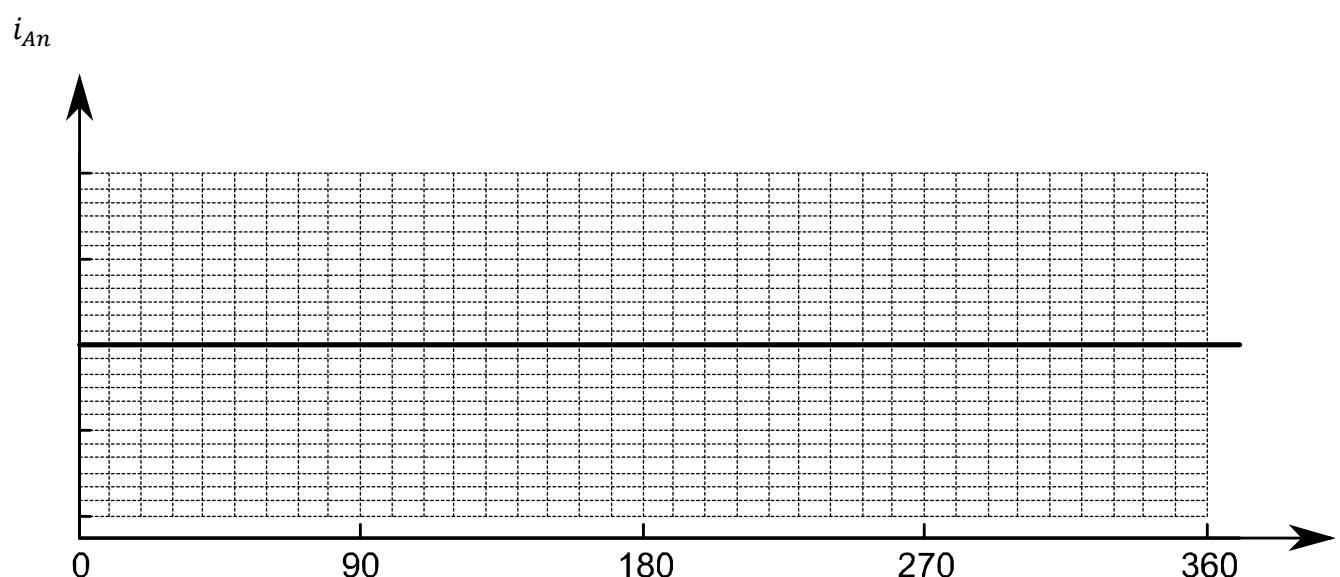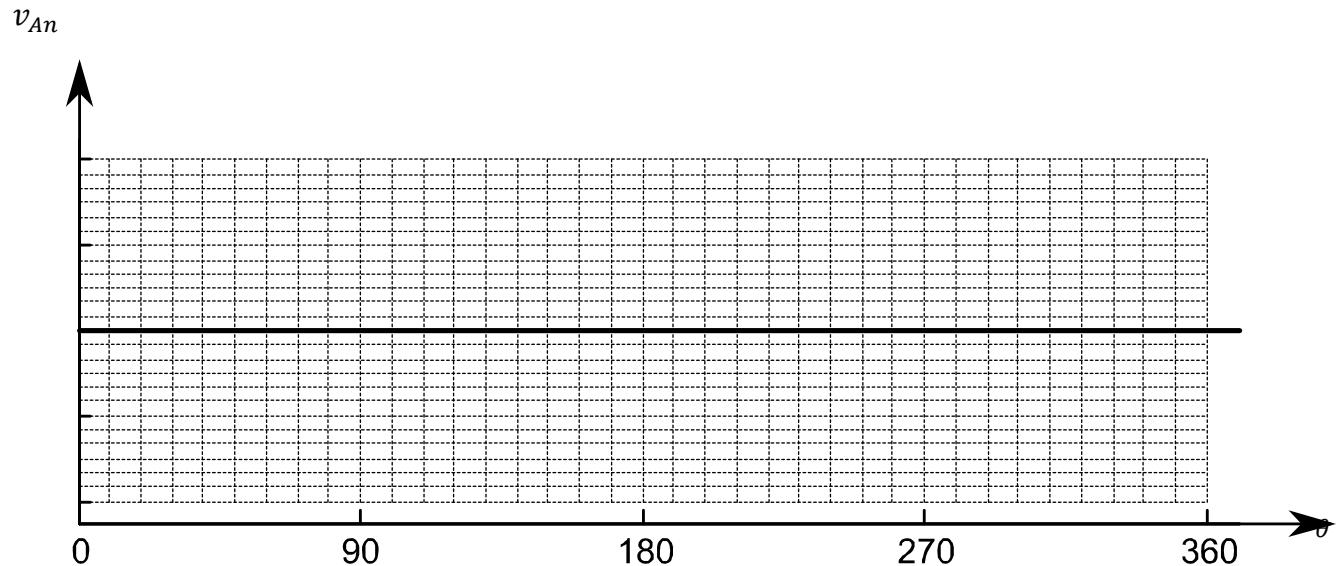



Equations used from previous lectures

Fourier analysis

$$g(\theta) = f(t), \theta = \omega t$$

$$g(\theta) = \frac{a_0}{2} + \sum_{n=1}^{\infty} [a_n \cos(n\theta) + b_n \sin(n\theta)]$$

$$a_n = \frac{1}{\pi} \int_{\theta_0}^{\theta_0+2\pi} g(\theta) \cos(n\theta) d\theta \quad n = 0, 1, 2, 3, \dots$$

$$b_n = \frac{1}{\pi} \int_{\theta_0}^{\theta_0+2\pi} g(\theta) \sin(n\theta) d\theta \quad n = 1, 2, 3, \dots$$

RMS value of a function

$$F_{rms} = \sqrt{\frac{1}{T} \int_0^T f(t)^2 dt}$$

Average value of a function

$$F_{avg} = \frac{1}{T} \int_0^T f(t) dt$$

Total harmonic distortion (THD)

$$\% THD = 100 \frac{\sqrt{F_{rms}^2 - F_{1,rms}^2}}{F_{1,rms}} = 100 \frac{F_{dis}}{F_{1,rms}}$$

Control of the cascaded full bridge inverter (Lecture slides 32)

- A typical modulation scheme is Selective Harmonic Elimination
- All switches operate with the fundamental frequency which gives low losses
- For each module, the switching angle (α) is controlled.

