

Dally, Harting and Aamodt: Digital Design Using VHDL


Kapitel 14

- 14.1 Vi har tillståndstabellen från *Tabell 14.2*, sida 308 som vi upprepar i *Figur 14.1a*.
Låt oss rita tillståndsgraf, *Figur 14.1b*.

State	Next state		out	
	in		in	
	0	1	0	1
00	00	01	0	0
01	00	11	0	0
11	01	10	0	0
10	11	00	0	1

Figur 14.1a

Vi söker en insignal som gör att vi alltid stegar tillbaka till starttillståndet 00 oberoende av nuvarande tillstånd. Vi ser att det inträffar om $in=0$.

 

Figur 14.1b


- 14.2 Vi har tillståndstabellen från *Tabell 14.4*, sida 311 som vi upprepar i *Figur 14.2a*.
Låt oss rita tillståndsgraf, *Figur 14.2b*.

State	Next state		Out
	carew		
	0	1	
GNS	GNS	YNS	100 001
YNS	GEW	GEW	010 001
GEW	YEW	YEW	001 100
YEW	GNS	GNS	001 010

Figur 14.2a

14.2 forts.


Vi söker en insignal som gör att vi alltid stegar tillbaka till starttillståndet GNS oberoende av nuvarande tillstånd. Vi ser att det inträffar om carew=0.

 

Figur 14.2b

14.3 Vi utgår från tillståndstabell och tillståndsgraf i Uppgift 14.2, dvs Figur 14.2a respektive Figur 14.2b. Våra utsignaler ligger enligt grön-gul-röd i nord-sydlig riktning följt av grön-gul-röd i öst-västlig riktning. Vi vill modifiera sekvensen så att det blir rött i båda riktningarna innan ett trafikljus går till grönt. Vi kan få det genom att lägga in tillstånd där båda riktningar har rött mellan YNS och GEW samt mellan YEW och GNS, Figur 14.3a.

Vi får tillståndstabellen i Figur 14.3b.

 

Figur 14.3a

State	Next state		Out
	carew		
	0	1	
GNS	GNS	YNS	100 001
YNS	RNSEW1	RNSEW1	010 001
RNSEW1	GEW	GEW	001 001
GEW	YEW	YEW	001 100
YEW	RNSEW2	RNSEW2	001 010
RNSEW2	GNS	GNS	001 001


Figur 14.3b

14.4 Vi får ersätta tillståndsnamnen i *Figur 14.3b* med tillståndsvariabler och utsignalen behöver delas upp i sina individuella bitar. Vi har sex tillstånd så vi behöver tre tillståndsvariabler. Vi tilldelar tillstånd slumpmässigt och får *Figur 14.4a*.


Vi ställer upp Karnaughdiagram för respektive signal. För tillstånden krävs diagram med fyra variabler medan utsignalerna kräver tre variabler. Då vi har ett förlopp uppifrån och ner i tabellen så är det förmodligen lämpligt att göra en tillståndstilldelning där vi rad för rad ändrar en tillståndsvariabel.

State	Next state		Out
	carew		
	0	1	
$x_2x_1x_0$	$y_2y_1y_0$	$y_2y_1y_0$	$z_5z_4z_3z_2z_1z_0$
000	000	001	100 001
001	011	011	010 001
011	111	111	001 001
111	110	110	001 100
110	100	100	001 010
100	000	000	001 001


Figur 14.4a

 


Figur 14.4b

 

Figur 14.4c

 

Figur 14.4d

 

Figur 14.4e

14.4 forts.

		x_1x_0			
		00	01	11	10
x_2	0	0	0	0	0
	1	0	0	0	1

$x_2x_1\bar{x}_0$ points to the cell (1, 10).

Figur 14.4f

		x_1x_0			
		00	01	11	10
x_2	0	0	0	0	0
	1	1	0	1	0

$x_2x_1x_0$ points to the cell (1, 11).

Figur 14.4g

		x_1x_0			
		00	01	11	10
x_2	0	0	0	1	0
	1	0	0	1	1

x_1x_0 points to the cell (0, 11).
 x_2x_1 points to the cell (1, 11).

Figur 14.4h

		x_1x_0			
		00	01	11	10
x_2	0	0	1	0	0
	1	0	0	0	0

$\bar{x}_2\bar{x}_1x_0$ points to the cell (0, 01).

Figur 14.4i


		x_1x_0			
		00	01	11	10
x_2	0	1	0	0	0
	1	0	0	0	0

$\bar{x}_2\bar{x}_1\bar{x}_0$ points to the cell (0, 00).

Figur 14.4j

14.4 forts.

Vi får kopplingen i *Figur 14.4k*

 

Figur 14.4k

14.5 Vi skriver VHDLK-kod för trafikljuset i *Exempel 14.3*

```
-- ex_14_5.vhdl
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY ex14_5 IS
    PORT(Clock:IN STD_LOGIC;
          Resetn:IN STD_LOGIC;
          carew:IN STD_LOGIC;
          z:OUT STD_LOGIC_VECTOR(5 DOWNTO 0));
END ex14_5;

ARCHITECTURE arch_ex14_5 OF ex14_5 IS
    TYPE state_type IS (GNS,YNS,RNSEW1,GEW,YEW,RNSEW2);
    SIGNAL state_signal:state_type;
    SIGNAL next_state_signal:state_type;
BEGIN
```

14.5 forts.

```
state_transition_proc:
  PROCESS(Resetn,Clock)
  BEGIN
    IF (Resetn='0') THEN
      state_signal<=GNS;
    ELSIF rising_edge(Clock) THEN
      state_signal<=next_state_signal;
    END IF;
  END PROCESS state_transition_proc;
```

```
stateflow_proc:
  PROCESS(state_signal,carew)
  BEGIN
    CASE state_signal IS
      WHEN GNS =>
        IF carew = '1' THEN
          next_state_signal <= YNS;
        ELSE
          next_state_signal <= GNS;
        END IF;
      WHEN YNS =>
        next_state_signal <= RNSEW1;
      WHEN RNSEW1 =>
        next_state_signal <= GEW;
      WHEN GEW =>
        next_state_signal <= YEW;
      WHEN YEW =>
        next_state_signal <= RNSEW2;
      WHEN RNSEW2 =>
        next_state_signal <= GNS;
    END CASE;
  END PROCESS stateflow_proc;
```

```
assignment_proc:
  PROCESS(state_signal,carew)
  BEGIN
    CASE state_signal IS
      WHEN GNS =>
        z <= "100001";
      WHEN YNS =>
        z <= "010001";
      WHEN RNSEW1 =>
        z <= "001001";
    END CASE;
  END PROCESS;
```


14.5 forts.

```
        WHEN GEW =>
            z <= "001100";
        WHEN YEW =>
            z <= "001010";
        WHEN RNSEW2 =>
            z <= "001001";
    END CASE;
END PROCESS assignment_proc;
END arch_ex14_5;
```

Och simulerar med en do-fil

```
-- ex_14_5.do
restart -f -nowave
view signals wave
add wave Clock Resetn carew state_signal
add wave next_state_signal z
force Clock 0 0, 1 50ns -repeat 100ns
force carew 0
force Resetn 0
run 225ns
force Resetn 1
force carew 1
run 100ns
force carew 0
run 600ns
force carew 1
run 100ns
force carew 0
run 600ns
```

14.6 Vi gör en liten modifiering av tillståndsgrafen i Uppgift 14.2, dvs *Figur 14.2a* respektive *Figur 14.6b* och får *Figur 14.6a*. Vad som inte framgår av uppgiften är vad som skall hända om det finns bilar i båda riktningarna men vi antar att carew har prioritet i tillstånd GNS medan carens har prioritet i GEW. Vi uppdaterar tillståndstabellen, *Figur 14.6b*

 

Figur 14.6a

14.6 forts.

State	Next state				Out
	carew/carsn				
	00	01	10	11	
GNS	GNS	GNS	YNS	YNS	100 001
YNS	GEW	GEW	GEW	GEW	010 001
GEW	GEW	YEW	GEW	YEW	001 100
YEW	GNS	GNS	GNS	GNS	001 010

Figur 14.6b

14.7 Vi gör samma typ av tillståndstilldelning som i Exempel 14.4 och låter bara en variabel ändra tillstånd i varje övergång, Figur 14.7a.

Vi ställer upp Karnaughdiagram, vi har fyra insignalerna och behöver fyra-variablers di-

State	Next state				Out
	carew/carsn				
	00	01	10	11	
x_1x_0	y_1y_0	y_1y_0	y_1y_0	y_1y_0	$z_5z_4z_3z_2z_1z_0$
00	00	00	01	01	100 001
01	11	11	11	11	010 001
11	11	10	11	10	001 100
10	00	00	00	00	001 010

Figur 14.7a

agram för tillstånden, Figur 14.7b-c, och två-variablers diagram för utsignalerna, Figur 14.7d-i.


x_1x_0	carew/carsn				
	00	01	11	10	
00	0	0	1	1	$\bar{x}_1 \text{carew}$
01	1	1	1	1	$\bar{x}_1x_0$
11	1	0	1	0	$x_0 \text{carew carsn}$
10	0	0	0	0	$x_0 \bar{\text{carew carsn}}$

Figur 14.7b


x_1x_0	carew/carsn				
	00	01	11	10	
00	0	0	1	0	$\bar{x}_1 \text{carew carsn}$
01	1	1	1	1	x_0
11	1	1	1	1	
10	0	0	0	0	

Figur 14.7c


14.7 forts.

 


Figur 14.7d

 


Figur 14.7e

 


Figur 14.7f

 

Figur 14.7g

 


Figur 14.7h

 

Figur 14.7i

Vi får kopplingen i Figur 14.7j

 

Figur 14.7j

14.8 Vi skriver VHDL-kod

```
-- ex_14_8.vhdl
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY ex_14_8 IS
    PORT(Clock:IN STD_LOGIC;
          Resetn:IN STD_LOGIC;
          carew:IN STD_LOGIC;
          carsn:IN STD_LOGIC;
          z:OUT STD_LOGIC_VECTOR(5 DOWNTO 0));
END ex_14_8;

ARCHITECTURE arch_ex14_8 OF ex_14_8 IS
    TYPE state_type IS (GNS,YNS,GEW,YEW);
    SIGNAL state_signal:state_type;
    SIGNAL next_state_signal:state_type;
    BEGIN
        state_transition_proc:
            PROCESS(Resetn,Clock)
            BEGIN
                IF (Resetn='0') THEN
                    state_signal<=GNS;
                ELSIF rising_edge(Clock) THEN
                    state_signal<=next_state_signal;
                END IF;
            END PROCESS state_transition_proc;

        stateflow_proc:
            PROCESS(state_signal,carew)
            BEGIN
                CASE state_signal IS
                    WHEN GNS =>
                        IF carew = '1' THEN
                            next_state_signal <= YNS;
                        ELSE
                            next_state_signal <= GNS;
                        END IF;
                    WHEN YNS =>
                        next_state_signal <= GEW;
                    WHEN GEW =>
                        IF carsn= '1' THEN
                            next_state_signal <= YEW;
```

14.8 forts.

```
        ELSE
            next_state_signal <= GEW;
        END IF;
    WHEN YEW =>
        next_state_signal <= GNS;
    END CASE;
END PROCESS stateflow_proc;

assignment_proc:
PROCESS(state_signal, carew)
BEGIN
    CASE state_signal IS
        WHEN GNS =>
            z <= "100001";
        WHEN YNS =>
            z <= "010001";
        WHEN GEW =>
            z <= "001100";
        WHEN YEW =>
            z <= "001010";
    END CASE;
END PROCESS assignment_proc;
END arch_ex14_8;
```

Vi simulerar med en do-fil


```
-- ex_14_8.do
restart -f -nowave
view signals wave
add wave Clock Resetn carew carsn
add wave state_signal next_state_signal z
force Clock 0 0, 1 50ns -repeat 100ns
force carew 0
force carsn 0
force Resetn 0
run 225ns
force Resetn 1
force carew 1
run 100ns
force carew 0
run 600ns
force carew 1
run 100ns
force carew 0
```

14.8 forts.

```
force carsn 1
run 600ns
force carsn 0
run 600ns
```

14.9 Vi gör en liten modifiering av tillståndsgrafen i Uppgift 14.2, dvs Figur 14.2a respektive Figur 14.6b och får Figur 14.9a.

Vi uppdaterar tillståndstabellen, Figur 14.9b

 

Figur 14.9a

State	Next state		Out
	carew		
	0	1	
GNS	GNS	YNS	100 001
YNS	GEW	GEW	010 001
GEW	YEW	GEW	001 100
YEW	GNS	GNS	001 010

Figur 14.9b

14.10 Vi gör samma typ av tillståndstilldelning som i Exempel 14.4 och låter bara en variabel ändra tillstånd i varje övergång, Figur 14.10a.

Vi ställer upp Karnaughdiagram, vi har fyra insignaler och behöver tre-variablers diagram för tillstånden, Figur 14.10b-c, och två variablers diagram för utsignalerna, Figur 14.7d-i. Utsignallogiken förändras inte från Exempel 14.7.

State	Next state		Out
	carew		
	0	1	
x_1x_0	y_1y_0	y_1y_0	$z_5z_4z_3z_2z_1z_0$
00	00	01	100 001
01	11	11	010 001
11	10	11	001 100
10	00	00	001 010

Figur 14.10a

14.10 forts.


	y_0	x_1x_0				
		00	01	11	10	$\bar{x}_1x_0$
0	carew	0	1	0	0	carew x_0
1		1	1	1	0	
						carew $\bar{x}_1$

Figur 14.10b

	y_1	x_1x_0				
		00	01	11	10	x_0
0	carew	0	1	1	0	
1		0	1	1	0	

Figur 14.10c

Vi får kopplingen i Figur 14.10d

 

Figur 14.10d

14.11 Vi skriver VHDL-kod

```
-- ex_14_11.vhdl
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY ex_14_11 IS
    PORT(Clock:IN STD_LOGIC;
         Reseth:IN STD_LOGIC;
         carew:IN STD_LOGIC;
         z:OUT STD_LOGIC_VECTOR(5 DOWNTO 0));
END ex_14_11;
```

14.11 forts.

```
ARCHITECTURE arch_ex_14_11 OF ex_14_11 IS
    TYPE state_type IS (GNS, YNS, GEW, YEW);
    SIGNAL state_signal:state_type;
    SIGNAL next_state_signal:state_type;
BEGIN
    state_transition_proc:
        PROCESS(Resetn,Clock)
        BEGIN
            IF (Resetn='0') THEN
                state_signal<=GNS;
            ELSIF rising_edge(Clock) THEN
                state_signal<=next_state_signal;
            END IF;
        END PROCESS state_transition_proc;

    stateflow_proc:
        PROCESS(state_signal, carew)
        BEGIN
            CASE state_signal IS
                WHEN GNS =>
                    IF carew = '1' THEN
                        next_state_signal <= YNS;
                    ELSE
                        next_state_signal <= GNS;
                    END IF;
                WHEN YNS =>
                    next_state_signal <= GEW;
                WHEN GEW =>
                    IF carew= '1' THEN
                        next_state_signal <= GEW;
                    ELSE
                        next_state_signal <= YEW;
                    END IF;
                WHEN YEW =>
                    next_state_signal <= GNS;
            END CASE;
        END PROCESS stateflow_proc;

    assignment_proc:
        PROCESS(state_signal, carew)
        BEGIN
            CASE state_signal IS
                WHEN GNS =>
                    z <= "100001";
```


14.11 forts.

```
        WHEN YNS =>
            z <= "010001";
        WHEN GEW =>
            z <= "001100";
        WHEN YEW =>
            z <= "001010";
    END CASE;
END PROCESS assignment_proc;
END arch_ex_14_11;
```

och simulerar med en do-fil

```
-- ex_14_11.do
restart -f -nowave
view signals wave
add wave Clock Resetn carew
add wave state_signal next_state_signal z
force Clock 0 0, 1 50ns -repeat 100ns
force carew 0
force Resetn 0
run 225ns
force Resetn 1
force carew 1
run 100ns
force carew 0
run 600ns
force carew 1
run 600ns
force carew 0
run 600ns
```


14.12 Vi utgår från tillståndsgra-
fen i *Figur 14.9*, sidan 312,
som vi upprepar i *Figur*
14.12a

 

Figur 14.12a

14.12 forts.

För att utöka räknecykeln till sex klockpulser så får vi lägga in et extra tillstånd i kedjan R – S3. Vi får också korrigera vägarna då en puls saknas eller är sen. Vi får *Figur 14.12b*

 


Figur 14.12b

Vi tecknar tillståndstabell, *Figur 14.12c*

State	a		z
	0	1	
R	R	S1	0
S1	S2	S2	1
S2	S3	S3	0
S3	S4	S4	0
S4	S5	S5	0
S5	S5	S1	0
S6	M	S1	0
M	S2	L	1
L	S2	S2	0

14.13 Vi har tillståndsgrafen i *Figur 14.9*, sidan 312, som vi upprepar i *Figur 14.13a*

14.13 forts.

 

Figur 14.13a

Vi tecknar tillståndstabell, Figur 14.13b

State	a		z
	0	1	
R	R	S1	0
S1	S2	S2	1
S2	S3	S3	0
S3	S4	S4	0
S4	S5	S1	0
S5	M	S1	0
M	S2	L	1
L	S2	S2	0

Figur 14.13b

14.14 Vi ska nu göra om tillståndstabellen i Figur 14.13b med, Figur 14.14a.

State	a		z
	0	1	
X ₂ X ₁ X ₀	Y ₂ Y ₁ Y ₀	Y ₂ Y ₁ Y ₀	
000	000	001	0
001	011	011	1
011	010	010	0
010	110	110	0
110	111	001	0
111	101	001	0
101	011	100	1
100	011	011	0

Figur 14.14a


Vi har tyvärr fyra diagonaler kvar där mer än en variabel byter värde. Vi kan nog inte eliminera det utan att dela upp tillstånd.

14.15 Vi ska nu använda en annan uppsättning tillståndsvariabler, *Figur 14.15a*.


Vi skall ta fram de logiska uttrycken och använder Karnaughdiagram. För tillstånden så har vi fyra variabler så vi behöver fyra-variablers Karnaughdiagram, *Figur 14.15b-d* medan vi behöver ett tre-variablers diagram för utsignalen, *Figur 14.15e*

State	<i>a</i>		<i>z</i>
	0	1	
$x_2x_1x_0$	$y_2y_1y_0$	$y_2y_1y_0$	
000	000	001	0
001	010	010	1
010	011	011	0
011	100	100	0
100	101	001	0
101	110	001	0
110	010	111	1
111	010	010	0


Figur 14.15a

 


Figur 14.15d

 

Figur 14.15d

 

Figur 14.15d

 

Figur 14.15d

$$y_0 = x_0 \cdot a + \bar{x}_2 \cdot x_1 \cdot \bar{x}_0 + x_2 \cdot \bar{x}_1 \cdot a + x_2 \cdot \bar{x}_1 \cdot \bar{x}_0$$

$$y_1 = \bar{x}_2 \cdot \bar{x}_1 \cdot x_0 + x_1 \cdot \bar{x}_0 + x_2 \cdot x_1 + x_2 \cdot x_0 \cdot \bar{a}$$

$$y_2 = \bar{x}_2 \cdot x_1 \cdot x_0 + x_2 \cdot x_1 \cdot \bar{x}_0 \cdot a + x_2 \cdot \bar{x}_1 \cdot \bar{a}$$

$$z = \bar{x}_2 \cdot \bar{x}_1 \cdot x_0 + x_2 \cdot x_1 \cdot \bar{x}_0$$

14.16 Vi ska nu göra en one-hot tillståndstilldelning av FSM:n från Exempel 14.12. Vi har åtta tillstånd så vi behöver åtta tillståndsvariabler samt en variabel för utsignalen. Vi får *Figur 14.16a*.

Vi kan inte söka en bra lösning på detta utan att använda optimeringsverktyg.

State	a		z
	0	1	
	X7X6X5X4X3X2X1X0	Y7Y6Y5Y4Y3Y2Y1Y0	
00000001	00000001	00000010	0
00000010	00000100	00000100	1
00000100	00001000	00001000	0
00001000	00010000	00010000	0
00010000	00100000	00000010	0
00100000	01000000	00000010	0
01000000	00000100	10000000	1
10000000	00000100	00000100	0

Figur 14.16a

14.17 Vi har tillståndstabellen för trafikljuset från *Tabell 14.4*, sida 311 som vi upprepar i *Figur 14.17a*.

Vi inför tillståndskodning, *Figur 14.17b*.

För tillstånden har vi tre variabler varför vi behöver tre-variablers Karnaughdiagram, *Figur 14.17c-d*, medan utsignalerna bestäms av bara två variabler så där behöver vi två-variablers Karnaughdiagram, *Figur 14.17e-j*.

State	Next state		Out
	carew		
	0	1	
GNS	GNS	YNS	100 001
YNS	GEW	GEW	010 001
GEW	YEW	YEW	001 100
YEW	GNS	GNS	001 010

Figur 14.17a

State	Next state		Out
	carew		
	0	1	
x_1x_0	y_1y_0	y_1y_0	$z_5z_4z_3z_2z_1y_0$
00	00	01	100 001
01	10	10	010 001
10	11	11	001 100
11	00	00	001 010

Figur 14.17a

	x_1x_0			
	00	01	11	10
y_0				
0	0	0	0	1
1	1	0	0	1

Figur 14.17c

	x_1x_0			
	00	01	11	10
y_0				
0	0	1	0	1
1	0	1	0	1

Figur 14.17d

14.17 forts.

	z_0	x_0
	0	1
x_1	0	1
1	0	0

Diagram showing a 2x2 Karnaugh map for z_0 and x_0 . The top row is labeled z_0 and the right column is labeled x_0 . The top-left cell (0,0) contains 1, and the top-right cell (0,1) contains 1. A blue circle highlights these two cells, with an arrow pointing to the label $\overline{x}_1$.

Figur 14.17e

	z_1	x_0
	0	1
x_1	0	0
1	0	1

Diagram showing a 2x2 Karnaugh map for z_1 and x_0 . The top row is labeled z_1 and the right column is labeled x_0 . The bottom-right cell (1,1) contains 1. A blue circle highlights this cell, with an arrow pointing to the label x_1x_0 .

Figur 14.17f

	z_2	x_0
	0	1
x_1	0	0
1	1	0

Diagram showing a 2x2 Karnaugh map for z_2 and x_0 . The top row is labeled z_2 and the right column is labeled x_0 . The bottom-left cell (1,0) contains 1. A blue circle highlights this cell, with an arrow pointing to the label $x_1\overline{x}_0$.

Figur 14.17g

	z_3	x_0
	0	1
x_1	0	0
1	1	1

Diagram showing a 2x2 Karnaugh map for z_3 and x_0 . The top row is labeled z_3 and the right column is labeled x_0 . The bottom-left cell (1,0) contains 1, and the bottom-right cell (1,1) contains 1. A blue circle highlights these two cells, with an arrow pointing to the label x_1 .

Figur 14.17h

	z_4	x_0
	0	1
x_1	0	0
1	0	0

Diagram showing a 2x2 Karnaugh map for z_4 and x_0 . The top row is labeled z_4 and the right column is labeled x_0 . The top-right cell (0,1) contains 1. A blue circle highlights this cell, with an arrow pointing to the label $\overline{x}_1x_0$.


Figur 14.17i

	z_5	x_0
	0	1
x_1	0	0
1	1	0

Diagram showing a 2x2 Karnaugh map for z_5 and x_0 . The top row is labeled z_5 and the right column is labeled x_0 . The top-left cell (0,0) contains 1. A blue circle highlights this cell, with an arrow pointing to the label $\overline{x}_1\overline{x}_0$.


Figur 14.17j

Vi får kopplingen i Figur 14.17k

 

Figur 14.17k

14.18 Om vi tar med alla eventualiteter, även att både a och b är höga så får vi
Figur 14.18a

 

Figur 14.18

och vi får tillståndstabellen i *Figur 4.18b*

State	Next state				UL
	ab				
	00	01	10	11	
S0	S0	S0	S1	S0	0
S1	S2	S0	S1	S0	0
S2	S2	S3	S0	S0	0
S3	S4	S3	S0	S0	0
S4	S4	S0	S5	S0	0
S5	S6	S0	S5	S0	0
S6	S6	S0	S7	S0	0
S7	S8	S0	S7	S0	1
S8	S8	S0	S0	S0	1

Figur 14.18b

14.19 Vi skriver VHDL-kod

```
-- ex_14_19.vhdl
LIBRARY ieee;
USE ieee.std_logic_1164.all;
```

14.19 forts.

```
ENTITY ex_14_19 IS
    PORT(Clock:IN STD_LOGIC;
          Resetn:IN STD_LOGIC;
          a:IN STD_LOGIC;
          b:IN STD_LOGIC;
          z:OUT STD_LOGIC);
END ex_14_19;

ARCHITECTURE arch_ex_14_19 OF ex_14_19 IS
    TYPE state_type IS (S0,S1,S2,S3,S4,S5,S6,S7,S8);
    SIGNAL state_signal:state_type;
    SIGNAL next_state_signal:state_type;
    SIGNAL ab:STD_LOGIC_VECTOR(1 DOWNTO 0);
    BEGIN
        ab <= a & b;

        state_transition_proc:
            PROCESS(Resetn,Clock)
            BEGIN
                IF (Resetn='0') THEN
                    state_signal<=S0;
                ELSIF rising_edge(Clock) THEN
                    state_signal<=next_state_signal;
                END IF;
            END PROCESS state_transition_proc;

        stateflow_proc:
            PROCESS(state_signal,a,b)
            BEGIN
                CASE state_signal IS
                    WHEN S0 =>
                        IF ab = "00" THEN
                            next_state_signal <= S0;
                        ELSIF ab = "01" THEN
                            next_state_signal <= S0;
                        ELSIF ab = "10" THEN
                            next_state_signal <= S1;
                        ELSE
                            next_state_signal <= S0;
                        END IF;
                    WHEN S1 =>
                        IF ab = "00" THEN
                            next_state_signal <= S2;
```

14.19 forts.

```
ELSIF ab = "01" THEN
    next_state_signal <= S0;
ELSIF ab = "10" THEN
    next_state_signal <= S1;
ELSE
    next_state_signal <= S0;
END IF;
WHEN S2 =>
IF ab = "00" THEN
    next_state_signal <= S2;
ELSIF ab = "01" THEN
    next_state_signal <= S3;
ELSIF ab = "10" THEN
    next_state_signal <= S0;
ELSE
    next_state_signal <= S0;
END IF;
WHEN S3 =>
IF ab = "00" THEN
    next_state_signal <= S4;
ELSIF ab = "01" THEN
    next_state_signal <= S3;
ELSIF ab = "10" THEN
    next_state_signal <= S0;
ELSE
    next_state_signal <= S0;
END IF;
WHEN S4 =>
IF ab = "00" THEN
    next_state_signal <= S4;
ELSIF ab = "01" THEN
    next_state_signal <= S0;
ELSIF ab = "10" THEN
    next_state_signal <= S5;
ELSE
    next_state_signal <= S0;
END IF;
WHEN S5 =>
IF ab = "00" THEN
    next_state_signal <= S6;
ELSIF ab = "01" THEN
    next_state_signal <= S0;
ELSIF ab = "10" THEN
    next_state_signal <= S5;
```

14.19 forts.

```
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S6 =>
        IF ab = "00" THEN
            next_state_signal <= S6;
        ELSIF ab = "01" THEN
            next_state_signal <= S0;
        ELSIF ab = "10" THEN
            next_state_signal <= S7;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S7 =>
        IF ab = "00" THEN
            next_state_signal <= S8;
        ELSIF ab = "01" THEN
            next_state_signal <= S0;
        ELSIF ab = "10" THEN
            next_state_signal <= S7;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S8 =>
        IF ab = "00" THEN
            next_state_signal <= S8;
        ELSIF ab = "01" THEN
            next_state_signal <= S0;
        ELSIF ab = "10" THEN
            next_state_signal <= S0;
        ELSE
            next_state_signal <= S0;
        END IF;
    END CASE;
END PROCESS stateflow_proc;

assignment_proc:
PROCESS(state_signal,a,b)
BEGIN
    CASE state_signal IS
        WHEN S7 =>
            z <= '1';
        WHEN S8 =>
            z <= '1';
    END CASE;
END assignment_proc;
```

14.19 forts.

```
        WHEN OTHERS =>
            z <= '0';
        END CASE;
    END PROCESS assignment_proc;
END arch_ex_14_19;
```


och simulerar med en do-fil

```
-- ex_14_19.do
restart -f -nowave
view signals wave
add wave Clock Resetn a b
add wave state_signal next_state_signal z
force Clock 0 0, 1 50ns -repeat 100ns
force a 0
force b 0
force Resetn 0
run 225ns
force Resetn 1
force a 1
run 100ns
force a 0
run 100ns
force b 1
run 100ns
force b 0
run 100ns
force a 1
run 100ns
force a 0
run 100ns
force a 1
run 100ns
force a 0
run 100ns
force b 1
run 100ns
force b 0
run 100ns
force a 1
run 100ns
force a 0
run 100ns
force b 1
```

14.19 forts.

run 100ns
force a 1
run 200ns

14.20 Vi ritar en tillståndsgraf, *Figur 14.20a*

 

Figur 14.20a

14.20 forts.

och ställer upp tillståndstabell, *Figur 4.20b*. Vi utelämnar alternativet att båda insignalerna skulle varahöga då inte kan inträffa. I VHDL-koden låter vi i det fallet FSM:n gå tillbaka till starttillståndet.

State	Next state				thing	change
	Nickel/dime					
	00	01	10	11		
S0	S0	S3	S1	-	0	0
S1	S2	S0	S1	-	0	0
S2	S2	S5	S3	-	0	0
S3	S4	S3	S3	-	0	0
S4	S4	S7	S5	-	0	0
S5	S6	S5	S5	-	0	0
S6	S6	S9	S7	-	0	0
S7	S8	S7	S7	-	0	0
S8	S8	S11	S9	-	0	0
S9	S10	S9	S9	-	0	0
S10	S10	S13	S11	-	0	0
S11	S12	S11	S11	-	0	0
S12	S12	S15	S13	-	0	0
S13	S14	S13	S13	-	0	0
S14	S14	S16	S15	-	0	0
S15	S0	S15	S15	-	1	0
S16	S0	S16	S0		0	1

Figur 14.20b

14.21 17 tillstånd så vi behöver 5 tillståndsvariabler

State	Next state				thing	change
	Nickel/dime					
	00	01	10	11		
00000	00000	00011	00001	-	0	0
00001	00010	00000	00001	-	0	0
00010	00010	00101	00011	-	0	0
00011	00100	00011	00011	-	0	0
00100	00100	00111	00101	-	0	0
00101	00110	00101	00101	-	0	0
00110	00110	01001	00111	-	0	0
00111	01000	00111	00111	-	0	0
01000	01000	01011	01001	-	0	0
01001	01010	01001	01001	-	0	0
01010	01010	01101	01011	-	0	0
01011	01100	01011	01011	-	0	0
01100	01100	01111	01101	-	0	0
01101	01110	01101	01101	-	0	0
01110	01110	10000	01111	-	0	0
01111	00000	01111	01111	-	1	0
10000	00000	10000	00000		0	1

Figur 14.20a

Lösningen blir rätt komplicerad med många variabler så vi utelämnar den här

14.22 Vi får VHDL-koden

```
-- ex_14_22.vhdl
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.numeric_std.all;

ENTITY ex_14_22 IS
    PORT(Clock:IN STD_LOGIC;
         Resetn:IN STD_LOGIC;
         nickel:IN STD_LOGIC;
         dime:IN STD_LOGIC;
         z:OUT STD_LOGIC;
         change:OUT STD_LOGIC);
END ex_14_22;
```

14.22 forts.

```
ARCHITECTURE arch_ex_14_22 OF ex_14_22 IS
  TYPE state_type IS
    (S0, S1, S2, S3, S4, S5, S6, S7, S8, S9,
     S10, S11, S12, S13, S14, S15, S16);
  SIGNAL state_signal:state_type;
  SIGNAL next_state_signal:state_type;
  SIGNAL nickel_dime_signal:STD_LOGIC_VECTOR(1
    DOWNT0 0);
  SIGNAL value:NATURAL RANGE 0 TO 45:=0;
  BEGIN
    nickel_dime_signal <= nickel & dime;

state_transition_proc:
  PROCESS(Resetn,Clock)
  BEGIN
    IF (Resetn='0') THEN
      state_signal<=S0;
    ELSIF rising_edge(Clock) THEN
      state_signal<=next_state_signal;
    END IF;
  END PROCESS state_transition_proc;

stateflow_proc:
  PROCESS(state_signal,nickel,dime)
  BEGIN
    CASE state_signal IS
      WHEN S0 =>
        value <= 0;
        IF nickel_dime_signal = "00" THEN
          next_state_signal <= S0;
        ELSIF nickel_dime_signal = "01" THEN
          next_state_signal <= S3;
        ELSIF nickel_dime_signal = "10" THEN
          next_state_signal <= S1;
        ELSE
          next_state_signal <= S0;
        END IF;
      WHEN S1 =>
        value <= 5;
        IF nickel_dime_signal = "00" THEN
          next_state_signal <= S2;
        ELSIF nickel_dime_signal = "01" THEN
          next_state_signal <= S0;
```

14.22 forts.

```
        ELSIF nickel_dime_signal = "10" THEN
            next_state_signal <= S1;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S2 =>
        value <= 5;
        IF nickel_dime_signal = "00" THEN
            next_state_signal <= S2;
        ELSIF nickel_dime_signal = "01" THEN
            next_state_signal <= S5;
        ELSIF nickel_dime_signal = "10" THEN
            next_state_signal <= S3;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S3 =>
        value <= 10;
        IF nickel_dime_signal = "00" THEN
            next_state_signal <= S4;
        ELSIF nickel_dime_signal = "01" THEN
            next_state_signal <= S3;
        ELSIF nickel_dime_signal = "10" THEN
            next_state_signal <= S3;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S4 =>
        value <= 10;
        IF nickel_dime_signal = "00" THEN
            next_state_signal <= S4;
        ELSIF nickel_dime_signal = "01" THEN
            next_state_signal <= S7;
        ELSIF nickel_dime_signal = "10" THEN
            next_state_signal <= S5;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S5 =>
        value <= 15;
        IF nickel_dime_signal = "00" THEN
            next_state_signal <= S6;
        ELSIF nickel_dime_signal = "01" THEN
            next_state_signal <= S5;
```

14.22 forts.

```
        ELSIF nickel_dime_signal = "10" THEN
            next_state_signal <= S5;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S6 =>
        value <= 15;
        IF nickel_dime_signal = "00" THEN
            next_state_signal <= S6;
        ELSIF nickel_dime_signal = "01" THEN
            next_state_signal <= S9;
        ELSIF nickel_dime_signal = "10" THEN
            next_state_signal <= S7;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S7 =>
        value <= 20;
        IF nickel_dime_signal = "00" THEN
            next_state_signal <= S8;
        ELSIF nickel_dime_signal = "01" THEN
            next_state_signal <= S7;
        ELSIF nickel_dime_signal = "10" THEN
            next_state_signal <= S7;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S8 =>
        value <= 20;
        IF nickel_dime_signal = "00" THEN
            next_state_signal <= S8;
        ELSIF nickel_dime_signal = "01" THEN
            next_state_signal <= S11;
        ELSIF nickel_dime_signal = "10" THEN
            next_state_signal <= S9;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S9 =>
        value <= 25;
        IF nickel_dime_signal = "00" THEN
            next_state_signal <= S10;
        ELSIF nickel_dime_signal = "01" THEN
            next_state_signal <= S9;
```

14.22 forts.

```
ELSIF nickel_dime_signal = "10" THEN
    next_state_signal <= S9;
ELSE
    next_state_signal <= S0;
END IF;
WHEN S10 =>
    value <= 25;
    IF nickel_dime_signal = "00" THEN
        next_state_signal <= S10;
    ELSIF nickel_dime_signal = "01" THEN
        next_state_signal <= S13;
    ELSIF nickel_dime_signal = "10" THEN
        next_state_signal <= S11;
    ELSE
        next_state_signal <= S0;
    END IF;
WHEN S11 =>
    value <= 30;
    IF nickel_dime_signal = "00" THEN
        next_state_signal <= S12;
    ELSIF nickel_dime_signal = "01" THEN
        next_state_signal <= S11;
    ELSIF nickel_dime_signal = "10" THEN
        next_state_signal <= S11;
    ELSE
        next_state_signal <= S0;
    END IF;
WHEN S12 =>
    value <= 30;
    IF nickel_dime_signal = "00" THEN
        next_state_signal <= S12;
    ELSIF nickel_dime_signal = "01" THEN
        next_state_signal <= S15;
    ELSIF nickel_dime_signal = "10" THEN
        next_state_signal <= S13;
    ELSE
        next_state_signal <= S0;
    END IF;
WHEN S13 =>
    value <= 35;
    IF nickel_dime_signal = "00" THEN
        next_state_signal <= S14;
    ELSIF nickel_dime_signal = "01" THEN
        next_state_signal <= S13;
```

14.22 forts.

```
        ELSIF nickel_dime_signal = "10" THEN
            next_state_signal <= S13;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S14 =>
        value <= 35;
        IF nickel_dime_signal = "00" THEN
            next_state_signal <= S14;
        ELSIF nickel_dime_signal = "01" THEN
            next_state_signal <= S16;
        ELSIF nickel_dime_signal = "10" THEN
            next_state_signal <= S15;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S15 =>
        value <= 40;
        IF nickel_dime_signal = "00" THEN
            next_state_signal <= S0;
        ELSIF nickel_dime_signal = "01" THEN
            next_state_signal <= S15;
        ELSIF nickel_dime_signal = "10" THEN
            next_state_signal <= S15;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S16 =>
        value <= 45;
        IF nickel_dime_signal = "00" THEN
            next_state_signal <= S0;
        ELSIF nickel_dime_signal = "01" THEN
            next_state_signal <= S16;
        ELSIF nickel_dime_signal = "10" THEN
            next_state_signal <= S0;
        ELSE
            next_state_signal <= S0;
        END IF;
    END CASE;
END PROCESS stateflow_proc;
```

14.22 forts.

```
assignment_proc:
PROCESS(state_signal,nickel,dime)
BEGIN
    CASE state_signal IS
        WHEN S15 =>
            z <= '1';
            change <= '0';
        WHEN S16 =>
            z <= '1';
            change <= '1';
        WHEN OTHERS =>
            z <= '0';
            change <= '0';
    END CASE;

    END PROCESS assignment_proc;
END arch_ex_14_22;
```


Som vi simulerar med en do-fil

```
-- ex_14_20.do
restart -f -nowave
view signals wave
add wave Clock Resetn nickel dime
add wave state_signal next_state_signal z change
add wave -radix unsigned value
force Clock 0 0, 1 50ns -repeat 100ns
force nickel 0
force dime 0
force Resetn 0
run 225ns
force Resetn 1
#1 dime = 10
force dime 1
run 100ns
force dime 0
run 100ns
#1+1 dime = 20
force dime 1
run 100ns
force dime 0
run 100ns
```

14.22 forts.

```
#1+1+1 dime = 30
force dime 1
run 100ns
force dime 0
run 100ns
#1+1+1+1 dime = 40
force dime 1
run 100ns
force dime 0
run 100ns
#10
force dime 1
run 100ns
force dime 0
run 100ns
#15
force nickel 1
run 100ns
force nickel 0
run 100ns
#25
force dime 1
run 100ns
force dime 0
run 100ns
#35
force dime 1
run 100ns
force dime 0
run 100ns
#45
force dime 1
run 100ns
force dime 0
run 100ns
```

14.23 Vi ritar en tillståndsgraf, *Figur 14.23a*

 

Figur 14.23a

14.23 forts.

Vi ställer upp tillståndstabell

State	Next state								thing	change
	Nickel/dime/quarter									
	000	001	010	100	011	101	110	111		
S0	S0	S9	S3	S1	-	-	-	-	0	0
S1	S2	S1	S1	S1	-	-	-	-	0	0
S2	S2	S11	S5	S3	-	-	-	-	0	0
S3	S4	S3	S3	S3	-	-	-	-	0	0
S4	S4	S13	S7	S5	-	-	-	-	0	0
S5	S6	S5	S5	S5	-	-	-	-	0	0
S6	S6	S15	S9	S7	-	-	-	-	0	0
S7	S8	S7	S7	S7	-	-	-	-	0	0
S8	S8	S19	S11	S9	-	-	-	-	0	0
S9	S10	S9	S9	S9	-	-	-	-	0	0
S10	S10	S18	S13	S11	-	-	-	-	0	0
S11	S12	S11	S11	S11	-	-	-	-	0	0
S12	S12	S17	S15	S13	-	-	-	-	0	0
S13	S14	S13	S13	S13	-	-	-	-	0	0
S14	S14	S16	S19	S15	-	-	-	-	0	0
S15	S0	S15	S15	S15	-	-	-	-	1	0
S16	S17	S17	S17	S17	-	-	-	-	0	1
S17	S18	S18	S18	S18	-	-	-	-	0	1
S18	S19	S19	S19	S19	-	-	-	-	0	1
S19	S0	S0	S0	S0	-	-	-	-	1	1

Figur 14.23b

14.24 Vi skriver VHDL-kod

```
-- ex_14_24.vhdl
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.numeric_std.all;
```

14.24 forts.

```
ENTITY ex_14_24 IS
    PORT(Clock:IN STD_LOGIC;
          Resetn:IN STD_LOGIC;
          nickel:IN STD_LOGIC;
          dime:IN STD_LOGIC;
          quarter:IN STD_LOGIC;
          z:OUT STD_LOGIC;
          change:OUT STD_LOGIC);
END ex_14_24;

ARCHITECTURE arch_ex_14_24 OF ex_14_24 IS
    TYPE state_type IS (S0,S1,S2,S3,S4,S5,S6,S7,S8,S9,
                        10,S11,S12,S13,S14,S15,S16,S17,S18,S19);
    SIGNAL state_signal:state_type;
    SIGNAL next_state_signal:state_type;
    SIGNAL nickel_dime_quarter_signal:
        STD_LOGIC_VECTOR(2 DOWNTO 0);
    SIGNAL value:NATURAL RANGE 0 TO 60:=0;
    BEGIN
        nickel_dime_quarter_signal <=
            nickel & dime & quarter;

    state_transition_proc:
        PROCESS(Resetn,Clock)
        BEGIN
            IF (Resetn='0') THEN
                state_signal<=S0;
            ELSIF rising_edge(Clock) THEN
                state_signal<=next_state_signal;
            END IF;
        END PROCESS state_transition_proc;

    stateflow_proc:
        PROCESS(state_signal,nickel,dime)
        BEGIN
            CASE state_signal IS
                WHEN S0 =>
                    value <= 0;
                    IF nickel_dime_quarter_signal = "000" THEN
                        next_state_signal <= S0;
                    ELSIF nickel_dime_quarter_signal = "001" THEN
                        next_state_signal <= S9;
```

14.24 forts.

```
ELSIF nickel_dime_quarter_signal = "010" THEN
    next_state_signal <= S3;
ELSIF nickel_dime_quarter_signal = "100" THEN
    next_state_signal <= S1;
ELSE
    next_state_signal <= S0;
END IF;
WHEN S1 =>
    value <= 5;
    IF nickel_dime_quarter_signal = "000" THEN
        next_state_signal <= S2;
    ELSIF nickel_dime_quarter_signal = "001" THEN
        next_state_signal <= S1;
    ELSIF nickel_dime_quarter_signal = "010" THEN
        next_state_signal <= S1;
    ELSIF nickel_dime_quarter_signal = "100" THEN
        next_state_signal <= S1;
    ELSE
        next_state_signal <= S0;
    END IF;
WHEN S2 =>
    value <= 5;
    IF nickel_dime_quarter_signal = "000" THEN
        next_state_signal <= S2;
    ELSIF nickel_dime_quarter_signal = "001"
    THEN
        next_state_signal <= S11;
    ELSIF nickel_dime_quarter_signal = "010"
    THEN
        next_state_signal <= S5;
    ELSIF nickel_dime_quarter_signal = "100"
    THEN
        next_state_signal <= S3;
    ELSE
        next_state_signal <= S0;
    END IF;
WHEN S3 =>
    value <= 10;
    IF nickel_dime_quarter_signal = "000" THEN
        next_state_signal <= S4;
    ELSIF nickel_dime_quarter_signal = "001" THEN
        next_state_signal <= S3;
    ELSIF nickel_dime_quarter_signal = "010" THEN
        next_state_signal <= S3;
```

14.24 forts.

```
ELSIF nickel_dime_quarter_signal = "100" THEN
    next_state_signal <= S3;
ELSE
    next_state_signal <= S0;
END IF;
WHEN S4 =>
    value <= 10;
    IF nickel_dime_quarter_signal = "000" THEN
        next_state_signal <= S4;
    ELSIF nickel_dime_quarter_signal = "001"
        THEN
        next_state_signal <= S13;
    ELSIF nickel_dime_quarter_signal = "010"
        THEN
        next_state_signal <= S7;
    ELSIF nickel_dime_quarter_signal = "100"
        THEN
        next_state_signal <= S5;
    ELSE
        next_state_signal <= S0;
    END IF;
WHEN S5 =>
    value <= 15;
    IF nickel_dime_quarter_signal = "000" THEN
        next_state_signal <= S6;
    ELSIF nickel_dime_quarter_signal = "001" THEN
        next_state_signal <= S5;
    ELSIF nickel_dime_quarter_signal = "010" THEN
        next_state_signal <= S5;
    ELSIF nickel_dime_quarter_signal = "100" THEN
        next_state_signal <= S5;
    ELSE
        next_state_signal <= S0;
    END IF;
WHEN S6 =>
    value <= 15;
    IF nickel_dime_quarter_signal = "000" THEN
        next_state_signal <= S6;
    ELSIF nickel_dime_quarter_signal = "001" THEN
        next_state_signal <= S15;
    ELSIF nickel_dime_quarter_signal = "010" THEN
        next_state_signal <= S9;
    ELSIF nickel_dime_quarter_signal = "100" THEN
        next_state_signal <= S7;
```

14.24 forts.

```
ELSE
    next_state_signal <= S0;
END IF;
WHEN S7 =>
    value <= 20;
    IF nickel_dime_quarter_signal = "000" THEN
        next_state_signal <= S8;
    ELSIF nickel_dime_quarter_signal = "001" THEN
        next_state_signal <= S7;
    ELSIF nickel_dime_quarter_signal = "010" THEN
        next_state_signal <= S7;
    ELSIF nickel_dime_quarter_signal = "100" THEN
        next_state_signal <= S7;
    ELSE
        next_state_signal <= S0;
    END IF;
WHEN S8 =>
    value <= 20;
    IF nickel_dime_quarter_signal = "000" THEN
        next_state_signal <= S8;
    ELSIF nickel_dime_quarter_signal = "001" THEN
        next_state_signal <= S19;
    ELSIF nickel_dime_quarter_signal = "010" THEN
        next_state_signal <= S11;
    ELSIF nickel_dime_quarter_signal = "100" THEN
        next_state_signal <= S9;
    ELSE
        next_state_signal <= S0;
    END IF;
WHEN S9 =>
    value <= 25;
    IF nickel_dime_quarter_signal = "000" THEN
        next_state_signal <= S10;
    ELSIF nickel_dime_quarter_signal = "001" THEN
        next_state_signal <= S9;
    ELSIF nickel_dime_quarter_signal = "010" THEN
        next_state_signal <= S9;
    ELSIF nickel_dime_quarter_signal = "100" THEN
        next_state_signal <= S9;
    ELSE
        next_state_signal <= S0;
    END IF;
WHEN S10 =>
    value <= 25;
```

14.24 forts.

```
IF nickel_dime_quarter_signal = "000" THEN
    next_state_signal <= S10;
ELSIF nickel_dime_quarter_signal = "001" THEN
    next_state_signal <= S18;
ELSIF nickel_dime_quarter_signal = "010" THEN
    next_state_signal <= S13;
ELSIF nickel_dime_quarter_signal = "100" THEN
    next_state_signal <= S11;
ELSE
    next_state_signal <= S0;
END IF;
WHEN S11 =>
    value <= 30;
    IF nickel_dime_quarter_signal = "000" THEN
        next_state_signal <= S12;
    ELSIF nickel_dime_quarter_signal = "001" THEN
        next_state_signal <= S11;
    ELSIF nickel_dime_quarter_signal = "010" THEN
        next_state_signal <= S11;
    ELSIF nickel_dime_quarter_signal = "100" THEN
        next_state_signal <= S11;
    ELSE
        next_state_signal <= S0;
    END IF;
WHEN S12 =>
    value <= 30;
    IF nickel_dime_quarter_signal = "000" THEN
        next_state_signal <= S12;
    ELSIF nickel_dime_quarter_signal = "001"
        THEN
        next_state_signal <= S17;
    ELSIF nickel_dime_quarter_signal = "010"
        THEN
        next_state_signal <= S15;
    ELSIF nickel_dime_quarter_signal = "100"
        THEN
        next_state_signal <= S13;
    ELSE
        next_state_signal <= S0;
    END IF;
WHEN S13 =>
    value <= 35;
    IF nickel_dime_quarter_signal = "000" THEN
        next_state_signal <= S14;
```

```

        ELSIF nickel_dime_quarter_signal = "001" THEN
            next_state_signal <= S13;
        ELSIF nickel_dime_quarter_signal = "010" THEN
            next_state_signal <= S13;
        ELSIF nickel_dime_quarter_signal = "100" THEN
            next_state_signal <= S13;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S14 =>
        value <= 35;
        IF nickel_dime_quarter_signal = "000" THEN
            next_state_signal <= S14;
        ELSIF nickel_dime_quarter_signal = "001" THEN
            next_state_signal <= S16;
        ELSIF nickel_dime_quarter_signal = "010" THEN
            next_state_signal <= S19;
        ELSIF nickel_dime_quarter_signal = "100" THEN
            next_state_signal <= S15;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S15 =>
        value <= 40;
        IF nickel_dime_quarter_signal = "000" THEN
            next_state_signal <= S0;
        ELSIF nickel_dime_quarter_signal = "001" THEN
            next_state_signal <= S15;
        ELSIF nickel_dime_quarter_signal = "010" THEN
            next_state_signal <= S15;
        ELSIF nickel_dime_quarter_signal = "100" THEN
            next_state_signal <= S15;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S16 =>
        value <= 60;
        IF nickel_dime_quarter_signal = "000" THEN
            next_state_signal <= S17;
        ELSIF nickel_dime_quarter_signal = "001" THEN
            next_state_signal <= S17;
        ELSIF nickel_dime_quarter_signal = "010" THEN
            next_state_signal <= S17;
        ELSIF nickel_dime_quarter_signal = "100" THEN
            next_state_signal <= S17;

```

14.24 forts.

```
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S17 =>
        value <= 55;
        IF nickel_dime_quarter_signal = "000" THEN
            next_state_signal <= S18;
        ELSIF nickel_dime_quarter_signal = "001" THEN
            next_state_signal <= S18;
        ELSIF nickel_dime_quarter_signal = "010" THEN
            next_state_signal <= S18;
        ELSIF nickel_dime_quarter_signal = "100" THEN
            next_state_signal <= S18;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S18 =>
        value <= 50;
        IF nickel_dime_quarter_signal = "000" THEN
            next_state_signal <= S19;
        ELSIF nickel_dime_quarter_signal = "001" THEN
            next_state_signal <= S19;
        ELSIF nickel_dime_quarter_signal = "010" THEN
            next_state_signal <= S19;
        ELSIF nickel_dime_quarter_signal = "100" THEN
            next_state_signal <= S19;
        ELSE
            next_state_signal <= S0;
        END IF;
    WHEN S19 =>
        value <= 45;
        IF nickel_dime_quarter_signal = "000" THEN
            next_state_signal <= S0;
        ELSIF nickel_dime_quarter_signal = "001" THEN
            next_state_signal <= S0;
        ELSIF nickel_dime_quarter_signal = "010" THEN
            next_state_signal <= S0;
        ELSIF nickel_dime_quarter_signal = "100" THEN
            next_state_signal <= S0;
        ELSE
            next_state_signal <= S0;
        END IF;
    END CASE;
END PROCESS stateflow_proc;
```

14.24 forts.

```
assignment_proc:
PROCESS(state_signal,nickel,dime)
BEGIN
    CASE state_signal IS
        WHEN S15 =>
            z <= '1';
            change <= '0';
        WHEN S16 =>
            z <= '0';
            change <= '1';
        WHEN S17 =>
            z <= '0';
            change <= '1';
        WHEN S18 =>
            z <= '0';
            change <= '1';
        WHEN S19 =>
            z <= '1';
            change <= '1';
        WHEN OTHERS =>
            z <= '0';
            change <= '0';
    END CASE;
END PROCESS assignment_proc;
END arch_ex_14_24;
```

Och vi simulerar med en do-fil som inte är heltäckande

```
-- ex_14_24.do
restart -f -nowave
view signals wave
add wave Clock Resetn nickel dime quarter
add wave state_signal next_state_signal z change
add wave -radix unsigned value
force Clock 0 0, 1 50ns -repeat 100ns
force nickel 0
force dime 0
force quarter 0
force Resetn 0
run 225ns
force Resetn 1
```

14.24 forts.

```
#1 dime = 10
force dime 1
run 100ns
force dime 0
run 100ns
#1+1 dime = 20
force dime 1
run 100ns
force dime 0
run 100ns
#1+1+1 dime = 30
force dime 1
run 100ns
force dime 0
run 100ns
#1+1+1+1 dime = 40
force dime 1
run 100ns
force dime 0
run 100ns
#5
force nickel 1
run 100ns
force nickel 0
run 100ns
#10
force nickel 1
run 100ns
force nickel 0
run 100ns
#15
force nickel 1
run 100ns
force nickel 0
run 100ns
#20
force nickel 1
run 100ns
force nickel 0
run 100ns
```

14.24 forts.

```
#25
force nickel 1
run 100ns
force nickel 0
run 100ns
#30
force nickel 1
run 100ns
force nickel 0
run 100ns
#35
force nickel 1
run 100ns
force nickel 0
run 100ns
#40
force nickel 1
run 100ns
force nickel 0
run 100ns
force quarter 1
run 100ns
force quarter 0
run 100ns
force quarter 1
run 100ns
force quarter 0
run 400ns
```

14.25 Lösningen utelämnas nu den blir så komplicerad att vi ändå inte kan gå igenom den

14.26 Lösningen utelämnas nu den blir så komplicerad att vi ändå inte kan gå igenom den

14.27 Lösningen utelämnas nu den blir så komplicerad att vi ändå inte kan gå igenom den

14.28 Lösningen utelämnas nu den blir så komplicerad att vi ändå inte kan gå igenom den

14.29 Lösningen utelämnas nu den blir så komplicerad att vi ändå inte kan gå igenom den

14.30 Lösningen utelämnas nu den blir så komplicerad att vi ändå inte kan gå igenom den

14.31 Lösningen utelämnas nu den blir så komplicerad att vi ändå inte kan gå igenom den