

# VHDL

## part 2

So far we've only looked at pure logic

To day we will look at clocked designs,  
conditional coding and shift operations

We will also look at testbenches

Let's start with the counter from the introductory lab assignment

We will do the implementation in three different ways

- Using a `STD_LOGIC_VECTOR` counting value
- Using an `INTEGER` counting value
- Using our ripple carry adder as component

Let's start with the entity. This will be the same no matter the implementation

We have a counter that should count from zero to twelve and then start all over again.

The counting is controlled by a clock signal

There is also a reset signal

We will start by making the design work for the given counting range and then make it generic

We have the entity

```
 ENTITY counter IS
  PORT (clk:IN STD_LOGIC;
        reset_n:IN STD_LOGIC;
        count:OUT STD_LOGIC_VECTOR(3 DOWNTO 0));
 END counter;
```

\_n indicates that the signal is active low ('0')

The size of the vector is given by  
the counting range

```
 ENTITY counter IS
  PORT (clk:IN STD_LOGIC;
        reset_n:IN STD_LOGIC;
        count:OUT STD_LOGIC_VECTOR(3 DOWNTO 0));
 END counter;
```

The architecture

Since the design is triggered by a clock signal we must have a process with the clock signal in the sensitivity list

The count port in the entity is of type OUT so it can't be read but we need to read the value to be able to add one (1) to it.

We introduce a SIGNAL as the active counting signal

```

ENTITY counter IS
  PORT (clk:IN STD_LOGIC;
        reset_n:IN STD_LOGIC;
        count:OUT STD_LOGIC_VECTOR(3 DOWNTO 0));
END counter;

```

## The architecture cont.

Let's see what we have so far

```

ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:std_logic_vector(3 DOWNTO 0);
BEGIN
  count_process:
  PROCESS(clk)
  BEGIN
    END PROCESS count_process;
END arch_counter_std_logic;

```

```

ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:std_logic_vector(3 DOWNTO 0);
BEGIN
  count_process:
  PROCESS(clk)
  BEGIN
    END PROCESS count_process;
END arch_counter_std_logic;

```

## The architecture cont.

The process we have written will be activated as soon as the clock signal `clk` changes value, that is on both positive and negative clock flank. This is not what we want.

Besides that: the counter value will be stored in flip-flops between the triggerings and flip-flops can only trigger on one flank, **not both**.

We must make sure that we trigger on only one flank.  
Let's take the positive flank

## The architecture cont.

Let's see what we have so far

```
ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:std_logic_vector(3 DOWNTO 0);
BEGIN
  count_process:
  PROCESS(clk)
  BEGIN
    IF RISING_EDGE(clk) THEN
      ...
    END IF;
  END PROCESS count_process;
END arch_counter_std_logic;
```

This is our first conditional code. We'll soon talk more about it

Negative flank is called FALLING\_EDGE

Note that you can only trigger on one flank, **never** on both

## The architecture cont.

```
ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:std_logic_vector(3 DOWNTO 0);
BEGIN
  count_process:
  PROCESS(clk)
  BEGIN
    IF RISING_EDGE(clock) THEN
      ...
    END IF;
  END PROCESS count_process;
END arch_counter_std_logic;
```

There is also an active low reset signal that should control the design.

We can make the reset signal either synchronous or asynchronous

In the synchronous case the counter will be reset synchronous with the clock that is on the positive flank of the clock signal

In the asynchronous case the counter will be reset as soon as the reset signal is activated

## The architecture cont.

### Synchronous implementation of the reset signal

```

ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:std_logic_vector(3 DOWNTO 0);
BEGIN
  count_process:
  PROCESS(clk)
  BEGIN
    IF RISING_EDGE(clk) THEN
      ...
    END IF;
  END PROCESS count_process;
END arch_counter_std_logic;

```

The process is only triggered by the clock

Keep the two IF clauses separate

Reset is within the RISING\_EDGE structure

A simple way to set all bits in the vector to zero (0)

## The architecture cont.

### Asynchronous implementation of the reset signal

```

ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:std_logic_vector(3 DOWNTO 0);
BEGIN
  count_process:
  PROCESS(reset_n,clk)
  BEGIN
    IF ((reset_n='0') THEN
      ...
    ELSIF RISING_EDGE(clk) THEN
      ...
    END IF;
  END PROCESS count_process;
END arch_counter_std_logic;

```

The process is triggered by both the reset and the clock signal

Reset outside of the RISING\_EDGE structure

Let's keep the asynchronous version

## The architecture cont.

Now VHDL doesn't have any rules for addition to `std_logic_vectors`.

To do arithmetic operations the system must know if the value should be treated as a signed or an unsigned value.

We introduce the `std_logic_vector` subtypes `SIGNED` and `UNSIGNED`.

To do this we must include another library

```
USE ieee.numeric_std.ALL;
```

**Don't use** the old libraries `std_logic_signed` and `std_logic_unsigned`. They are not part of VHDL anymore

## The architecture cont.

Let's update

```
ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:std_logic_vector(3 DOWNTO 0);
BEGIN
  count_process:
  PROCESS(reset_n,clk)
  BEGIN
    IF ((reset_n='0') THEN
      count_signal<=(OTHERS=>'0')
    ELSIF RISING_EDGE(clk) THEN
      count_signal<=count_signal+1;
    END IF;
  END PROCESS count_process;
END arch_counter_std_logic;
```

Since we only count positive values we use the `UNSIGNED` type

`count_signal` is of subtype `UNSIGNED` in the whole process

## The architecture cont.

The counting value will have to be passed on to the output port

```
ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:UNSIGNED(3 DOWNTO 0);
BEGIN
  count_process:
  PROCESS(reset_n,clk)
  BEGIN
    IF ((reset_n='0') THEN
      count_signal<=(OTHERS=>'0')
    ELSIF RISING_EDGE(clk) THEN
      count_signal<=count_signal+1;
    END IF;
  END PROCESS count_process;
  count<=STD_LOGIC_VECTOR(count_signal);
END arch_counter_std_logic;
```

The value must be interpreted as a std\_logic\_vector when passed on to the output

## The architecture cont.

```
ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:UNSIGNED(3 DOWNTO 0);
BEGIN
  count_process:
  PROCESS(clk)
  BEGIN
    IF RISING_EDGE(clock) THEN
      count_signal<=count_signal+1;
    END IF;
  END PROCESS count_process;
  count<=STD_LOGIC_VECTOR(count_signal);
END arch_counter_std_logic;
```

The transfer to the output is done outside of the process.  
Can we just as well do it within the process?

No!

If we put it in the process then the value will have to be remembered from one clock pulse to the next so we have to store it in flip-flops and it will also take one extra clock cycle for this value to update

If we put it outside of the process then it will only be wires from the count\_signal, no extra flip-flops

## The architecture cont.

```

ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:UNSIGNED(3 DOWNTO 0);
BEGIN
  count_process:
  PROCESS(clk)
  BEGIN
    IF RISING_EDGE(clock) THEN
      count_signal<=count_signal+1;
    END IF;
  END PROCESS count_process;
  count<=STD_LOGIC_VECTOR(count_signal);
END arch_counter_std_logic;

```

We must make sure that the counter goes back to zero (0) when we have counted up to the maximal value twelve (12).

We need one more condition

## The architecture cont.

```

ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:UNSIGNED(3 DOWNTO 0);
BEGIN
  count_process:
  PROCESS(reset_n,clk)
  BEGIN
    IF ((reset_n='0') THEN
      count_signal<=(OTHERS=>'0');
    ELSIF RISING_EDGE(clk) THEN
      IF (count_signal="1100") THEN
        count_signal<=(OTHERS=>'0');
      ELSE
        count_signal<=count_signal+1;
      END IF;
    END IF;
  END PROCESS count_process;
  count<=STD_LOGIC_VECTOR(count_signal);
END arch_counter_std_logic;

```

```

ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:UNSIGNED(3 DOWNTO 0);
BEGIN
  count_process:
  PROCESS(clk)
  BEGIN
    IF RISING_EDGE(clock) THEN
      count_signal<=count_signal+1;
    END IF;
  END PROCESS count_process;
  count<=STD_LOGIC_VECTOR(count_signal);
END arch_counter_std_logic;

```

Don't mix the clocking condition  
(RISING\_EDGE)  
with any of the other conditions.

## The architecture cont.

We could have used a count variable instead of the count signal

```
ARCHITECTURE arch_counter OF counter IS
BEGIN
    count_process:
    PROCESS(clk)
        VARIABLE count_variable:UNSIGNED(3 DOWNTO 0);
    BEGIN
        IF RISING_EDGE(clk)
            IF (reset_n='0') THEN
                count_variable:=(OTHERS=>'0');
            ELSIF (count_variable="1100") THEN
                count_variable:=(OTHERS=>'0');
            ELSE
                count_variable:=count_variable+1;
            END IF;
        END IF;
        count<=STD_LOGIC_VECTOR(count_variable);
    END PROCESS count_process;
END arch_counter_std_logic;
```

```
ARCHITECTURE arch_counter OF counter IS
SIGNAL count_signal:UNSIGNED(3 DOWNTO 0);
BEGIN
    count_process:
    PROCESS(clk)
    BEGIN
        IF RISING_EDGE(clock)
            IF (reset_n='0') THEN
                count_signal<=(OTHERS=>'0');
            ELSIF (count_signal="1100") THEN
                count_signal<=(OTHERS=>'0');
            ELSE
                count_signal:=count_signal+1;
            END IF;
        END IF;
    END PROCESS count_process;
    count<=STD_LOGIC_VECTOR(count_signal);
END arch_counter_std_logic;
```

The variable is local to the process

Notice the variable assignment

Since the variable is local to the process its value must be transferred to the output within the process. This will not give any extra flipflops though

## The architecture cont.

Now let's see how we can use an integer as the counting parameter.

If we just declare the parameter as an integer then it will be of size 32 bits which is a waste of hardware so we limit the range.

Since the counter only count from zero and upwards we can also limit the range by using NATURAL numbers.

```
ARCHITECTURE arch_counter OF counter IS
SIGNAL count_signal:UNSIGNED(3 DOWNTO 0);
BEGIN
    count_process:
    PROCESS(clk)
    BEGIN
        IF RISING_EDGE(clock) THEN
            count_signal<=count_signal+1;
        END IF;
    END PROCESS count_process;
    count<=STD_LOGIC_VECTOR(count_signal);
END arch_counter_std_logic;
```

### The architecture cont.

We could have used an integer instead of std\_logic as the count parameter.

```
ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:NATURAL RANGE 0 to 12;
BEGIN
  count_process:
  PROCESS(clk)
  BEGIN
    IF RISING_EDGE(clk)
      IF (reset_n='0') THEN
        count_signal<=0;
      ELSIF (count_signal=12) THEN
        count_signal<=0;
      ELSE
        count_signal<=count_signal+1;
      END IF;
    END IF;
  END IF;
  END PROCESS count_process;
  count<=STD_LOGIC_VECTOR(TO_UNSIGNED(count_signal,4));
END arch_counter_std_logic;
```

```
ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:UNSIGNED(3 DOWNTO 0);
BEGIN
  count_process:
  PROCESS(clk)
  BEGIN
    IF RISING_EDGE(clock)
      IF (reset_n='0') THEN
        count_signal<=(OTHERS=>'0');
      ELSIF (count_signal="1100") THEN
        count_signal<=(OTHERS=>'0');
      ELSE
        count_signal<=count_signal+1;
      END IF;
    END IF;
  END PROCESS count_process;
  count<=STD_LOGIC_VECTOR(count_signal);
END arch_counter_std_logic;
```

Limited range of the integer subtype NATURAL

First we go from NATURAL to UNSIGNED and then to std\_logic\_vector

We must give the number of bits for the vector

### The architecture cont.

For the third option we will use our earlier ripple carry adder as a component to do the addition.

A component is a fixed instantiation and can not be placed in the sequential code of a process.

We should instantiate the component outside of the process and then assign values to it from within the process using signals

## The architecture cont.

We start with the component and other stuff outside of the process

```

ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:UNSIGNED(3 DOWNTO 0);
  COMPONENT ripple_adder IS
    GENERIC(WIDTH:NATURAL:=4);
    PORT(a:IN STD_LOGIC_VECTOR(WIDTH-1 DOWNTO 0);
         b:IN STD_LOGIC_VECTOR(WIDTH-1 DOWNTO 0);
         y:OUT STD_LOGIC_VECTOR(WIDTH-1 DOWNTO 0));
  END COMPONENT ripple_adder;
  SIGNAL adder_a_signal:STD_LOGIC_VECTOR(3 DOWNTO 0);
  SIGNAL adder_y_signal:STD_LOGIC_VECTOR(3 DOWNTO 0);
BEGIN
  ripple_adder_comp:
  ripple_adder
    GENERIC MAP(WIDTH=>4)
    PORT MAP(a=>adder_a_signal, b=>"0001",y=>adder_y_signal);

```

Here we can use  
STD\_LOGIC\_VECTOR  
since we never do any  
addition in the code

We always add one

## The architecture cont.

And then the process

```

PROCESS(reset_n,clk)
BEGIN
  IF (reset_n='0') THEN
    adder_a_signal<="1111";
  ELSIF RISING_EDGE(clk) THEN
    IF (adder_y_signal="1100") THEN
      adder_a_signal<="1111"; Together with "0001" in  
b this will give zero
    ELSE
      adder_a_signal<=adder_y_signal;
    END IF;
  END IF;
  END PROCESS count_process;
  count<=adder_y_signal; Transfer from counting  
signal to output
END arch_counter;

```

## The architecture cont.

Let's add one last feature to our design.

We introduce an enable signal so we can start and stop the counter.

This port should also be added to the entity.

```
ENTITY counter IS
  PORT (clk:IN STD_LOGIC;
        reset_n:IN STD_LOGIC;
        enable:IN STD_LOGIC;
        count:OUT STD_LOGIC_VECTOR(3 DOWNTO 0));
END counter;
```

Let's use the UNSIGNED version of the counter with an asynchronous reset.

## The architecture cont.

```
ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:UNSIGNED(3 DOWNTO 0);
BEGIN
  count_process:
  PROCESS(reset_n,clk)
  BEGIN
    IF (reset_n='0') THEN
      count_signal<=(OTHERS=>'0');
    ELSIF RISING_EDGE(clk)
      IF (enable='1') THEN
        IF (count_signal="1100") THEN
          count_signal<=(OTHERS=>'0');
        ELSE
          count_signal<=count_signal+1;
        END IF;
      END IF;
    END PROCESS count_process;
    count<=STD_LOGIC_VECTOR(count_signal);
  END arch_counter_std_logic;
```

If written this way the counter can be reset although it isn't enabled.

How would you write if you only want to be able to reset it when it's enabled?

## The architecture cont.

```

ARCHITECTURE arch_counter OF counter IS
    SIGNAL count_signal:UNSIGNED(3 DOWNTO 0);
BEGIN
    count_process:
    PROCESS(reset_n,clk,enable)
    BEGIN
        IF ((reset_n='0') AND (enable='1')) THEN
            count_signal<=(OTHERS=>'0');
        ELSIF RISING EDGE(clk)
            IF (enable='1') THEN
                IF (count_signal="1100") THEN
                    count_signal<=(OTHERS=>'0');
                ELSE
                    count_signal<=count_signal+1;
                END IF;
            END IF;
        END PROCESS count_process;
        count<=STD_LOGIC_VECTOR(count_signal);
    END arch_counter_std_logic;

```

The asynchronous reset makes it a bit complicated

## Generic counter

```

ENTITY counter IS
    PORT (clk:IN STD_LOGIC;
          reset_n:IN STD_LOGIC;
          enable:IN STD_LOGIC;
          count:OUT STD_LOGIC_VECTOR(3 DOWNTO 0));
END counter;

```

Let's look at how to make our designs generic

First the entity.

What we have to do is add a GENERIC and make that control the size of the count port

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
USE ieee.math_real.ALL;

ENTITY counter IS
    GENERIC (COUNT_MAX:NATURAL:=12);
    PORT (clk:IN STD_LOGIC;
          reset_n:IN STD_LOGIC;
          count:OUT STD_LOGIC_VECTOR( INTEGER(CEIL(LOG2(REAL(COUNT_MAX))))-1 DOWNTO 0));
END counter;

```

We calculate the size of the port

LOG2 only works on REAL values and is included in the math\_real library

Round upwards

From REAL to INTEGER

We have three different implementations so we must look at what needs to be done to them to make them generic.

Let's look at the versions without enable signal to make it simple.

We start with the version with `std_logic_vector` and `UNSIGNED` vector.

We must make the size of the `count_signal` generic.

We do this in the same way as in the entity but since we need to do this more than once we use it to set a constant that we can reuse

```
CONSTANT NO_BITS:NATURAL:=INTEGER(CEIL(LOG2(REAL(COUNT_MAX))));
```

Then we can use this to set the size of the count signal and to set the max value for the calculation

```
ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:UNSIGNED(3 DOWNTO 0);
BEGIN
  count_process:
  PROCESS(reset_n,clk)
  BEGIN
    IF ((reset_n='0') THEN
      count_signal<=(OTHERS=>'0');
    ELSIF RISING_EDGE(clk) THEN
      IF (count_signal="1100") THEN
        count_signal<=(OTHERS=>'0');
      ELSE
        count_signal<=count_signal+1;
      END IF;
    END IF;
  END PROCESS count_process;
  count<=STD_LOGIC_VECTOR(count_signal);
END arch_counter_std_logic;
```

```

ARCHITECTURE arch_counter OF counter IS
  CONSTANT NO_BITS:NATURAL:=INTEGER(CEIL(LOG2(REAL(COUNT_MAX))));
  CONSTANT MAX_VECTOR:UNSIGNED(NO_BITS-1 DOWNTO 0):=
    TO_UNSIGNED(COUNT_MAX,NO_BITS);
  SIGNAL count_signal:UNSIGNED(NO_BITS-1 DOWNTO 0);
BEGIN
  count_process:
  PROCESS(reset_n,clk)
  BEGIN
    IF (reset_n='0') THEN
      count_signal<=(OTHERS=>'0');
    ELSIF RISING_EDGE(clk) THEN
      IF (count_signal=MAX_VECTOR) THEN
        count_signal<=(OTHERS=>'0');
      ELSE
        count_signal<=count_signal+1;
      END IF;
    END IF;
  END PROCESS count_process;
  count<=STD_LOGIC_VECTOR(count_signal);
END arch_counter;

```

Interpret UNSIGNED as  
STD\_LOGIC\_VECTOR

No for the version with the NATURAL  
count variable.

Here the size of the count signal is  
already given by the GENERIC.

The only thing we need to do is set the  
number of bits for the count port.

```

ARCHITECTURE arch_counter OF counter IS
  SIGNAL count_signal:NATURAL RANGE 0 to 12;
BEGIN
  count_process:
  PROCESS(clk)
  BEGIN
    IF RISING_EDGE(clk)
      IF (reset_n='0') THEN
        count_signal<=0;
      ELSIF (count_signal=12) THEN
        count_signal<=0;
      ELSE
        count_signal<=count_signal+1;
      END IF;
    END IF;
  END PROCESS count_process;
  count<=STD_LOGIC_VECTOR(TO_UNSIGNED(count_signal,4));
END arch_counter_std_logic;

```

```
ARCHITECTURE arch_counter OF counter IS
  CONSTANT NO_BITS:NATURAL:=INTEGER(CEIL(LOG2(REAL(COUNT_MAX)) ));
  SIGNAL count_signal:NATURAL RANGE 0 TO COUNT_MAX;
BEGIN
  count_process:
  PROCESS(reset_n,clk)
  BEGIN
    IF (reset_n='0') THEN
      count_signal<=0;
    ELSIF RISING_EDGE(clk) THEN
      IF (count_signal=COUNT_MAX) THEN
        count_signal<=0;
      ELSE
        count_signal<=count_signal+1;
      END IF;
    END IF;
  END PROCESS count_process;
  count<=STD_LOGIC_VECTOR(TO_UNSIGNED(count_signal,NO_BITS));
END arch_counter;
```

No for the version with the adder component.

The changes are similar to the earlier ones.

We split the solution into two slides.

```

ARCHITECTURE arch_counter OF counter IS
  CONSTANT NO_BITS:NATURAL:=INTEGER(CEIL(LOG2(REAL(COUNT_MAX))));
  CONSTANT MAX_VECTOR:STD_LOGIC_VECTOR(NO_BITS-1 DOWNTO 0):=
    STD_LOGIC_VECTOR(TO_UNSIGNED(COUNT_MAX,NO_BITS));

  SIGNAL count_signal:UNSIGNED(NO_BITS-1 DOWNTO 0);
  COMPONENT ripple_adder IS
    GENERIC(WIDTH:NATURAL:=8);
    PORT(a:IN STD_LOGIC_VECTOR(NO_BITS-1 DOWNTO 0);
         b:IN STD_LOGIC_VECTOR(NO_BITS-1 DOWNTO 0);
         y:OUT STD_LOGIC_VECTOR(NO_BITS-1 DOWNTO 0));
  END COMPONENT ripple_adder;
  SIGNAL adder_a_signal:STD_LOGIC_VECTOR(NO_BITS-1 DOWNTO 0);
  SIGNAL adder_b_signal:STD_LOGIC_VECTOR(NO_BITS-1 DOWNTO 0);
  SIGNAL adder_y_signal:STD_LOGIC_VECTOR(NO_BITS-1 DOWNTO 0);
  CONSTANT B_CONSTANT:STD_LOGIC_VECTOR(NO_BITS-1 DOWNTO 0):=
    STD_LOGIC_VECTOR(TO_UNSIGNED(1,NO_BITS));
BEGIN
  --> This gives a vector with the
  value 000...1

```

```

BEGIN
  ripple_adder_comp:
  ripple_adder
    GENERIC MAP(WIDTH=>NO_BITS)
    PORT MAP(a=>adder_a_signal,
              b=>B_CONSTANT,--> The b input is
              y=>adder_y_signal);--> always one
  count_process:
  PROCESS(reset_n,clk)
  BEGIN
    IF (reset_n='0') THEN
      adder_a_signal<=(OTHERS=>'1');--> Together with
    ELSIF RISING_EDGE(clk) THEN
      IF (adder_y_signal=MAX_VECTOR) THEN
        adder_a_signal<=(OTHERS=>'1');--> b we get zero
      ELSE
        adder_a_signal<=adder_y_signal;
      END IF;
    END IF;
  END PROCESS count_process;
  count<=STD_LOGIC_VECTOR(adder_y_signal);
END arch_counter;

```

## Conditional coding cont.

We've touched on conditional coding by using IF


Let's look at it a bit more taking a MUX as an example

We can do this with or without a process.

The coding will not be the same though

But the entity is the same

 
```
ENTITY conditional_MUX IS
  PORT (a:IN STD_LOGIC;
        b:IN STD_LOGIC;
        control:IN STD_LOGIC;
        s:OUT STD_LOGIC);
END conditional_MUX;
```


 
## Conditional coding cont.

In concurrent code we get

```
ARCHITECTURE arch_conditional_MUX_conc OF
conditional_when IS
BEGIN
  s<=b WHEN (control='1') ELSE
  a;
END arch_conditional_MUX_conc;
```




Make sure to cover all values for control

Remember that there are nine possible values for STD\_LOGIC
 
## Conditional coding cont.

In a process we get

```
ARCHITECTURE arch_conditional_MUX_proc OF
conditional_when IS
BEGIN
if_proc:
  PROCESS(control)
  BEGIN
    IF (control='1') THEN
      s<=b;
    ELSE
      s<=a;
    END IF;
  END PROCESS if_proc; END
arch_conditional_MUX_proc;
```



The problem is that  
this won't work!

Why?

## Conditional coding cont.

The process only triggers when control  
changes value and doesn't care what happens in  
between. It doesn't react to changes in a or b

To make it work we must add all signals that  
influence the output to the sensitivity list

```
ARCHITECTURE arch_conditional_MUX_proc OF
conditional_when IS
BEGIN
if_proc:
  PROCESS(control)
  BEGIN
    IF (control='1') THEN
      s<=b;
    ELSE
      s<=a;
    END IF;
  END PROCESS if_proc;
END arch_conditional_MUX_proc;
```


```
ARCHITECTURE arch_conditional_MUX_proc OF
conditional_when IS
BEGIN
if_proc:
  PROCESS(control,a,b)
  BEGIN
    IF (control='1') THEN
      s<=b;
    ELSE
      s<=a;
    END IF;
  END PROCESS if_proc; END
arch_conditional_MUX_proc;
```

Make sure to cover all  
values of control
 
## Conditional coding cont.

Let's add one input to the MUX.

We need one more input and a two bit control signal.



```

ENTITY conditional_MUX IS
    PORT (a:IN STD_LOGIC;
          b:IN STD_LOGIC;
          c:IN STD_LOGIC;
          control:IN STD_LOGIC_VECTOR(1 DOWNTO 0);
          s:OUT STD_LOGIC);
END conditional_MUX;

```

## Conditional coding cont.

We get the architecture

```

ENTITY conditional_MUX IS
    PORT (a:IN STD_LOGIC;
          b:IN STD_LOGIC;
          c:IN STD_LOGIC;
          control:IN STD_LOGIC_VECTOR(1 DOWNTO 0);
          s:OUT STD_LOGIC);
END conditional_MUX;

```

```

ARCHITECTURE arch_conditional_when_3 OF
    conditional_when_3 IS
BEGIN
    s<= a WHEN (control="00") ELSE
        b WHEN (control="01") ELSE
        c;
END arch_conditional_when_3;

```

We have three inputs but the control signal has four possibilities so we need to decide what to do with the unused value.

In this code we assign c to the output in that case too but there are other possibilities

## Conditional coding cont.

We can also use another structure

```
ARCHITECTURE arch_conditional_with_select OF
    conditional_with_select IS
BEGIN
    WITH control SELECT
        s<=a WHEN "00",
        b WHEN "01",
        c WHEN OTHERS;
END arch_conditional_with_select;
```

```
ENTITY conditional_MUX IS
    PORT (a:IN STD_LOGIC;
          b:IN STD_LOGIC;
          b:IN STD_LOGIC;
          control:IN STD_LOGIC_VECTOR(1 DOWNTO 0);
          s:OUT STD_LOGIC);
END conditional_MUX;
```

It's similar to a switch  
structure in software

## Conditional coding cont.

Let's once again use a process

```
ARCHITECTURE arch_conditional_if_3 OF
    conditional_if_3 IS
BEGIN
    if_proc:
    PROCESS(control,a,b,c)
    BEGIN
        IF (control="00") THEN
            s<=a;
        ELSIF (control="01") THEN
            s<=b;
        ELSE
            s<=c;
        END IF;
    END PROCESS if_proc;
END arch_conditional_if_3;
```

```
ENTITY conditional_MUX IS
    PORT (a:IN STD_LOGIC;
          b:IN STD_LOGIC;
          b:IN STD_LOGIC;
          control:IN STD_LOGIC_VECTOR(1 DOWNTO 0);
          s:OUT STD_LOGIC);
END conditional_MUX;
```

Once again all signals from  
the assignment must be in  
the sensitivity list

## Conditional coding cont.

We have another structure here too

```

ENTITY conditional_MUX IS
  PORT (a:IN STD_LOGIC;
        b:IN STD_LOGIC;
        b:IN STD_LOGIC;
        control:IN STD_LOGIC_VECTOR(1 DOWNTO 0);
        s:OUT STD_LOGIC);
END conditional_MUX;

ARCHITECTURE arch_conditional_case OF
  conditional_case IS
BEGIN
  if_proc:
  PROCESS(control,a,b,c)
  BEGIN
    CASE control IS
      WHEN "00" =>
        s<=a;
      WHEN "01" =>
        s<=b;
      WHEN OTHERS =>
        s<=c;
    END CASE;
  END PROCESS if_proc;
END arch_conditional_case;

```


This is also simular to the software switch structure.

Once again all signals from the assignment must be in the sensitivity list
 
## Shift operations

There are a number of common shift operations

- Logic shift left
- Logic shift right
- Arithmetic shift left
- Arithmetic shift right
- Rotate



For bit patterns and unsigned numbers

For signed numbers

For bit patterns

## Shift operations

### Logic shifts

In logic shifts we treat the vector that is to be shifted as a number of bits and don't have to think about any sign of the value.

This also works for unsigned numbers.

A left shift moves the bits a number of steps to the left pushing out the bits that will no longer fit in the vector and fill the new LSB's with zeros.

Let's shift the vector 01101101 two steps to the left

01101101 → 10110100

01 are pushed out      00 are added

## Shift operations

### Logic shifts cont.

A right shift moves the bits a number of steps to the right pushing out the bits that will no longer fit in the vector and fill the new MSB's with zeros.

Let's take the same vector 01101101 and shift it three steps to the right

01101101 → 00001101

101 are pushed out      000 are added

## Shift operations

### Aritmetic shifts

In an aritmetic shift we need to take the sign of the number into account, but only when we do a right shift.

We must sign extend the number.

Let's once again take the number 01101101 and shift it two steps to the right.

The value is positive so extention means inserting zeros

$$01101101 \rightarrow 00011011$$

01 are pushed out      00 are added

A logical and an aritmetic left shift are the same

## Shift operations

### Aritmetic shifts

Let's now take another vector 11010110 and shift it two steps to the right.

The value is negative so extention means inserting ones

$$11010110 \rightarrow 11110101$$

10 are pushed out      11 are added

## Shift operations

### Rotation

In rotation a number of bits are pushed out at one end of the vector and reenters the vector at the other end.

We take the same number as before 01101101 and rotate it two steps to the right.

01101101 → 01011011  
 01 are pushed out      01 reenters

If we rotate the number three steps to the left we get

01101101 → 01101011  
 011 are pushed out      011 reenters

## Shift operations

### Implementation

We can write our own shift and rotate functions.

We assign the value to be shifted to a signal

```
SIGNAL shift_vector: STD_LOGIC_VECTOR(7 DOWNTO 0);
shift_vector<="01101101";
```

Three steps shift to the left, arithmetic or logic gives

```
shift_vector<=shift_vector(4 DOWNTO 0) & "000";
```

Two steps logic shift to the right gives

```
shift_vector<="00" & shift_vector(7 DOWNTO 2);
```

## Shift operations

### Implementation cont.

Two steps arithmetic shift to the right gives

```
shift_vector<="00" & shift_vector(7 DOWNTO 2);
```

Since the value is positive it's the same as the logical shift

Let's take a negative value

```
shift_vector<="110111010";
```

Three steps arithmetic shift to the right gives

```
shift_vector<="111" & shift_vector(7 DOWNTO 3);
```

## Shift operations

### Implementation cont.

Now rotation

```
shift_vector<="110111010";
```

Three steps rotation to the left gives

```
shift_vector<=shift_vector(4 DOWNTO 0) &
shift_vector(7 DOWNTO 5);
```

Four steps rotation to the right gives

```
shift_vector<=shift_vector(3 DOWNTO 0) &
shift_vector(7 DOWNTO 4);
```

## Shift operations

### Shifts using library functions

We have some ready made shift functions in the numeric\_std library.

Note that **you should not use** the functions in the libraries std\_logic\_signed or std\_logic\_unsigned

We have two functions

- shift\_right
- shift\_left

Each function has two declarations, one for signed values and one for unsigned values

The two versions are **overloaded**.

We don't have to declare which version that is used. The compiler uses the correct version depending on the signal type

## Shift operations

### Shifts using library functions cont.

If we for example look at shift\_left we have the function declarations

```
function shift_left ( ARG: UNSIGNED; COUNT: NATURAL) return UNSIGNED;
function shift_left ( ARG: SIGNED; COUNT: NATURAL) return SIGNED;
```

The vector to shift

The number of steps to shift.  
Positive for left shift, negative for right shift

Note that we must use the STD\_LOGIC\_VECTOR sub types SIGNED and UNSIGNED

## Shift operations

Shifts using library functions cont.

Now to shift a vector `shift_vector` three steps to the right we write

```
shift_vector<=shift_right(shift_vector, 3);
```

If the result will be sign extended or not depends on if the vector `shift_vector` is defined as `SIGNED` or as `UNSIGNED`


## Testbenches

To verify that our design is correct we need to simulate our results.

We will be using the simulator [QuestaSim](#) (or ModelSim) from Mentor for this.

To assist in the simulation we can create a kind of test fixture in VHDL, a [testbench](#).

 This is a top level design where we instantiate our own design as a component and generate input stimuli for the component and watch or check the resulting output signals. We might also check internal signals



## Testbenches cont.

We can have three different types of testbenches

- **Type 1** only generates input stimuli and we have to watch the results in the simulator
- **Type 2** generates input stimuli, checks the results and gives an OK signal if the resulting output values are correct
- **Type 3** generates input stimuli and writes a message to the simulator output window if something goes wrong with the simulation results

## Testbenches cont.

### Example

Let's take our one bit full adder as an example.


We have the entity

```
ENTITY full_adder IS
  PORT(a:IN STD_LOGIC;
       b:IN STD_LOGIC;
       cin:IN STD_LOGIC;
       s:OUT STD_LOGIC
       cout:OUT STD_LOGIC);
END full_adder;
```

## Testbenches cont.

 Example cont.

We need to generate eight different input stimuli to fully test the circuit



To simplify things we will accept that more than one signal changes its value at a given time

## Testbenches cont.

Example cont.

Let's start creating the testbench. We begin with [test benchtype 1](#)

In this case we only watch the results from the simulation and we do not need any input or output ports to the testbench.

```
ENTITY full_adder_tb1 IS
END full_adder_tb1;
```

The entity is empty since we have no inputs and no outputs

[This causes a problem in QuestaSim since by default signals that don't connect to outputs are optimized away.](#)

[To overcome this we can simulate without optimization. The paper on QuestaSim describes how to do this](#)

Example cont.

In the testbench architecture we instantiate our full adder as a component

```

ENTITY full_adder_tb1 IS
  PORT ( y_tb:OUT STD_LOGIC;
         cout_tb:OUT STD_LOGIC);
END full_adder_tb1;

ARCHITECTURE arch_full_adder_tb1 OF full_adder_tb1 IS
  COMPONENT full_adder IS
    PORT(a:IN STD_LOGIC;
         b:IN STD_LOGIC;
         cin:IN STD_LOGIC;
         s:OUT STD_LOGIC
         cout:OUT STD_LOGIC);
  END COMPONENT full_adder;
  SIGNAL a_signal:STD_LOGIC;
  SIGNAL b_signal:STD_LOGIC;
  SIGNAL cin_signal:STD_LOGIC;
  SIGNAL s_signal:STD_LOGIC;
  SIGNAL cout_signal:STD_LOGIC;
BEGIN
  full_adder_comp:COMPONENT full_adder
    PORT MAP(a=>a_tb,b=>b_tb,cout=>cout_tb,
              s=>s_signal,cout=>cout_signal);

```

## Testbenches cont.

Example cont.

We complete the architecture with the input stimuli

```

a_signal <= '0',
  '1' AFTER 100 ns,
  '0' AFTER 200 ns,
  '1' AFTER 300 ns,
  '0' AFTER 400 ns,
  '1' AFTER 500 ns,
  '0' AFTER 600 ns,
  '1' AFTER 700 ns;
b_signal <= '0',
  '1' AFTER 200 ns,
  '0' AFTER 400 ns,
  '1' AFTER 600 ns;
cin_signal <= '0',
  '1' AFTER 400 ns;
END arch_full_adder_tb1;

```

This is one of the few times when we can and should use time in our designs

The exact times are not important since we deal with simulation of a design without circuit delays

But we should create all the input signal combinations we want to test for

## Testbenches cont.

Example cont.

We need a do file.

Since the instimuli is given in the testbench all the do file need to is to set up signals we like to watch and run the simulation time.

```
-- full_adder_tb1.do

restart -f -nowave
view signals wave
add wave a_signal b_signal cin_signal | Signals to watch
add wave s_signal cout_signal
run 730ns
```

Run the simulation for this time

## Testbenches cont.

Example cont.

We move on to [test benchtype 2](#)

Here we will need a output signal that signals if something goes wrong with the output signals from the component during simulation.

We add an output to our testbench entity

```
ENTITY full_adder_tb2 IS
    PORT(test_OK:OUT STD_LOGIC);
END full_adder_tb2;
```

## Testbenches cont.

Example cont.

In the architecture we keep the component declaration and do a component instantiation using signals and not outputs

```
ARCHITECTURE arch_full_adder_tb2 OF full_adder_tb2 IS
COMPONENT full_adder IS
    PORT(a:IN STD_LOGIC;
         b:IN STD_LOGIC;
         cin:IN STD_LOGIC;
         s:OUT STD_LOGIC;
         cout:OUT STD_LOGIC);
END COMPONENT full_adder;
SIGNAL a_signal:STD_LOGIC;
SIGNAL b_signal:STD_LOGIC;
SIGNAL cin_signal:STD_LOGIC;
SIGNAL s_signal:STD_LOGIC;
SIGNAL cout_signal:STD_LOGIC;
BEGIN
    full_adder_comp:COMPONENT full_adder
    PORT MAP(a=>a_tb,b=>b_tb,cin=>cin_tb,
              s=>s_signal,cout=>cout_signal);
```

## Testbenches cont.

Example cont.

We keep the imput stimuli from testbench type 1

```
a_signal <= '0',
      '1' AFTER 100 ns,
      '0' AFTER 200 ns,
      '1' AFTER 300 ns,
      '0' AFTER 400 ns,
      '1' AFTER 500 ns,
      '0' AFTER 600 ns,
      '1' AFTER 700 ns;
b_signal <= '0',
      '1' AFTER 200 ns,
      '0' AFTER 400 ns,
      '1' AFTER 600 ns;
cin_signal <= '0',
      '1' AFTER 400 ns;
```

## Testbenches cont.

Example cont.

We have to complete the code with a test of the output signals

We write the code so that the `test_OK` signal will go low if an error occurs and then stay low even if the next stimuli gives a correct result

## Testbenches cont.

```

a_signal <= '0',
          '1' AFTER 100 ns,
          '0' AFTER 200 ns,
...
b_signal <= '0',
          '1' AFTER 200 ns,
...
cin_signal <= '0',
          '1' AFTER 400 ns;

```

Example cont.

```

test_proc:PROCESS
BEGIN
  test_OK <= '1';           Default value for test_OK
  WAIT FOR 50 ns; -- 000    Wait until the input signals have stabilized
  IF ((s_signal /= '0') OR (cout_signal /= '0')) THEN
    test_OK <= '0';          If the result isn't 00 then set test_OK low
  END IF;
  WAIT FOR 100 ns; -- 100    Test for next stimuli
  IF ((s_signal /= '1') OR (cout_signal /= '0')) THEN
    test_OK <= '0';
  END IF;
  WAIT FOR 100 ns; -- 010
  IF ((s_signal /= '1') OR (cout_signal /= '0')) THEN
    test_OK <= '0';
  END IF;
  .....                   Continue for all eight combinations
                           of input signals
END PROCESS test_proc;
END arch_test_bench_type2;

```

## Testbenches cont.


Example cont.

We need a do file here too.

The only difference from the do file for testbench type 1 is that we have added the signal `test_OK` to the signals we watch

```
-- full_adder_tb2.do

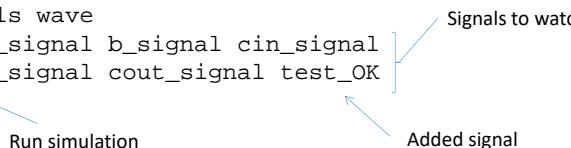restart -f -nowave
view signals wave
add wave a_signal b_signal cin_signal
add wave s_signal cout_signal test_OK
run 730ns
```



The only signal to watch in the test bench is really `test_OK` but it is practical to keep the rest of the signals for debugging

## Testbenches cont.

Example cont.

```
test:PROCESS
BEGIN
  test_OK <= '1';
  WAIT FOR 50 ns; -- 000
  IF ((s_signal /= '0') OR (cout_signal /= '0')) THEN
    test_OK <= '0';
  END IF;
  WAIT FOR 100 ns; -- 010
  IF ((s_signal /= '1') OR (cout_signal /= '0')) THEN
    test_OK <= '0';
  END IF;
  ....
END PROCESS test;
END arch_test_bench_type2;
```

Observe that as soon as a test sets `test_OK` to zero then it will stay at zero although following tests can be OK

We shouldn't run this simulation longer than the added WAIT times since the process will restart when it reaches its end and then the results will most likely be incorrect

## Testbenches cont.

Example cont.

Now over to [testbenchtype 3](#)

In this case we don't need any output signal either since the internal signals are used for our test and since these tests will give the written reports if something is wrong then we have an empty entity

```
ENTITY full_adder_tb3 IS
END full_adder_tb3;
```

We will rewrite the test process, that is replace the test\_OK process, but keep the rest of the architecture code

## Testbenches cont.

Example cont.

```
test_proc:PROCESS
BEGIN
    WAIT FOR 50 ns; -- 000
    ASSERT ((s_signal='0') AND (cout_signal = '0'))
    REPORT "000 50ns"
    SEVERITY warning;
    WAIT FOR 100 ns; -- 100
    ASSERT ((s_signal='1') AND (cout_signal = '0'))
    REPORT "100 150ns"
    SEVERITY warning;
    WAIT FOR 100 ns; -- 010
    ...
END PROCESS test_proc;
END arch_test_bench_type3;
```

If this condition is true then nothing is wrong with the signals so do nothing

The current simulation time and this text will be written to the simulators Transcript window if the output signals are incorrect

Continue for all eight combinations of input signals

## Testbenches cont.

Example cont.

If the **ASSERT** expression is true then the output signals have the correct values

If the expression is false then the test time and the **REPORT** message will be written to the simulators output window

We can have four different levels of **SEVERITY**

- **note**, the message will have the header Note
- **warning**, the message will have the header Warning
- **error**, the message will have the header Error
- **failure**, the message will have the header Failure

The severity levels are given in increasing order

The severity level should be chosen based on the kind of action the error calls for

The simulation continues

The simulation will stop at current time

Example cont.

The assert messages that you write can be simple or very detailed.

You decide!

For a more advanced design the test will be quite extensive and you need to write a lot of code just for the test

## Testbenches cont.


Example cont.

Once again we need a do file.

We're back to the same do file as the one we used for testbench 1 since we have no output.

```
-- full_adder_tb3.do

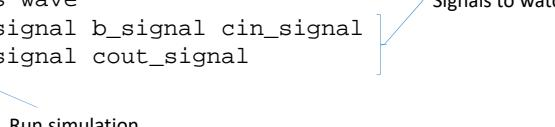restart -f -nowave
view signals wave
add wave a_signal b_signal cin_signal
Add wave s_signal cout_signal
run 730ns
```



Strictly we don't need to watch any signals since we have the assertions but like in test bench type 2 it is practical to keep the signals for debugging

## Test benches

### Clocks in test benches

We can create our clocks in the do file like before

```
force clk_tb 0 0,1 50ns -repeat 100ns
```

or create it in the test bench

```
clk_proc:PROCESS
BEGIN
    WAIT FOR 50 ns;
    clk_tb<=NOT(clk_tb);
END PROCESS clk_process;
```

Don't forget to set a start value for the clock signal

```
SIGNAL clk_tb:STD_LOGIC:='0';
```

In this case this is OK to do this since the signal value will only be used in simulation, not in synthesis