

DAT093

Introduction to Electronic System Design

Accessing a component from within a process

Sven Knutsson
svenk@chalmers.se
Dept. Of Computer Science and Engineering
Chalmers University of Technology
Gothenburg
Sweden

Introduction

We will look on how to use a component from a process.

Let's say that we want to use or earlier full adder from a clocked process.

The full adder is implemented as a block of hardware so it can not be placed within the process.

We must assign signals to the in- and outputs of the full adder and then assign values to these signals in the process.

Let's look at our code.

VHDL code

We have the entity

```
ENTITY component_from_process IS
  PORT(a:IN STD_LOGIC;
        b:IN STD_LOGIC;
        cin:IN STD_LOGIC;
        clk:IN STD_LOGIC;
        s:OUT STD_LOGIC;
        cout:OUT STD_LOGIC);
END component_from_process;
```

VHDL code cont.

And we have the setup part of our architecture

```
ARCHITECTURE arch_component_from_process OF
  component_from_process IS
```

```
  COMPONENT full_adder IS
    PORT(a:IN STD_LOGIC;
          b:IN STD_LOGIC;
          cin:IN STD_LOGIC;
          s:OUT STD_LOGIC;
          cout:OUT STD_LOGIC);
  END COMPONENT full_adder;
```

```
  SIGNAL a_comp_signal:STD_LOGIC;
  SIGNAL b_comp_signal:STD_LOGIC;
  SIGNAL cin_comp_signal:STD_LOGIC;
  SIGNAL s_comp_signal:STD_LOGIC;
  SIGNAL cout_comp_signal:STD_LOGIC;
```

```
BEGIN
```

```
  U0:COMPONENT full_adder
    PORT MAP(a=>a_comp_signal,
             b=>b_comp_signal,
             cin=>cin_comp_signal,
             s=>s_comp_signal,
             cout=>cout_comp_signal);
```

```
ENTITY component_from_process IS
  PORT(a:IN STD_LOGIC;
        b:IN STD_LOGIC;
        cin:IN STD_LOGIC;
        clk:IN STD_LOGIC;
        s:OUT STD_LOGIC;
        cout:OUT STD_LOGIC);
END component_from_process;
```

VHDL code cont.

And finally we have the process

```
full_adder_process:
PROCESS(clk)
BEGIN
    IF RISING_EDGE(clk) THEN
        a_comp_signal <= a;
        b_comp_signal <= b;
        cin_comp_signal <= cin;
        s <= s_comp_signal;
        cout <= cout_comp_signal;
    END IF;
END PROCESS full_adder_process;
```

```
ENTITY component_from_process IS
PORT(a:IN STD_LOGIC;
      b:IN STD_LOGIC;
      cin:IN STD_LOGIC;
      clk:IN STD_LOGIC;
      s:OUT STD_LOGIC;
      cout:OUT STD_LOGIC);
END component_from_process;

ARCHITECTURE arch_component_from_process OF
    component_from_process IS
    COMPONENT full_adder IS
        PORT(a:IN STD_LOGIC;
              b:IN STD_LOGIC;
              cin:IN STD_LOGIC;
              s:OUT STD_LOGIC;
              cout:OUT STD_LOGIC);
    END COMPONENT full_adder;

    SIGNAL a_comp_signal:STD_LOGIC;
    SIGNAL b_comp_signal:STD_LOGIC;
    SIGNAL cin_comp_signal:STD_LOGIC;
    SIGNAL s_comp_signal:STD_LOGIC;
    SIGNAL cout_comp_signal:STD_LOGIC;
BEGIN
    U0:COMPONENT full_adder
        PORT MAP(a=>a_comp_signal,
                 b=>b_comp_signal,
                 cin=>cin_comp_signal,
                 s=>s_comp_signal,
                 cout=>cout_comp_signal);
```

VHDL code cont.

Let's study the process

```
full_adder_process:
PROCESS(clk)
BEGIN
    IF RISING_EDGE(clk) THEN
        a_comp_signal <= a;
        b_comp_signal <= b;
        cin_comp_signal <= cin;
        s <= s_comp_signal;
        cout <= cout_comp_signal;
    END IF;
END PROCESS full_adder_process;
```


On each positive flank of our clock we will assign values to the full adder and read its outputs.

But the values we assign will not update the full adder until we reach the end of the process.

So what we read from the full adders outputs are actually related to the input values we assigned in the clock period **before** that.

VHDL code cont.

Let's look at the timing diagram

 

VHDL code cont.

Let's zoom in

We input values 2 Values 2 are written to the component

