

# On-chip filter implementations

DAT116, Dec 13 2018

[larssv@chalmers.se](mailto:larssv@chalmers.se)


# Why?

- Implementation insight helps understand limitations
  - True for all technologies, not only electronic circuits!
  - Switched-capacitor circuits and dual-rail signalling are ubiquitous in integrated filters
    - ... and in ADCs, DACs
    - Learn to recognize some simple forms

# Outline


- Basic switched-capacitor (SC) circuits
  - Some sources of performance limitations
  - A few examples
- Dual-rail signalling: benefits + drawbacks

# Discrete-time signals

 

Recap  
slide


$f_s = 32$

 

$$y = \sin(2\pi \cdot t), 0 < t \leq 1$$


$$y = \sin(2\pi \cdot t_k), t_k = (k / f_s)$$

# A switched capacitor

 

$$\Delta Q = (V_1 - V_0) C_s$$

# “Resistor”

 

- $\Delta Q = (V_0 - V_1) \cdot C_s$
- $I = \Delta Q \cdot f_s = (V_0 - V_1) \cdot f_s C_s$
- ... so, a “resistor” from  $V_0$  to  $V_1$ ;  $R = 1 / f_s C_s$
- Note:  $R$  controlled by  $f_s$  !

# HISTORY



If the condenser is now removed, and a resistance coil substituted for it, and adjusted till the steady current through the galvanometer produces the same deflexion as the succession of discharges, and if  $R$  is the resistance of the whole circuit when this is the case,

$$\frac{E}{R} = \frac{2BC}{T}; \quad (1)$$


or

$$R = \frac{T}{2C}. \quad (2)$$

[James Clerk Maxwell. A Treatise on Electricity and Magnetism. 1873.]



IC applications came later.

# Simple low-pass link

 

- Time constant given by  $R \cdot C_i = C_i / (f_s \cdot C_s)$
- Depends on
  - capacitance ratio (accurate)
  - frequency (accurate and controllable)


# Opamp circuits

  

- Integrator:  $V_{out} = - (C_i / C_{fb}) \cdot \int V_{in} dt$
- Inverting amplifier
  - Reset integrator after each cycle!
  - Gain:  $- C_i / C_{fb}$

Cf. resistor-based circuit:  
gain:  $- R_{fb} / R_i$


# Comparator

 



- Phase 1: switches 1 and 3 closed, switch 2 open
  - $V_{out}$ ,  $V_{in-}$  close to 0
  - $\sim V_A$  across  $C_i$
- Phase 2: switches 1 and 3 open, switch 2 closed
  - Still  $\sim V_A$  across  $C_i$
  - $V_{in-} \approx V_B - V_A$
  - $V_{out}$  swings to maximum or minimum voltage
 
# Non-idealities

- Significant sources of deviations from ideal behavior:
  - Stray capacitances
  - Charge injection
  - Offset voltages
  - Limited gain
  - Settling time





# Stray caps

  

[Maloberti, fig 6.28]


- Integrated capacitors suffer from stray capacitances
  - Asymmetrical (most from bottom plate)
  - Simple SC R still sensitive to top-plate stray capacitances!
  - Standard circuit solution exists
    - Bonus: switch control allows “free” signal inversion

# Charge injection

  


- Non-linear  $C_{stray}$  couples edge from  $V_{\emptyset}$  to  $V_{samp}$ 
  - Non-linear  $\rightarrow$  step depends on  $V_{samp}$ : distortion!
- Introduce bottom-plate sampling
  - Isolate charge on  $C_s$  with  $V_{\emptyset'}$  (no voltage dependence); then disconnect from  $V_{in}$  with  $V_{\emptyset}$

# Offset voltage

 


- Offset: voltage difference at inputs for  $V_{out} = 0$ 
  - Conventionally represented as voltage source in series with positive input
  - Small value (ideally =0), but worse with increasing circuit variations (theme 2!)
- Reset phase sets output, negative input to  $\approx V_{off}$ !
  - O/w,  $V_{off}$  would be amplified at output...


# Limited gain

 

- Negative input not pulled all the way to ground
  - Charge transfer incomplete
  - Output settles to “wrong” value
    - Worse with lower gain
  - Compare with CT case: discrepancy  $D = A\beta / (1 + A\beta)$

 


TPC 16. Open-Loop Gain vs.  
Frequency

 

- OP-amp with one dominant pole is first-order system
  - Step response is a damped exponential
  - Feedback moves pole!
  - Time constant  $\tau$  determines settling speed
    - $3 \cdot \tau$  to 95%;  $5 \cdot \tau$  to 99%;  $9 \cdot \tau$  to 99.9%; etc
  - Select GBW for desired accuracy (tradeoff: \$, W)

# Nonlinear settling (slewwing)

 

- Ideally, settling error shrinks exponentially with time
  - Remaining final error (%) at time  $t_x$  depends only on amplifier gain and on time spent vs pole position
- If **limited max current  $I_{out}$** , error also depends on level
  - Worse at high amplitudes! Non-linear! Distortion!


# How size capacitances?

- Small C brings high speed
- Small C brings low power
- Small C brings matching problems
  - Best matching for small-integer ratios (2, 3, 4, 5, etc)
  - Does not fit Butterworth etc. poles :-(
- Small C brings fundamental noise problems
  - Noise power:  $kT / C$

# SC drawbacks


- Sampling brings aliasing problems
  - Will need CT anti-alias pre-sampling filter
  - Need a GBW  $\sim 5x$  the clock frequency, so  $10x$  highest signal frequency
    - Worse than BW margin for continuous-time implementations
    - High GBW costs power!

# Example: SC ladder filter

 

- CT filter design styles re-usable in DT!

# Performance example

 


- 6-order filter, 176 MHz clock, < 100 mW, 0.35um CMOS

TABLE I  
SUMMARY OF THE MEASURED RESULTS OF THE OPAMP

Parameters	Results
Technology	0.35 $\mu$ m CMOS
Supply Voltage	3V
Low-Frequency Gain	56 dB
Unity-Gain Frequency	600 MHz
Phase Margin	50°
Power Consumption	30.8 mW
Single-Ended Output Swing	0.9 V <sub>PP</sub>
0.1% Settling Time @ 1.5pF	<5ns

Parameters	This design	J. Silva-Martinez [12]	R. F. Neves [13]
Technology	0.35- $\mu$ m CMOS	0.35- $\mu$ m CMOS	0.8- $\mu$ m CMOS
Supply voltage	3V	3V	5V
Power consumption	92.7 mW	54mW	125mW
Sampling frequency	176MHz	68MHz	100MHz
No. of Clock phases	3	4	42
Orders of filter	6	6	N/A
Q	7	32	7.5
Center frequency	44MHz	10.7MHz	37.5MHz
V <sub>in</sub> @ IM3 = 3%	0.893V <sub>p-p</sub>		N/A
Total output noise	383.0 $\mu$ V <sub>rms</sub>	N/A	N/A
Dynamic range ( 3% IM3)	58.3 dB	58 dB (SNR)	34dB SNDR with V <sub>out</sub> = 0dBm
Active area	0.52mm <sup>2</sup>	0.84mm <sup>2</sup>	7.27mm <sup>2</sup>

# Other SC circuits: DAC


 


# Dual-rail signalling

# Dual-rail signalling

- Almost universal in on-chip analog circuits
- Not only in DT filters
  - CT filters from theme 4!
- Increased complexity
  - Benefits outweigh costs
  - Often ignored for simpler drawings :-/

# What?

  

- Signals maintained as voltage differences
- Symmetrical circuits

# Dual-rail + and -

- 1. Twice the swing
- 2. Improved SNR
- 3. Common-mode coupled noise eliminated
- 4. Even-order harmonics cancel out

- 1. Twice the hardware
- 2. Twice the power
- 3. Relies on symmetry
- 4. CMFB circuitry needed

# 1. Twice the swing

- If single-rail swing from  $-1$  to  $+1$ , then dual-rail swing is from  $(-1) - (+1) = -2$  to  $(+1) - (-1) = 2$
- Important at low supply voltages in modern processes

## 2. Improved SNR

- Signal voltage amplitude doubled
  - Signal power up by 4x (6dB)
- Uncorrelated random noise at both rails adds as powers
  - Noise power up by 2x (3dB)
- 3dB SNR improvement!

# 3. Coupled-noise reduction

- Externally-generated noise (from supplies, substrate, capacitive coupling) tends to be highly correlated
- If identical (ideal case), does not affect output at all!
- Even better SNR improvement

# 4. Harmonic reduction

- Even-order nonlinearities are cancelled
- Consider DR circuit with slight nonlinearity  $h$
- Inputs:  $x_+ = a \sin(\omega t)$  ;  $x_- = -a \sin(\omega t)$
- Outputs:  $y_+ = h(a \sin(\omega t))$  ;  $y_- = h(-a \sin(\omega t))$
- Taylor expansion:  $h(x) = h_0 + h_1 x + h_2 x^2 + \dots$
- But  $x^{2n} = (-x)^{2n}$ , so no even harmonics in  $(y_+ - y_-)$

# 1. Twice the hardware

- Twice as many capacitors
- Twice as many switches
- Twice as many wires
- ...
- Affordable with present-day miniaturization


## 2. Twice the power

- Twice the capacitive load driven to the same swing as before
- Twice the number of switches to control
- May be traded for the 3dB SNR improvement...

### 3. Relies on symmetry

- Benefits assume that all paths are symmetrical!
  - Example: harmonics won't cancel perfectly if one capacitive load is larger!
  - Symmetry is never perfect
    - Layouts
    - Variability

## 4. CMFB circuits needed

 



# Non-standard schematic symbol

- Common-mode feedback circuits needed to control average output voltages
  - Extra input (here) or added to both DM inputs
  - Extra feedback loop! Stability issue!

# Two combined examples


# Successive approximation

Recap  
slide

  


- Simple Finite State Machine sets bits in sequence from MSB downwards, depending on previous decisions
  - Search by interval halving / bisection
  - One full conversion in  $N$  cycles
- + No subtractions or other analog processing
- DAC needs to be good to  $N$  bits!

# DAC + comparator

 

- DAC capacitors also work as ADC sample cap!
- Capture value on caps, then switch back plates to zero out difference by binary scaling
- Principle used for lowest-FoM ADCs today!
  - Also for high speed (next week!)

# Forward-looking example

 

- Two-integrator filter
- Part of Sigma-Delta ADC (also next week!)

[Pavan, Schreier, Temes: Understanding Delta-Sigma Data Converters, 2017]

# Summary

- SC circuits allow high-performance analog circuits on silicon
  - Good accuracy
  - Controllability
- Dual-rail signalling ubiquitous in on-chip analog and mixed-signal circuits
  - May be used even if not shown in schematics!