 


2017-09-11 Example of ILA design before prelab 2


An equal circuit implemented as an iterative logic array (ILA)

A	B	EQ _{in}	EQ _{out}
0	0	0	0
0	1	0	0
1	0	0	0
1	1	0	0
0	0	1	1
0	1	1	0
1	0	1	0
1	1	1	1

Karnaugh diagram



 We need an inverter to generate $\overline{EQ_{in}}$




2

Note that we can also implement

$\overline{EQ_{out}}$

	AB			
	00	01	11	10
EQ_{in} 0	1	1	1	1
1	0	1	0	1

the corresponding circuit diagram is

 


We need an inverter here too!


Which solution is better?

③

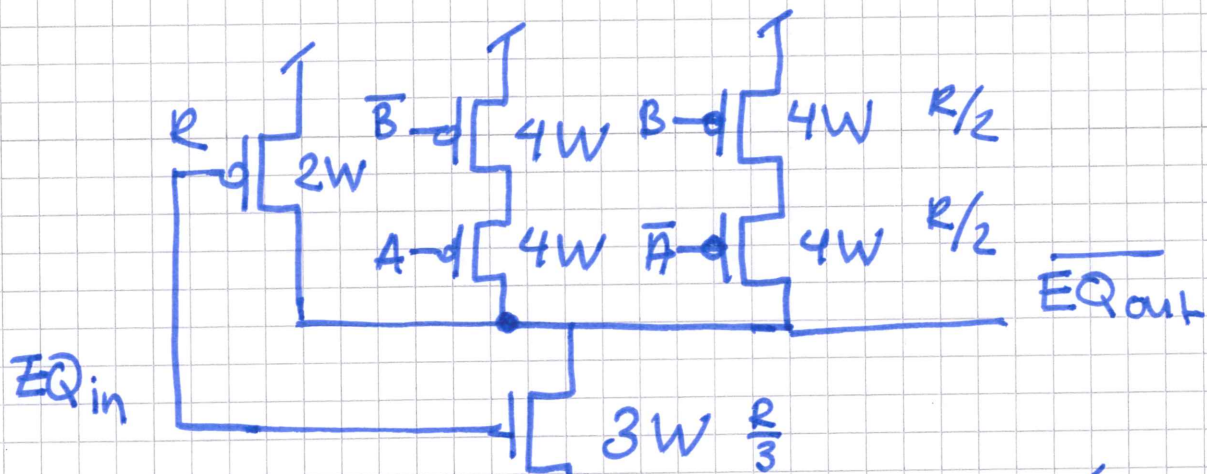The second solution is better due to fewer PMOS transistors in series



 scaling
for same
worst-case
resistance $\Rightarrow$
as for inverter



$$g_{EQ_{IN}} = \frac{2C + 3C}{3C} = \frac{5}{3}$$


$$P_{EQ} = \frac{2C + 4C + 4C + 3C}{3C} \cdot p_{inv} = \frac{13}{3} p_{inv}$$

for completeness

$$g_{A, B, \bar{A}, \bar{B}} = \frac{4C + 3C}{3C} = \frac{7}{3}$$

(4)

calculate delay with given scaling

 

$$p = \frac{13}{3} p_{inv}$$

$$p = p_{inv}$$

$$h = ? \frac{C_{in}}{2C_{in}} = \frac{1}{2}$$

$$h = ? \frac{2C_{in}}{C_{in}} = 2$$

normalized delay $d = g \cdot h + p$

$$\frac{5}{3} \cdot \frac{1}{2} + \frac{13}{3} p_{inv} + 1 \cdot 2 + p_{inv} =$$

$$\frac{5}{6} + \frac{13}{3} p_{inv} + 2 + p_{inv}$$

$$= \boxed{2 \frac{5}{6} + 5 \frac{2}{3} p_{inv}}$$