 


Lecture 2

The MOSFET

The MOSFET as a switch


In the digital world, the MOSFET is a switch that is either **ON** with a conductance $G_{ON} > 0$, or **OFF** with no conductance, $G_{OFF} = 0$



For now we have assumed that $R_{ON} = 0$, but today we'll learn more about this

The MOSFET as a switch

 In the digital world, the MOSFET is a switch that is either **ON** with a conductance $G_{ON} > 0$, or **OFF** with no conductance, $G_{OFF} = 0$




For now we have assumed that $R_{ON}=0$, but today we'll learn more about this

ON/OFF piecewise linear MOSFET model

The piece-wise linear model based on two parameters (G_{ON} and I_{DSAT}) is our backbone model

Why current saturation?

 Current saturation is a combination of drain end charge $\rightarrow 0$, and charge-carrier velocity saturation



$$I_{DS} = \begin{cases} 0 & \text{OFF } V_{GS} < V_T \\ G_{ON} V_{DS} & \text{ON linear} \\ I_{DSAT} & \text{ON saturated} \end{cases}$$

Why piecewise linear model?


- + Simple
- + Focus on important behavior
- + Asymptotically correct
- Poor transition region model
- Derivative not continuous

The MOSFET is a square-law device

The piece-wise linear model based on two parameters (G_{ON} and I_{DSAT}) is our backbone model

Why current saturation?

 Current saturation is a combination of drain end charge $\rightarrow 0$, and charge-carrier velocity saturation



$$I_{DS} = \begin{cases} 0 & \text{OFF } V_{GS} < V_T \\ G_{ON} V_{DS} & \text{ON linear} \\ I_{DSAT} & \text{ON saturated} \end{cases}$$

$$I_{DSAT} = \frac{k}{2} (V_{GS} - V_T)^2$$



$$G_{ON} = k (V_{GS} - V_T)$$

Classic square-law MOSFET model

The piece-wise linear model based on two parameters (G_{ON} and I_{DSAT}) is our backbone model

Why current saturation?

  Current saturation is a combination of drain end charge $\rightarrow 0$, and charge-carrier velocity saturation



$$I_{DS} = \begin{cases} 0 & \text{OFF } V_{GS} < V_T \\ G_{ON} V_{DS} \left(1 - \frac{V_{DS}}{2V_{DSAT}} \right) & \text{ON linear} \\ I_{DSAT} & \text{ON saturated} \end{cases}$$

$$I_{DSAT} = \frac{k}{2} (V_{GS} - V_T)^2$$



$$G_{ON} = k (V_{GS} - V_T)$$

Classic square-law MOSFET model

The piece-wise linear model based on two parameters (G_{ON} and I_{DSAT}) is our backbone model

Why current saturation?

  Current saturation is a combination of drain end charge $\rightarrow 0$, and charge-carrier velocity saturation



$$I_{DS} = \begin{cases} 0 & \text{OFF } V_{GS} < V_T \\ G_{ON} V_{DS} \left(1 - \frac{V_{DS}}{2V_{DSAT}} \right) & \text{ON linear} \\ I_{DSAT} & \text{ON saturated} \end{cases}$$

$$I_{DSAT} = \frac{k}{2} (V_{GS} - V_T)^2$$


$$G_{ON} = k (V_{GS} - V_T)$$

$$\text{Define } V_{GT} = V_{GS} - V_T$$

MOSFET models can predict I_{DS} for any V_{GS}/V_{DS}


Focus on
saturated
region

 Blue and red
regions tell us
when to be alert
for errors in using
saturation model



$$V_{DS} = V_{GS} - V_T = V_{GT}$$

 
I_{DS} can be plotted in 3D vs. V_{GS} & V_{DS}



Piecewise linear MOSFET model is actually closer to modern short-channel MOSFET behavior

Focus on saturated region

 
Blue and red regions tell us when to be alert for errors in using saturation model




$$V_{DS} = \frac{V_{GS} - V_T}{2} = \frac{V_{GT}}{2}$$

Electrical two-port MOSFET model

FOCUS ON THE SATURATED MOSFET

 


Electrical relay two-port model

 


Some slides on MOSFET theory

- To find out how G_{ON} depends on geometry and voltages we need a little theoretical discussion
- MOSFETs are field effect transistors, i.e. FETs, which means that the ON/OFF function is a capacitive effect
- Capacitor charge = capacitance * voltage: $Q=CV$
- Parallel plate capacitance per unit area $C=\epsilon/\text{thickness}$, where ϵ is the permittivity of the insulator. In a MOSFET $\epsilon_{ox}=4\epsilon_0$

 


MOSFET geometry

MOSFET top view

 


MOSFET cross sectional view

 

The n-channel MOSFET


MOSFET theory – no gate voltage applied

MOSFET switch model

 

MOSFET switch is OFF


MOSFET cross sectional view

 

The n-channel MOSFET

MOSFET theory – applying a gate voltage

MOSFET switch model

 


MOSFET switch is leaky

The threshold voltage V_T is the gate voltage needed to form the isolation layer

V_D

MOSFET cross sectional view

 


The n-channel MOSFET

MOSFET theory – applying a gate voltage


MOSFET switch model

MOSFET switch is ON

 

The threshold voltage V_T is the gate voltage needed to form the isolation layer

MOSFET cross sectional view

 


The n-channel MOSFET

For $V_G > V_T$ a channel of mobile electrons is formed between the source and drain

MOSFET theory – applying a gate voltage

MOSFET switch model

MOSFET switch is ON

 


A parallel-plate capacitor
between gate and channel
MOS means

Metal-oxide-semiconductor

Hence, a MOS capacitor

Capacitor formula $Q = C \cdot V$

 

The threshold voltage V_T is the gate voltage needed to form the inversion layer

For $V_G > V_T$ a channel of mobile electrons is formed between the source and drain

$$Q_{channel} = W C_{ox} (V_{GS} - V_T)$$

W is MOSFET channel width
 C_{ox} is gate capacitance per unit area


MOSFET theory – applying a drain voltage

- The drain to source voltage creates an electric field that gives the mobile electrons in the channel at the silicon surface a drift velocity

$$v_{channel} = \mu \frac{V_{DS}}{L}$$

μ is electron mobility
 $E = V_{DS}/L$ is electric field

MOSFET cross sectional
 view

 

$V_D \neq 0$ but still considered small

For $V_G > V_T$ a channel of mobile electrons is formed between the source and drain

$$Q_{channel} = WC_{ox} (V_{GS} - V_T)$$


W is MOSFET channel width
 C_{ox} is gate capacitance per unit area

Determining the ON-conductance G_{ON}

- Current is number of charges that pass per unit time
- i.e. Current = charge per unit length x velocity
- Therefore, $I_{DS} = WC_{ox}(V_{GS} - V_T) \times \mu \frac{V_{DS}}{L}$
- Rewrite $I_{DS} = \frac{W}{L} \mu C_{ox} (V_{GS} - V_T) V_{DS} = G_{ON} V_{DS} \Rightarrow G_{ON} = \frac{W}{L} \mu C_{ox} (V_{GS} - V_T)$
- L is the channel length, i.e. distance between source and drain

MOSFET theory – forcing MOSFET into saturation

 
- When the drain voltage increases the MOSFET approaches saturation and enters saturation when $V_{DS} = V_{GS} - V_T$
- Charge injected at source $Q_{source} = WC_{ox} (V_{GS} - V_T)$
- Maximum charge velocity at source: $v_{source} = \mu \frac{V_{GS} - V_T}{2L}$



MOSFET theory – forcing MOSFET into saturation


- When the drain voltage increases the MOSFET approaches saturation and enters saturation when $V_{DS} = V_{GS} - V_T$

 - Saturation current:
$$I_{DS} = \frac{1}{2} \frac{W}{L} \mu C_{ox} (V_{GS} - V_T)^2$$



It is like cars on a motorway

 - Cars entering motorway at 10 km/h and exits at 100 km/h.
- Flow rate of cars is constant: one exit for each entry



How abrupt is the turn-off at V_T ?


- Is there no current at all below the threshold?

How abrupt is the turn-off at V_T ?

- Is there no current at all below the threshold?



- Finding a sub- V_T model
 
$$I_{DS,sub-VT} = I_{OFF} e^{V_{GS}/nV_{th}}$$



The MOSFET in detail

  - A number of textbooks treat MOSFET models in great detail, including their physical background and shortcomings due to short-channel effects in nanoscale devices



BSIM4v4.7 MOSFET Model

-User's Manual

Tanvir Hasan Morshed, Darsen D. Lu, Wenwei (Morgan) Yang, Mohan V. Dunga, Xuemei (Jane) Xi, Jin He,

Weidong Liu, Kanyu, M. Cao, Xiaodong Jin, Jeff J. Ou, Mansun Chan,

All M. Niknejad, Chenming Hu

Department of Electrical Engineering and Computer Sciences
University of California, Berkeley, CA 94720

BSIM4v4.7 Manual Copyright © 2011 UC Berkeley


Summary

- The MOSFET is treated as an electrically controlled ON/OFF switch.
- The input gate voltage is referred to the source, hence V_{GS} .
- The output drain voltage is also referred to the source, hence V_{DS} .
- The MOSFET current is a function of both voltages, V_{GS} and V_{DS} .
- The ON MOSFET behaves like a resistor R_{ON} in the linear region, and like a constant-current source I_{DSAT} in the saturation region.
- First-order model of the saturation current is a square-law model.
- In an OFF MOSFET there is a subthreshold leakage current, I_{SUB} .
- Use color-coding in red, blue, and green to separate the three regions of MOSFET operation
 - Useful when deriving the static properties of the CMOS inverter.
- Focus on MOSFET as a saturated device


Lecture 2b

The MOSFET
Dynamic properties
(Capacitances)


Saturated MOSFET model

 

Saturated MOSFET model

 


MOSFET gate capacitance

 


The gate capacitance C_G , causing the field effect is considered a parallel-plate capacitor: $C_G = WLC_{ox}$
i.e. (the red gate area) x (the oxide capacitance C_{ox} per unit area)
In a 65 nm CMOS process, typically $C_{ox} = 20 \text{ fF}/\mu\text{m}^2$

Source/drain parasitic capacitances

 

The parasitic source and drain capacitances, C_S and C_D respectively, can be calculated as a sum of the bottom plate capacitance C_{bottom} and the sidewall capacitances $C_{sidewall}$ where the sidewall to the channel and the sidewalls to the shallow trench isolations (STIs) are to be treated differently.

65 nm CMOS capacitances

 

Gate oxide capacitance per unit area $C_{ox} \approx 20 \text{ fF}/\mu\text{m}^2$
(corresponds to 1.2 nm effective oxide thickness, EOT)

Gate capacitance $C_G = C_{ox} * 60 \text{ nm}$ per micron channel width
(For different reasons the channel length in this 65 nm CMOS process is only 60 nm, so we have used $L = 60 \text{ nm}$)

For our calculations: $C_G = 1.2 \text{ fF}/\mu\text{m}$

The parasitic drain/source capacitances are of the same order of magnitude as the gate capacitance, $C_S = C_D = p_{inv} C_G$

Generic approach: use $p_{inv} = 1$ to avoid detailed calculations
(We leave the detailed calculations to the circuit simulator)

Conclusion

In this lecture, we started considering MOSFET static properties

- Three regions of operation
 - Two ON regions: linear or saturated
 - One OFF region: subthreshold

In second half of lecture we also considered dynamic properties

- The intrinsic gate capacitance
- The extrinsic, or parasitic drain capacitance

We came up with a final two-port model including both static circuit elements (current-source), and dynamic elements, i.e. capacitances!