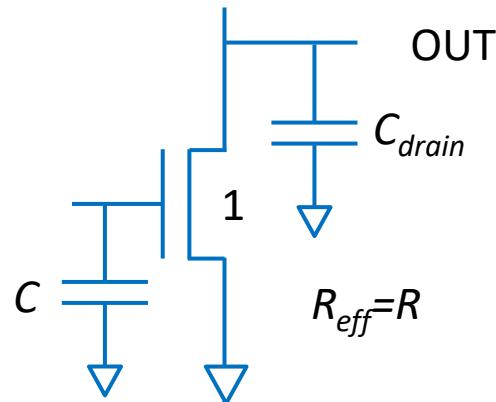


Q & A session


Lecture 5

Transistor sizing

If these are the R and C parameters of the unit width n-channel MOSFET . . .



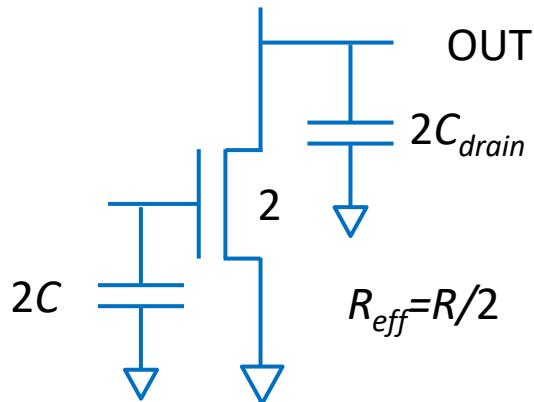. . . what would be the R and C parameters of a 2 unit width n-channel MOSFET?




The unit width is just arbitrarily chosen, but for any width W , the MOSFET gate capacitance and its effective resistance can be calculated as shown below

$$R_{eff} = \frac{2}{W} \frac{[k\Omega \times \mu m]}{[\mu m]}, \quad C_{gate} = 1.2 \times W \quad [fF/\mu m] \times [\mu m], \quad C_{drain} = p_{inv} C_{gate}$$


CMOS inverter –Transistor sizing

Q: What if the MOSFET is a p-channel device?

 The R and C parameters of the unit width p-channel MOSFET



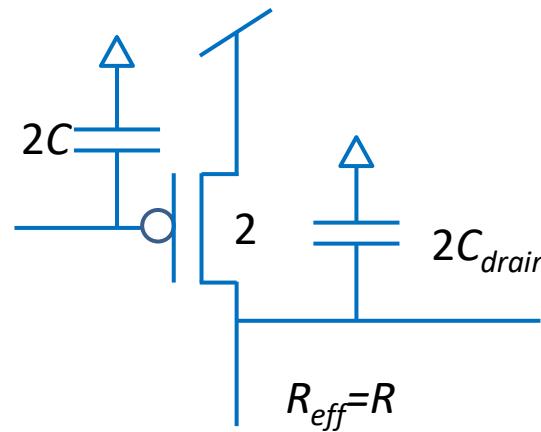
The R and C parameters of the 2 unit width p-channel MOSFET



The higher effective resistance is because of the hole mobility in the p-channel being only half of that of the electron mobility in the n-channel.


The 2 unit width p-channel device has the same effective resistance as the 1 unit width n-channel device, but twice its capacitances.

So, this is our reference CMOS inverter

 


Size X	WN [nm]	WP [nm]
2	200	400
3	280	560
4	370	740
5	510	1020
8	720	1440
10	1000	2000

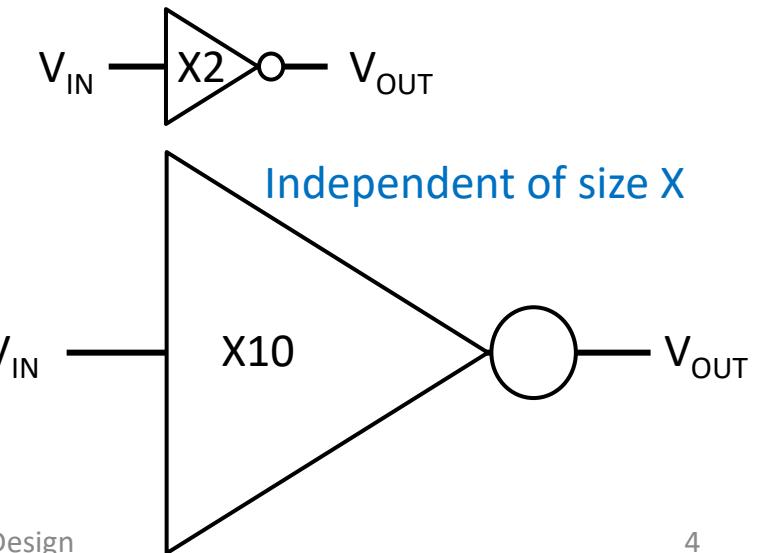All inverters in cell library
have $WP/WN=2$



How to size MOSFETs in a logic gate

 Now we want to apply the same model to any CMOS logic gate




In a logic gate, the pull-up and pull-down networks may have many different resistive paths from the output to the VDD and VSS rails, respectively.

Q: Why do we want all resistive paths to have the same effective resistance?

A: Because it makes life simpler! Just one number to keep track of.

Let the EDA tools keep track of more detailed approaches!

A logic gate example: the AOI22 gate

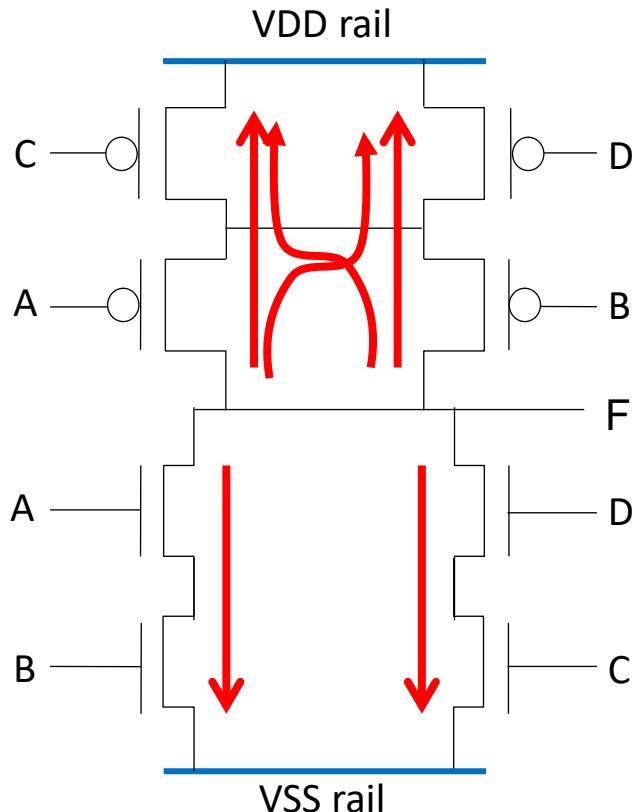

The AOI22 gate has two pull-down paths to VSS and four pull-up paths to VDD.

The **worst case** propagation delay occurs when only **one** path connects the output to a rail.


When two or more paths are ON, charging/discharging the load capacitor through parallel paths will be faster.

These cases will not be the speed limiting cases potentially violating the timing constraints.

Q: Which input combinations lead to more than one conducting path?

A: This can be deduced from the Boolean truth table. Obviously $A=B=C=D=1$ opens up 2 paths to ground. 3 or 4 zero inputs will open up two or more conducting paths to VDD.

A logic gate example: the AOI22 gate

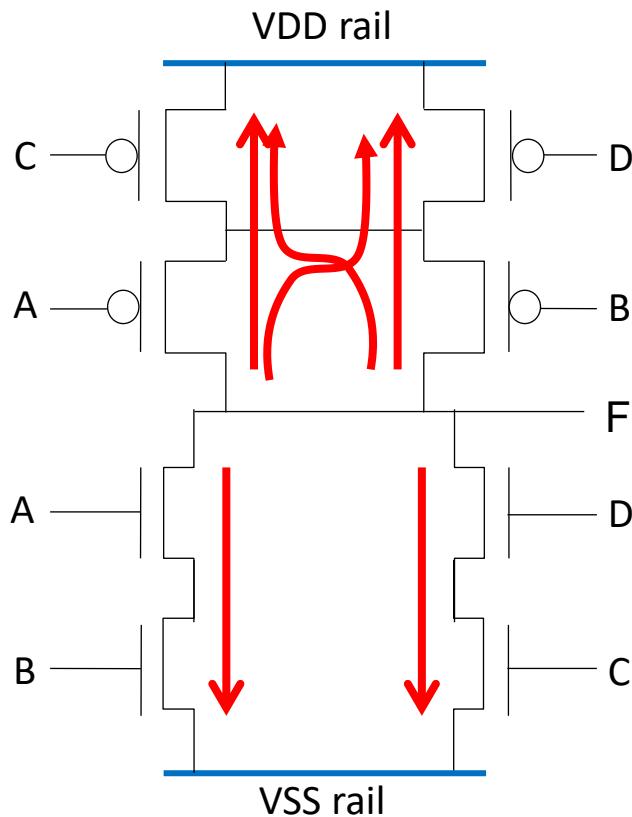


A	B	C	D	OUT	# ON paths
0	0	0	0	1	4↑
0	0	0	1	1	2↑
0	0	1	0	1	2↑
0	0	1	1	0	1↓
0	1	0	0	1	2↑
0	1	0	1	1	1↑
0	1	1	0	1	1↑
0	1	1	1	0	1↓
1	0	0	0	1	2↑
1	0	0	1	1	1↑
1	0	1	0	1	1↑
1	0	1	1	0	1↓
1	1	0	0	0	1↓
1	1	0	1	0	1↓
1	1	1	0	0	1↓
1	1	1	1	0	2↓

Q: Which input combinations lead to more than one conducting path?


A: This can be deduced from the Boolean truth table. Obviously $A=B=C=D=1$ leads to 2 paths to ground. 3 or 4 zero inputs lead to 2 or more conducting paths to VDD.

Exercise:

Calculate NAND2 NOR2 logical efforts

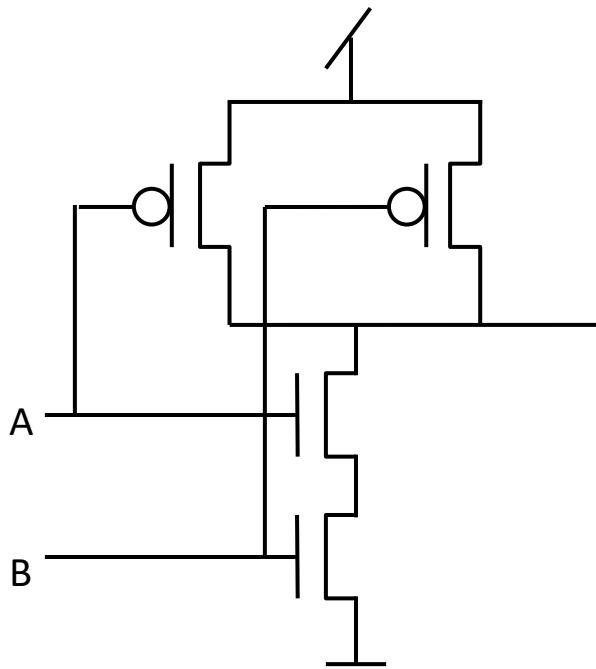


NAND2
Show that $g=4/3$, and $p=2p_{inv}$

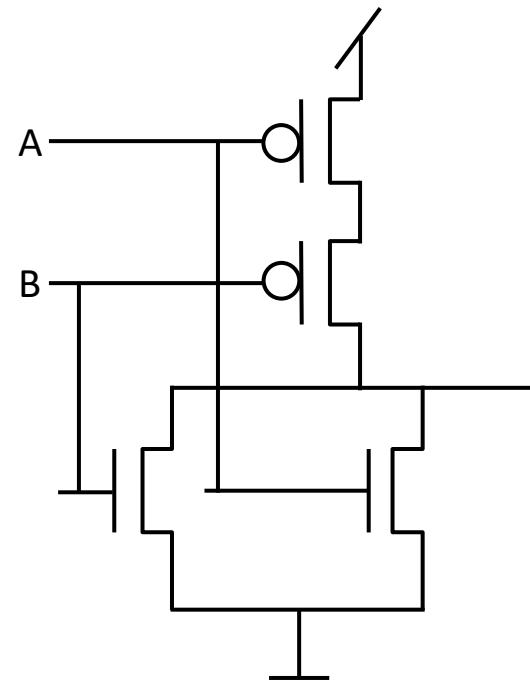

NOR2
Show that $g=5/3$, and $p=2p_{inv}$


Exercise:

Calculate NAND3 & NOR3 logical efforts

 

NAND3


Show that $g=5/3$, and $p=3p_{inv}$

 

NOR3

Show that $g=7/3$, and $p=3p_{inv}$

Consider the NAND2 logical gate

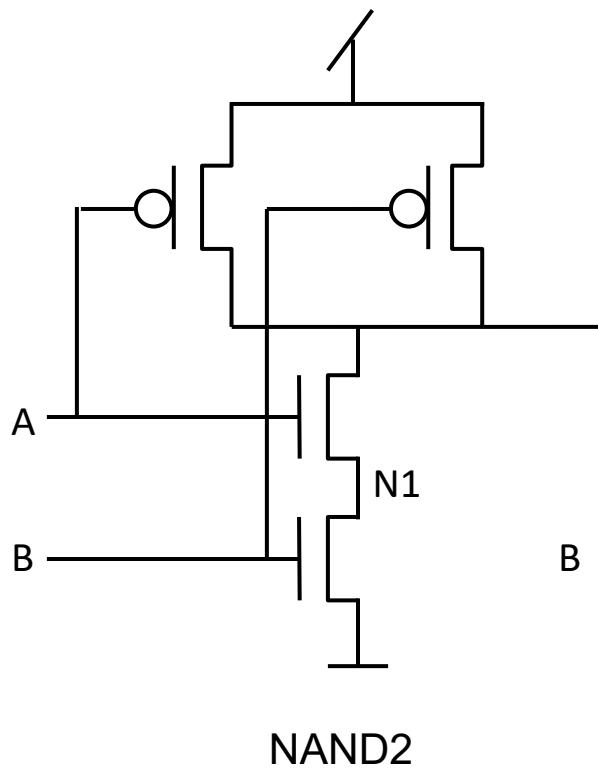

Q: Does it make any difference to the switching properties of the NAND2 gate that the source of the A-input n-channel device is not connected to ground?

A: Interesting question. Actually it does. Consider the case when $A=1$ and $B=0$. Both the output and N1 nodes are then at VDD.

The node N1 voltage not being at GND actually increases the threshold voltage of the A-input n-channel device, thereby increasing its effective resistance and making it a bottleneck device once B goes high.

Therefore it is better to arrange inputs so that the B-input goes high before the A input.

When $A=0$ and $B=1$, the N1 node is being discharged to GND. Thereby the threshold voltage of the A-input MOSFET is not affected. Furthermore, node N1 is already discharged when the A-input goes high!

VT modulation

- The effect that the MOSFET source potential not being at GND affects the threshold voltage is called VT-modulation.
- Why do I tell you about this?
- Because it is going to be important in your carry cell design!
- When you add two bits, a and b, considering an incoming carry from less significant bits, which is the order of signal arrival? Should be considered while designing your cell for the course lab series!

- Design task:

