

Lab 2 Summary


Carry cell design

Prelab 2


- Design task: design with MOSFETs the carry bit-cell for an 8-bit ripple-carry adder!
- The 8-bit carry logic is to be implemented by an iterative logic array consisting of eight instances of the bit-cell that you have designed.
- The carry bit-cell has three inputs (two bits a , b and a carry-in memory bit), and one output, the carry-out memory bit to the next more significant bit.

Iterative logic arrays: FULL ADDDER

Find Boolean equations
from truth table!

 


BOOLEAN TRUTHTABLE				
A	B	CIN	COUT	SUM
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

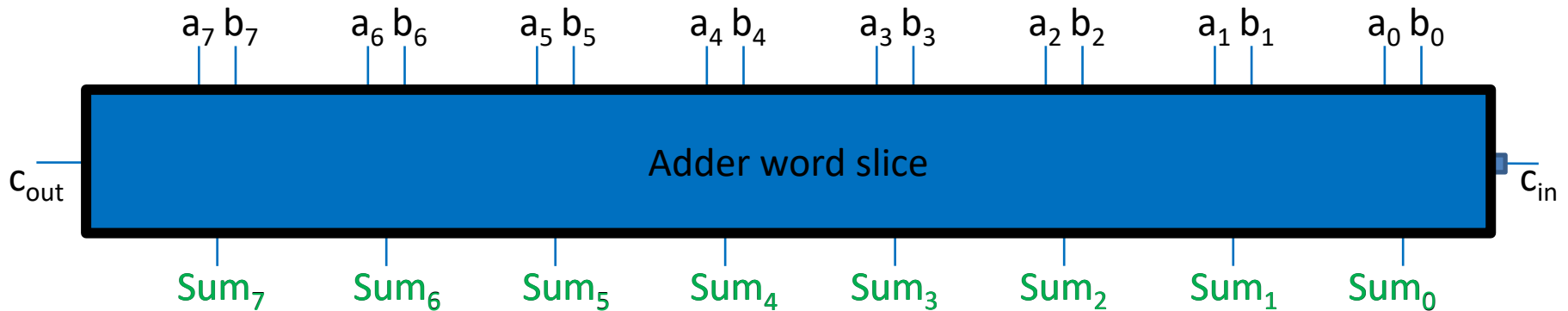


Iterative logic arrays: FULL ADDER

Find Boolean equations from truth table!

 


BOOLEAN TRUTH TABLE			LOGIC FORMULAS			
A	B	CIN	COUT	SUM	COUT	SUM
0	0	0	0	0	=OR(AND(A;B;CIN);	
0	0	1	0	1	AND(NOT(COUT);OR(A;B;CIN)))	*1
0	1	0	0	1	0	1
0	1	1	1	0	1	0
1	0	0	0	1	0	1
1	0	1	1	0	1	0
1	1	0	1	0	1	0
1	1	1	1	1	1	1

Design full adder by divide and conquer

 

Iterative logic arrays: FULL ADDER

Find Boolean equations from truth table!

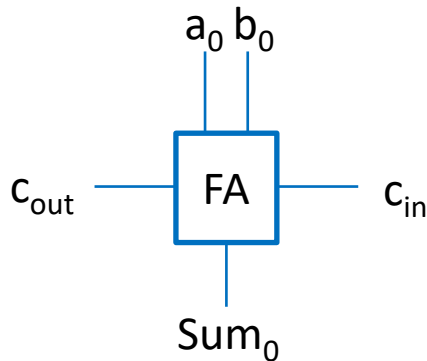

Propagation delay estimation:

Assume carry cell has logical effort g and parasitic delay p .


8-bit adder delay: A first crude estimate!

$$d=8*(p+g*2+p_{inv}+1/2)\approx 8*10=80 \rightarrow t_{pd}=400 \text{ ps}$$

Corresponding to 1.25 GHz clock frequency


But load from SUM cell was neglected and will slow down the design!

 Design 8-bit full adder as an iterative logic array!




Designing the carry cell

 
$$\overline{C_{OUT}} = (\overline{A} + \overline{B})(\overline{C_{IN}} + \overline{AB}) = \overline{AB} + \overline{C_{IN}}(\overline{A} + \overline{B})$$




$$Y = (A+B)C_{IN} + AB$$

 

Designing the carry cell


 


$$Y = (A+B)C_{IN} + AB$$

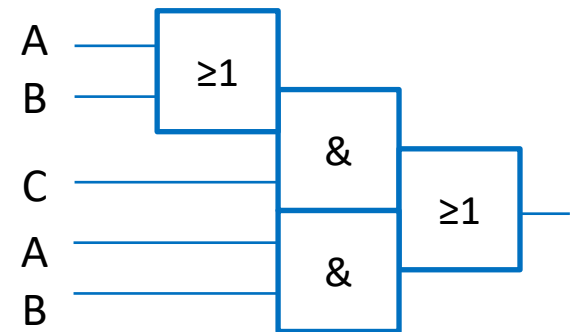


Designing the carry cell
  
$$\overline{C_{OUT}} = (\overline{A} + \overline{B})(\overline{C_{IN}} + \overline{AB}) = \overline{AB} + \overline{C_{IN}}(\overline{A} + \overline{B})$$




Designing the carry cell
 
$$\overline{C_{OUT}} = (\overline{A} + \overline{B})(\overline{C_{IN}} + \overline{AB}) = \overline{AB} + \overline{C_{IN}}(\overline{A} + \overline{B})$$



$$C_{OUT} = AB + C_{IN}(A + B)$$


 
Logical effort $g=2$,
Parasitic delay $p=4$





8-bit adder delay: Improved estimate!

$$d = 8 * (p + g * 2 + p_{inv} + 1/2) \approx 8 * (4 + 2 * 2 + 1.3) = 74.4 \rightarrow t_{pd} = 372 \text{ ps}$$

2015 hand-in examples

  


2015 hand-in examples

  


Design structure chosen by a number of 2015 students!


2017 hand-in example

 


2017 hand-in example

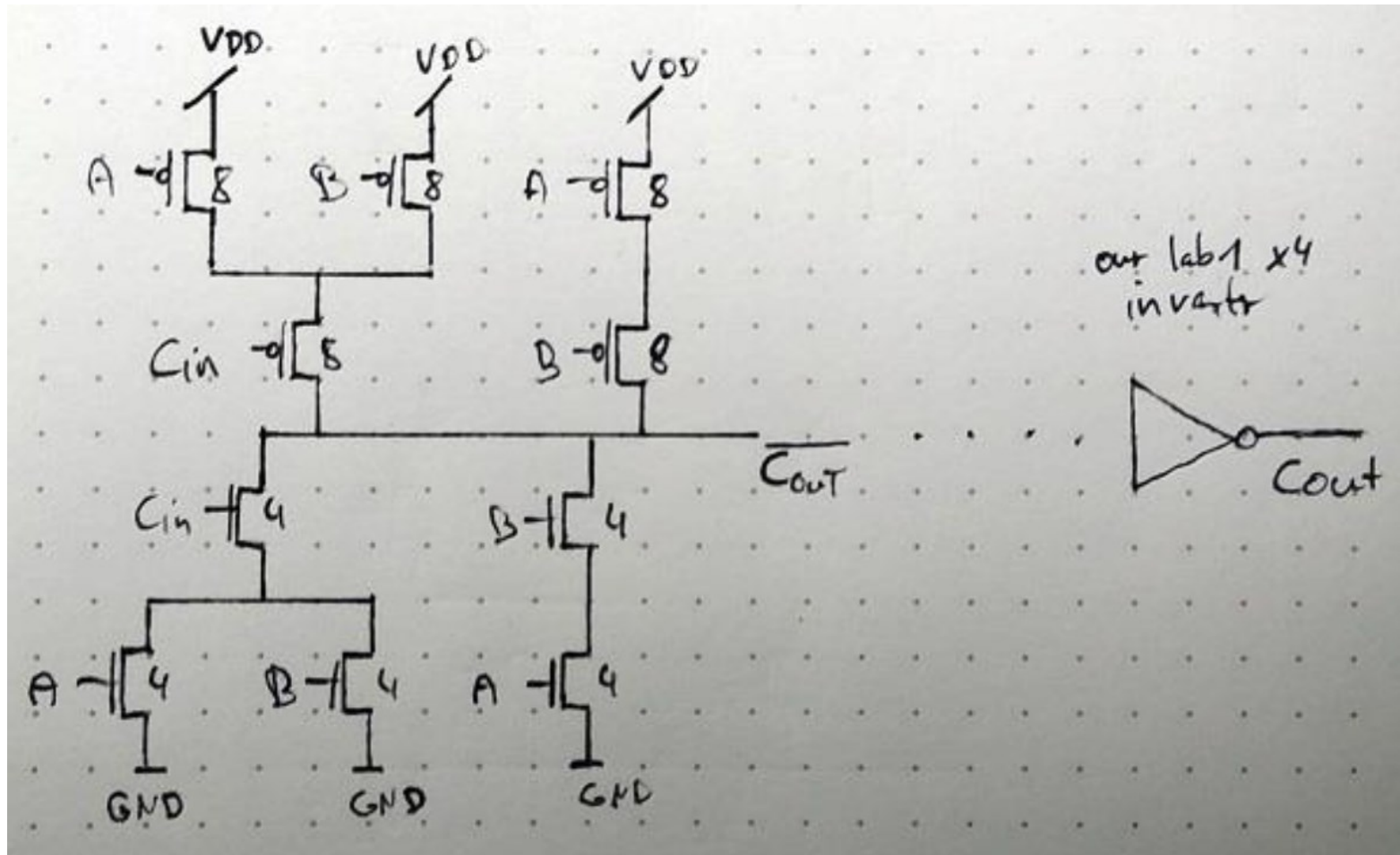

Textbook solution

 

 
Design structure as proposed in textbook!



Textbook solution

CARRY DELAY (CIN input)
 
$$d = 4 + 2 \times (6 + 12) / 6 + 1 + (6 + 6 + 6) / 12 = 4 + 6 + 1 + 1.5 = 12.5$$



CARRY LOGIC

(C input)

$$g = (2 + 4) / 3 = 2$$

$$p = 2 \times (2 + 4) / 3 = 4$$


8-bit adder delay: Consider also SUM cell load

$$d = 8 * (p + g * (2 + 4) / 2 + p_{inv} + 3 * 2 / 4) \approx 8 * (4 + 2 * 3 + 2.5) = 100$$

$$\rightarrow t_{pd} = 500 \text{ ps}$$

Textbook solution


What if we resize
MOSFETs in SUM cell?

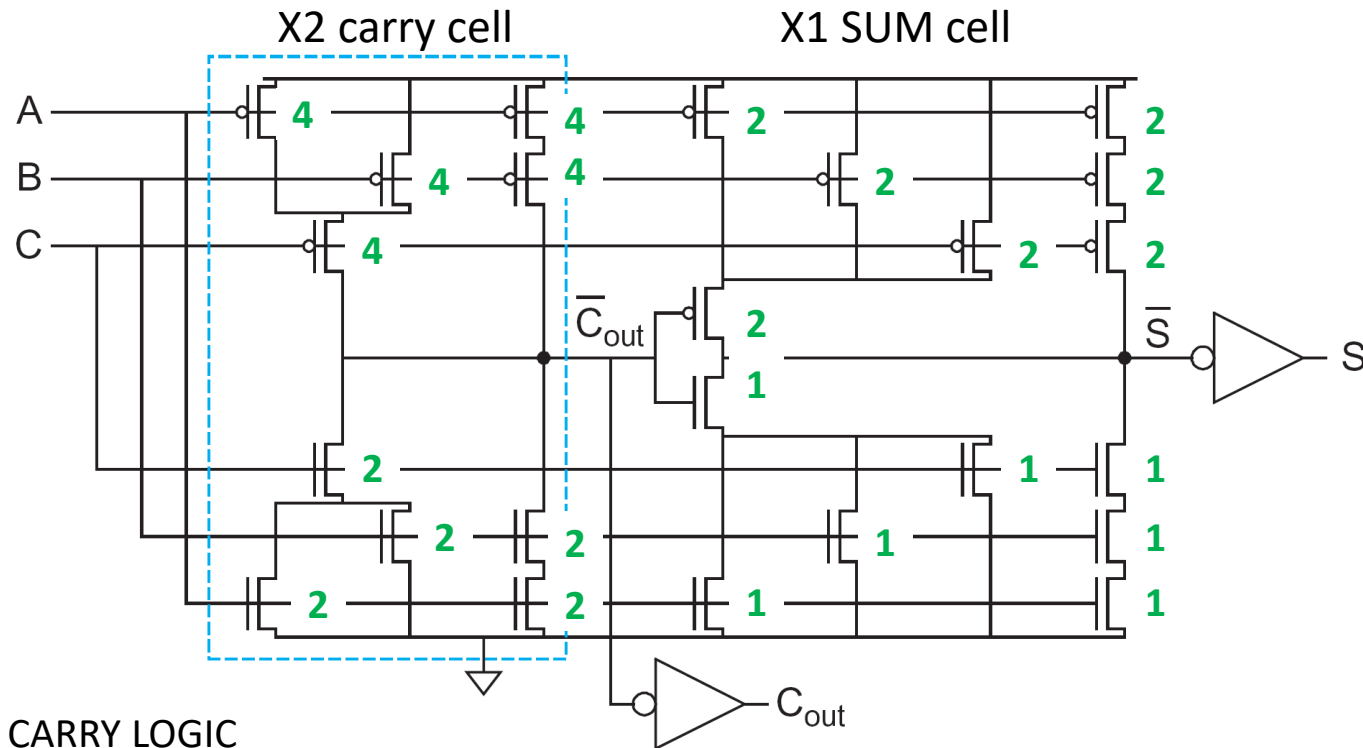

CARRY LOGIC
(C input)
 $g = (2+4)/3 = 2$
 $p = 2 \times (2+4)/3 = 4$

8-bit adder delay: Consider also SUM cell load
 $d = 8 \times (4 + 2 \times (1+2)/2 + 1 + (2+1+1)) = 8 \times (4+3+1) = 8 \times 10 = 80$
 $\rightarrow t_{pd} = 400 \text{ ps}$

What if we resize MOSFETs in SUM cell?

 


X2
↑
Which size is optimal? X2? X4?

Textbook solution

CARRY DELAY (CIN input)

 What if we resize the MOSFETs as shown in red, what is the parasitic delay, p , now?



CARRY LOGIC
(C input)

$$g = (2+4)/3 = 2$$

$$p = (2+4+2+1)/3 = 3$$

CARRY DELAY (C input)

$$d = 3 + 2 \times (1+2)/2 + 1 + (2+1+1)/2 = 3 + 3 + 1 + 2 = 9 \text{ units/stage}$$

$$\rightarrow t_{pd} = 360 \text{ ps}$$

The End

Q & A session!