

Lecture 1

Course subject intro

Designing CMOS gates

2018-09-04

Lecture outline

- CMOS design overview
- Skills developed and knowledge gained from the course
 - Tool handling skills: Cadence Electronic Design Automation (EDA)
 - Theoretical insights –pre-design estimations with pencil on paper
- The design flow – textbook MIPS example
- Iterative Logic Arrays (ILAs)
- Adder designs – custom design vs. synthesis from VHDL
- CMOS Fabrication
- Designing CMOS logic gates using MOSFET switches
- Exercises and
- Summary

Design flow


 



FIGURE 1.70 Design and verification sequence

DRC = Design Rule Checker

LVS = Layout Versus Schematic

 

Gajski Y-chart

 

Block Diagram (textbook MIPS example)



 


FIGURE 1.56 Top-level MIPS block diagram

Floor planning

 

MIPS Layout

 

Datapath layout


 


FIGURE 1.67 MIPS datapath layout


Bitslices form iterative logic arrays (ILAs)

Custom design vs. synthesis from VHDL

 8-bit implementations of MIPS from Patterson & Hennessy



 Custom design, 0.6 um CMOS, 1.5x1.5 mm die



Standard cells, 130 nm CMOS, 7 metal layers



Iterative Logic Array (ILA)



 



FIGURE 1.67 MIPS datapath layout

 


Iterative Logic Array (ILA)

 


4-bit adder

 

4-bit adder

 

Example: synthesized 32-bit ALU layout

 


CMOS Fabrication

- CMOS transistors are fabricated on silicon wafer
- Lithography process similar to printing press
- On each step, different materials are deposited or etched
- Easiest to understand by viewing both top and cross-section of wafer in a simplified manufacturing process


Inverter Cross-section

 - Typically use p-type substrate for nMOS transistors
- Requires n-well for body of pMOS transistors




Well and substrate taps

 - Substrate must be tied to GND and n-well to V_{DD}
- Metal to lightly-doped semiconductor forms poor connection called Shottky Diode
- Use heavily doped well and substrate contacts/taps





Inverter Mask Set

 - Transistors and wires are defined by *masks*
- Cross-section taken along dashed line



Inverter mask set and fabrication

  

P+ select

Contact cuts

Metal wires

Poly gate

Active areas

N-well


Fabrication

- Chips are built in huge factories called fabs
- Contain clean rooms as large as football fields




Courtesy of IBM Corporation. Unauthorized use not permitted.

Back to the Y-chart

 


Designing gates with switches

N-switch

 

nMOSFET

P-switch



 


pMOSFET

ON when input A is HIGH
OFF when input A is LOW

OFF when input A is HIGH
ON when input A is LOW


Designing gates with switches

   


input A is HIGH

Designing gates with switches

N-switch

 

P-switch

 


nMOSFET


pMOSFET

input A is LOW


Designing gates: AOI22

 

Designing gates: AOI22

 

Designing gates: AOI22

 


According to de
Morgan's theorem



$$Y = (\overline{A} + \overline{B})(\overline{C} + \overline{D})$$

$$\overline{Y} = \overline{AB} + \overline{CD}$$

Designing gates: AOI22

 

Designing gates: AOI22

  


$$Y = (\overline{A} + \overline{B})(\overline{C} + \overline{D})$$

$$Y = \overline{AB + CD}$$

Simple CMOS gates

The Inverter

 


(a)

(b)

FIGURE 1.11

Inverter schematic
(a) and symbol
(b) $Y = \overline{A}$

The NAND Gate

 


(a)

(b)

FIGURE 1.12 2-input NAND
gate schematic (a) and symbol

$$Y = \overline{AB} = \overline{A} + \overline{B}$$

The NOR Gate

 

(a)

(b)

FIGURE 1.16 2-input NOR
gate schematic (a) and symbol

$$Y = \overline{A + B} = \overline{A}g\overline{B}$$

TABLE 1.1 Inverter truth table

A	Y
0	1
1	0

TABLE 1.2 NAND gate truth table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

TABLE 1.4 NOR gate truth table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Exercise: AOI21 AOI31, OAI22

Derive gate from Karnaugh map

End of CMOS design lecture!

Q & A?