

MCC092

Postlab lab 3

Prelab lab 4

2018-10-02

Lena Peterson


Week 5

- Monday October 1
 - Lab 3
- Tuesday October 2
 - Lecture on wires (Kjell)
 - Postlab 3 + prelab 4 session
- Thursday October 4
 - Prelab 4 + preparation for adder exercise 1
 - Wire exercise
- Friday October 5
 - Deadline prelab 4

Lab 3

- Do your design on paper first.
- Euler analysis is good - but there may be multiple solutions.
- Stick diagrams help.
 - If you must revise your solution do that on paper first!
- Usually no metal-2 in standard cells.

Euler path

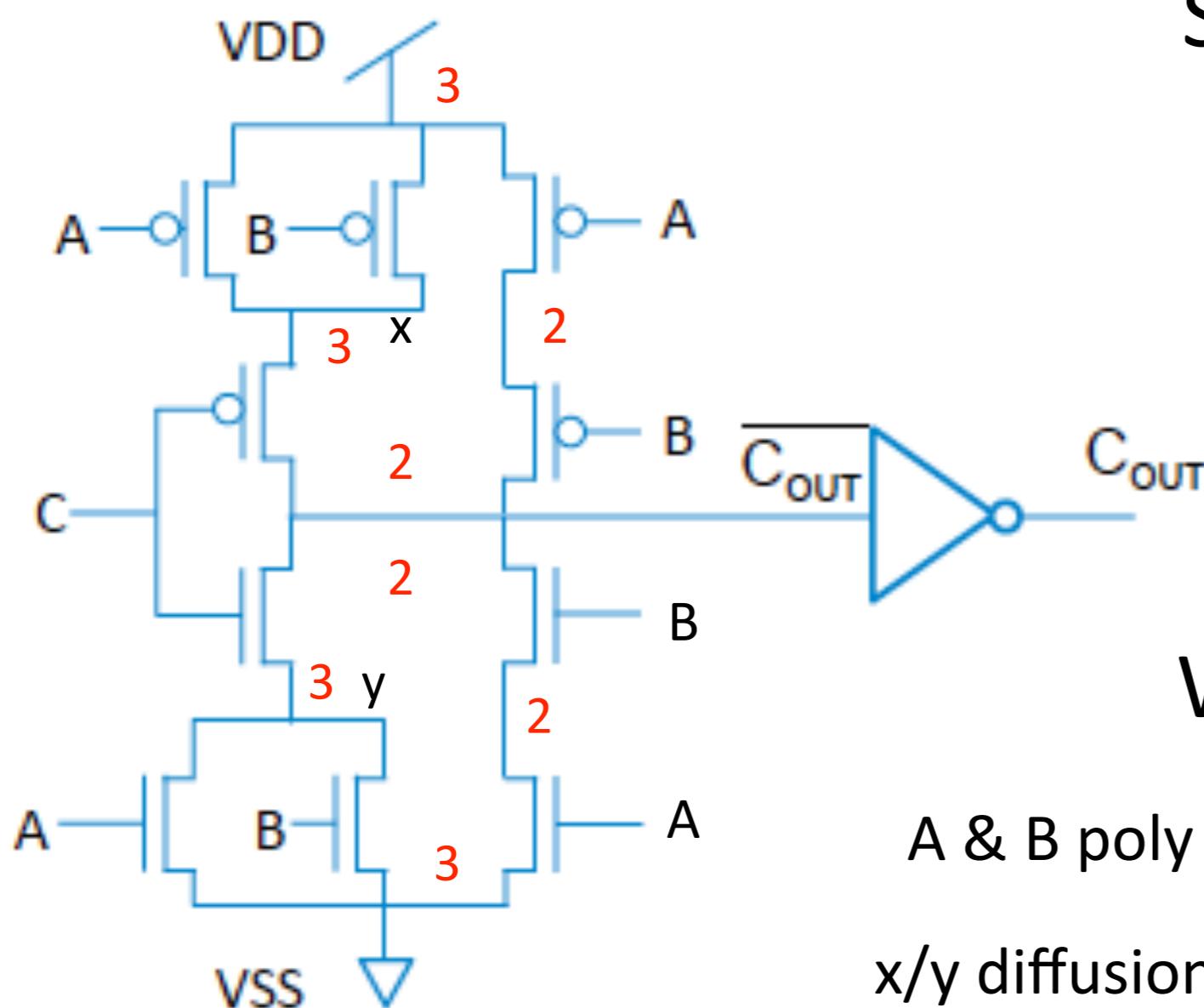

Same topology in n-net and p-net.


Odd order nodes:
Start/end in x/y and V_{DD}/V_{SS}

Which one to choose?

A & B poly lines must be connected


x/y diffusion areas must be connected with metal-1 wire since their node order is > 2

Three Euler paths

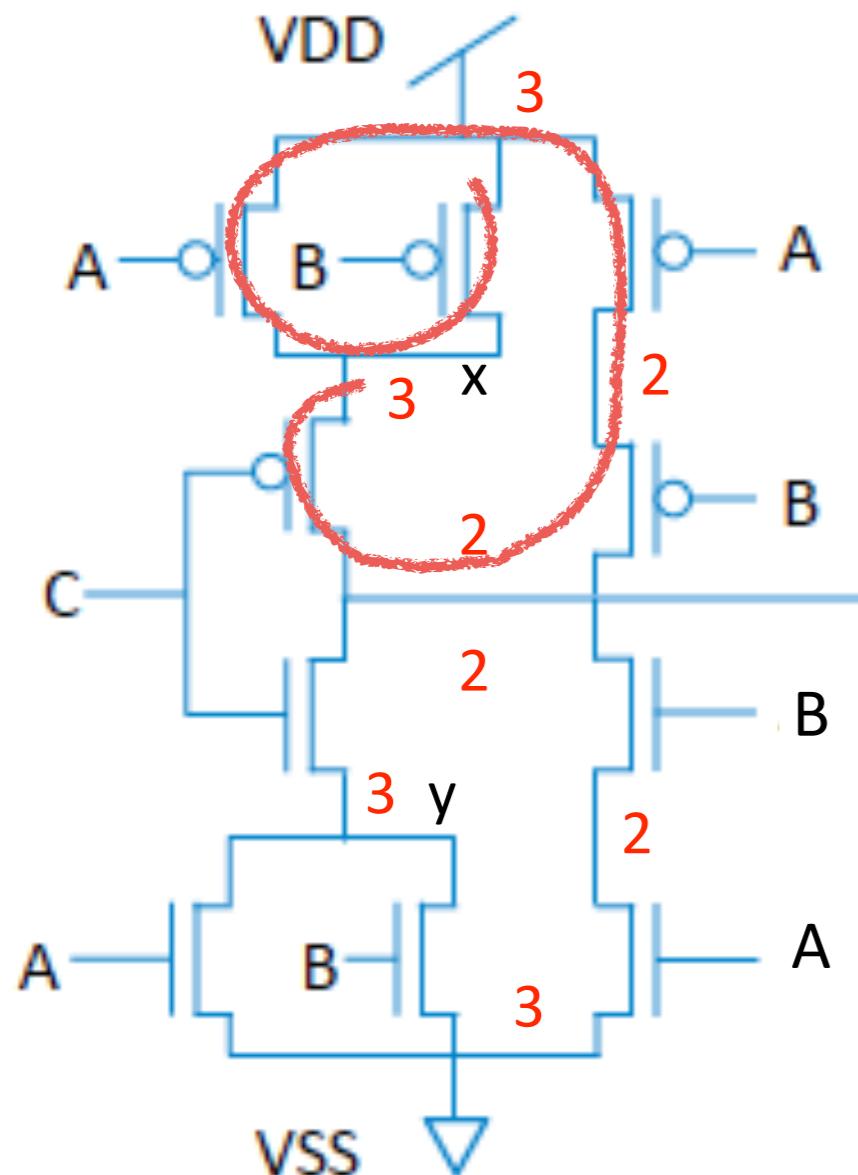


(1) That is: BAABC

(2) Also possible: ABABC

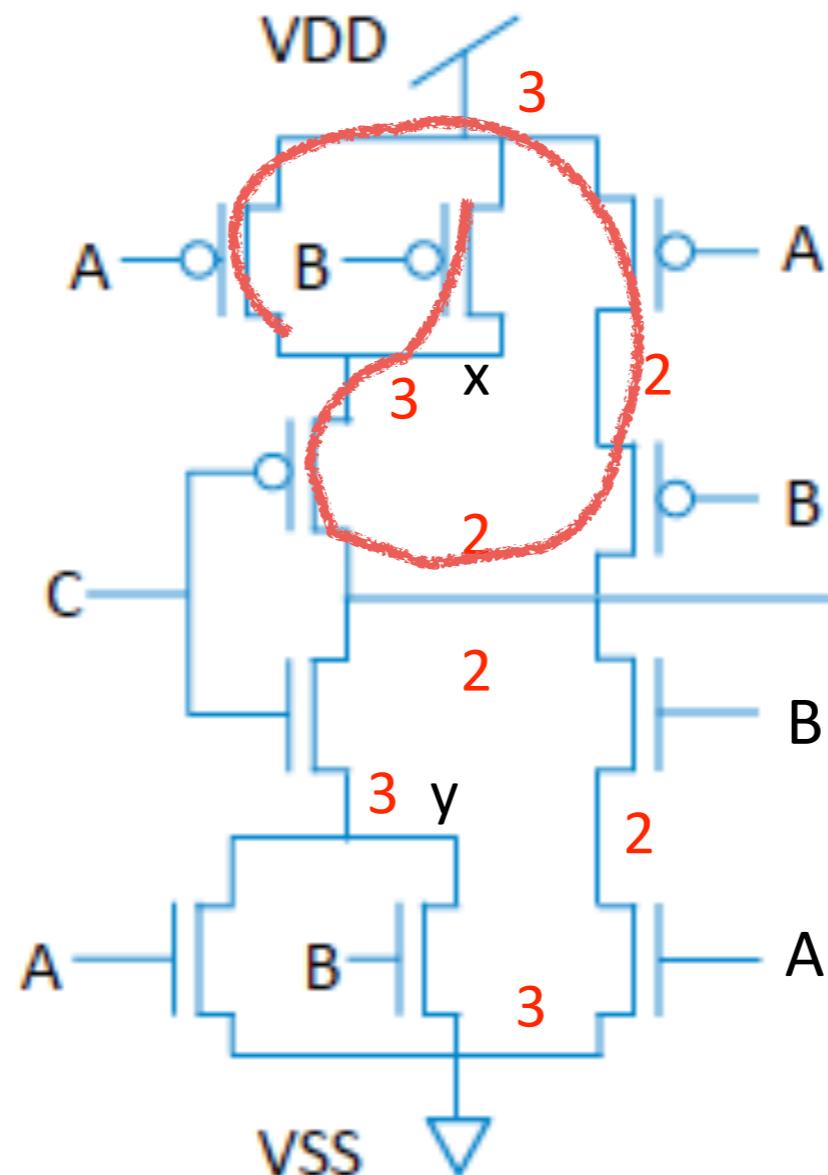

(3) That is: AABCB

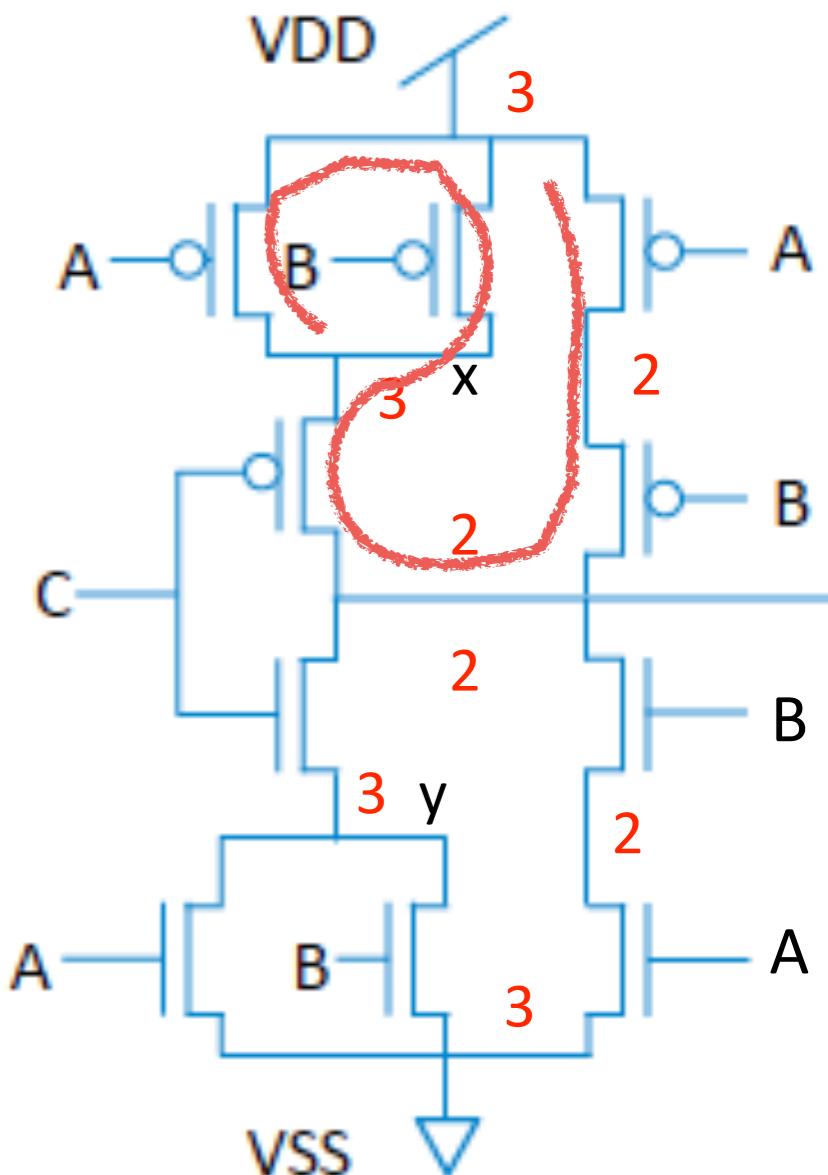
(4) Also possible: BABCA (6) Also possible: BACBA




(5) That is: ABCBA

Four single-lines-of diffusion



(1) BAABC

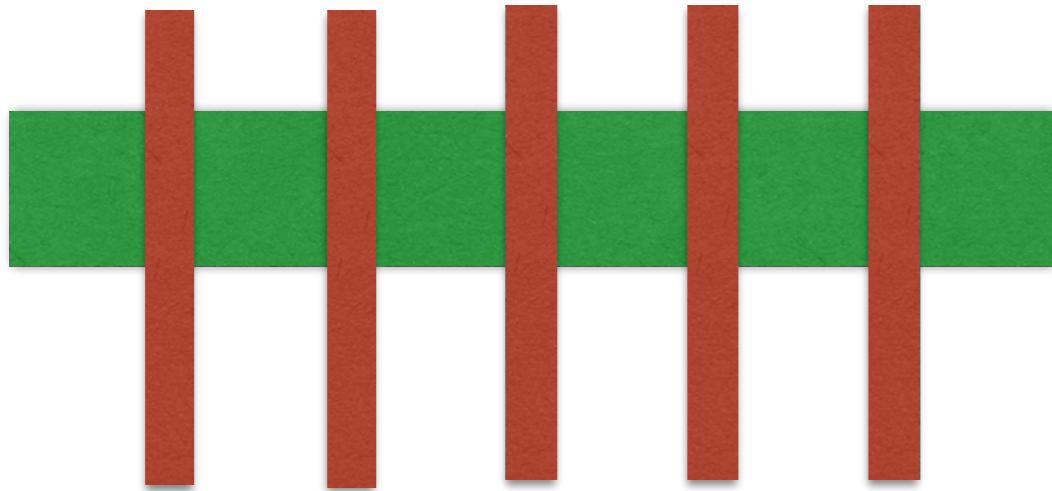

(3) AABCB

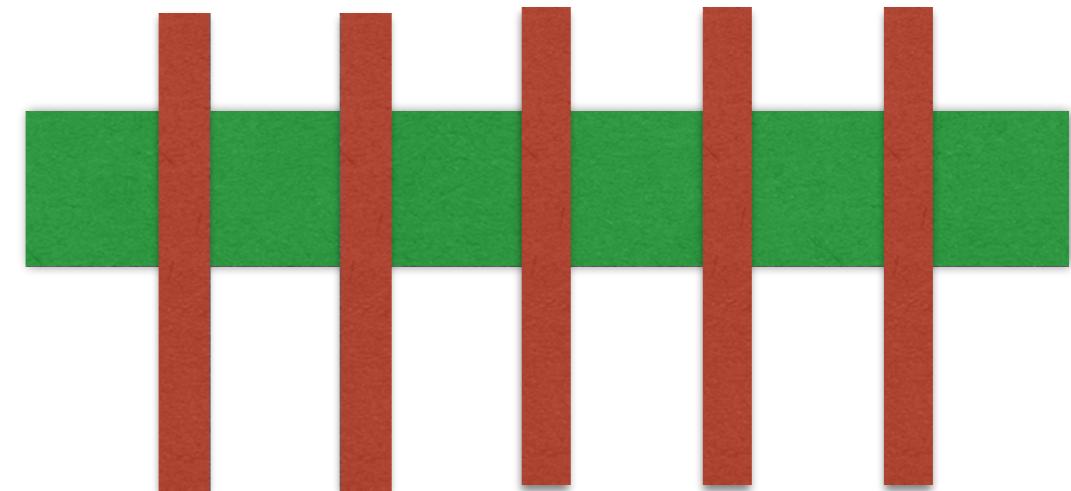


(5) ABCBA

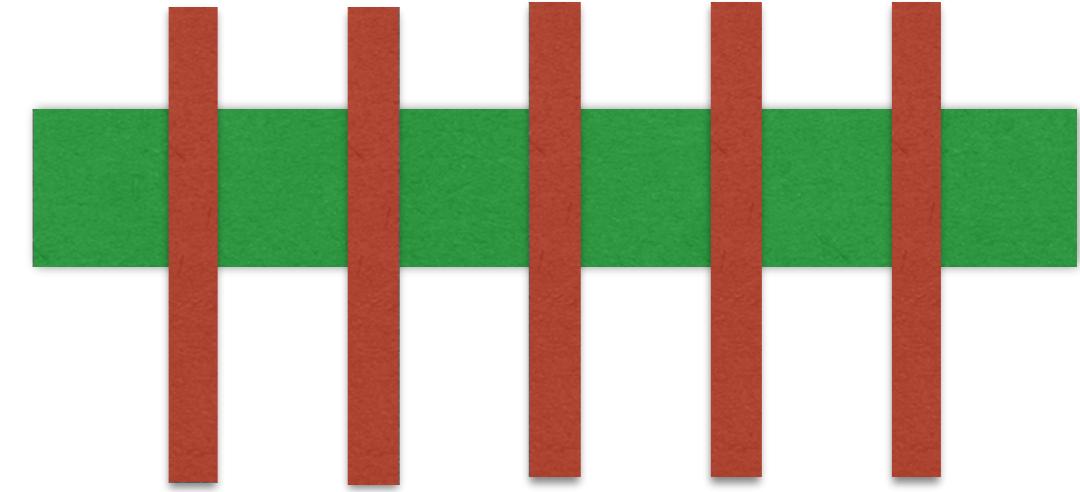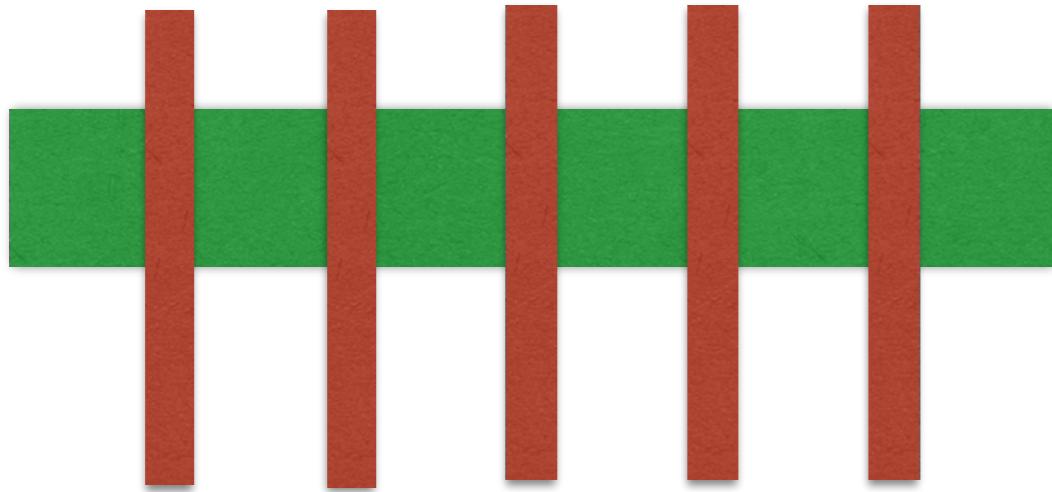


Four single-lines-of diffusion



(1) BAABC

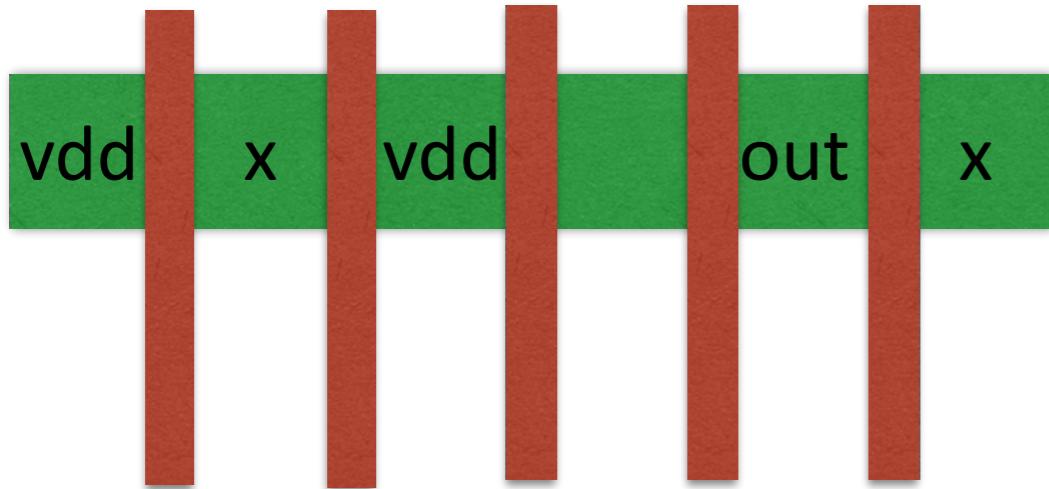

(3) AABCB

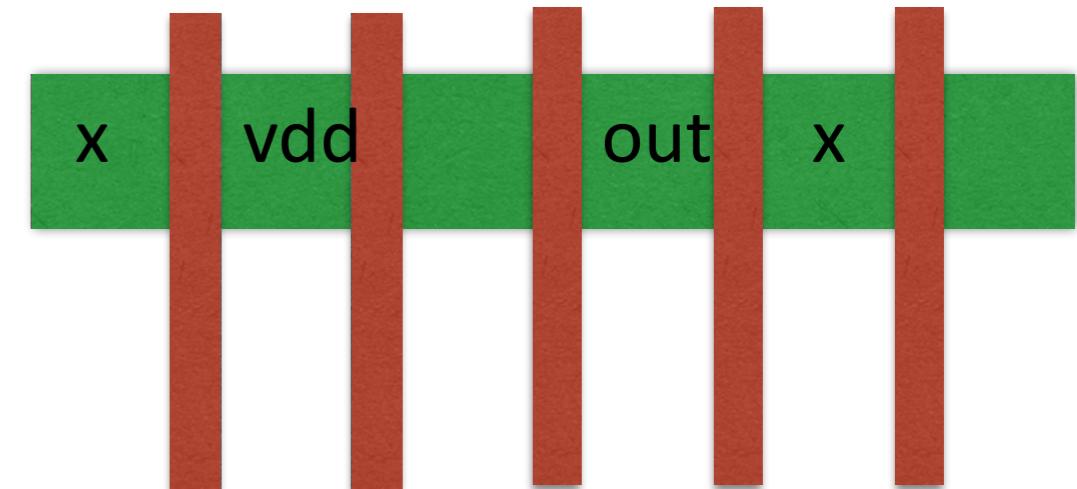


(5) ABCBA

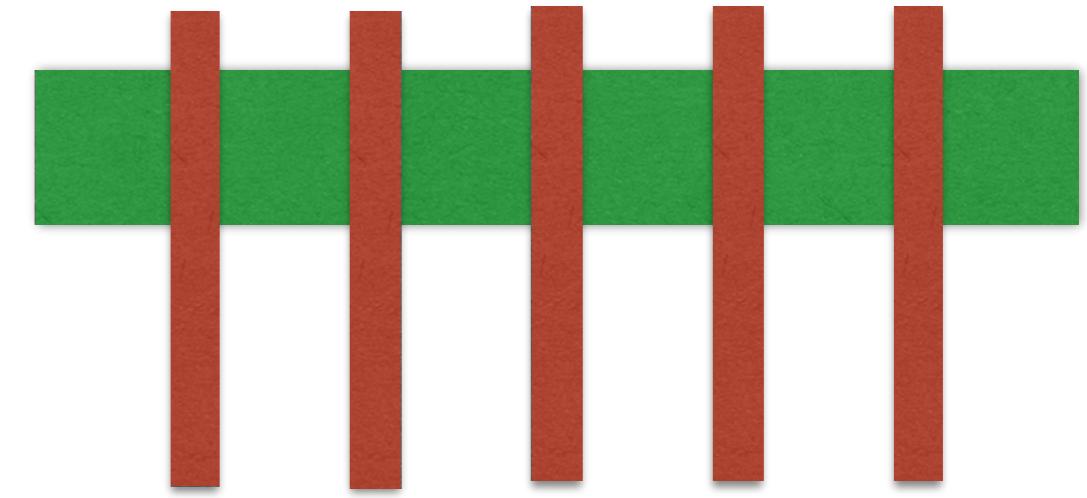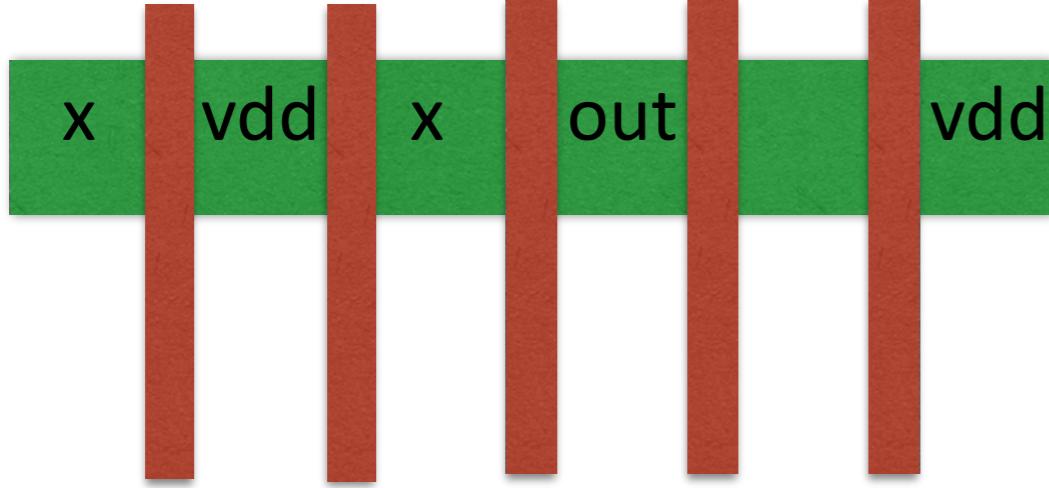


Mapping path to single-line-of diffusion


Step 1: The path as drawn

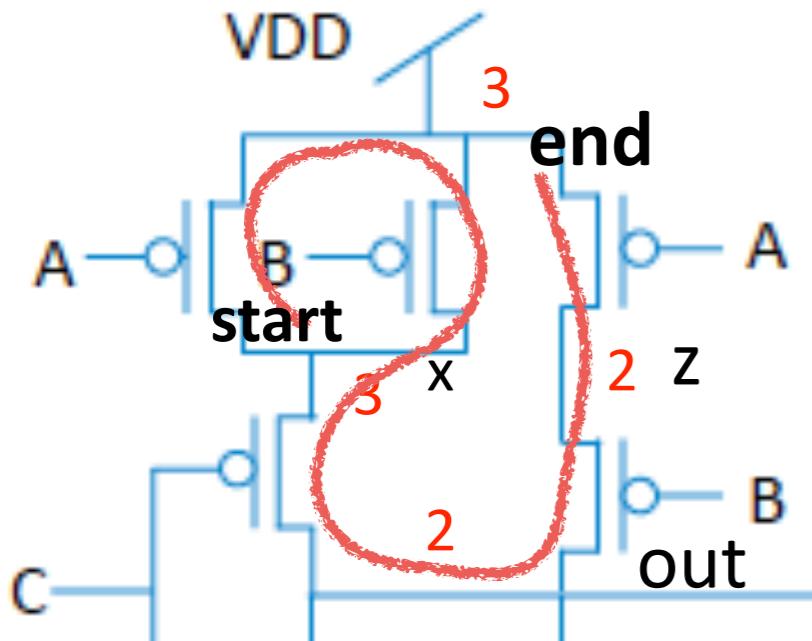

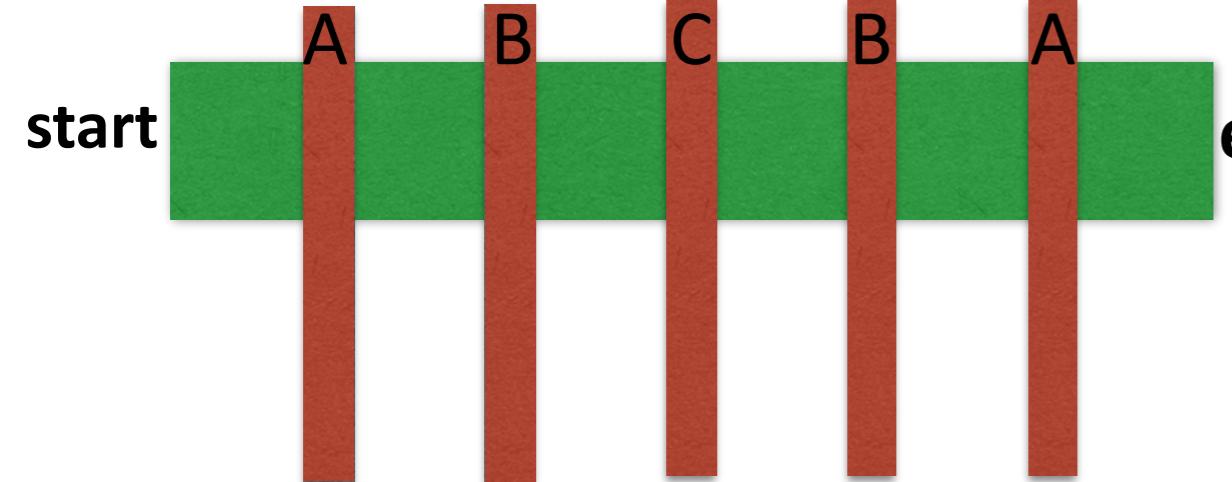
Step 2: Label the gates on diffusion from start to end of path



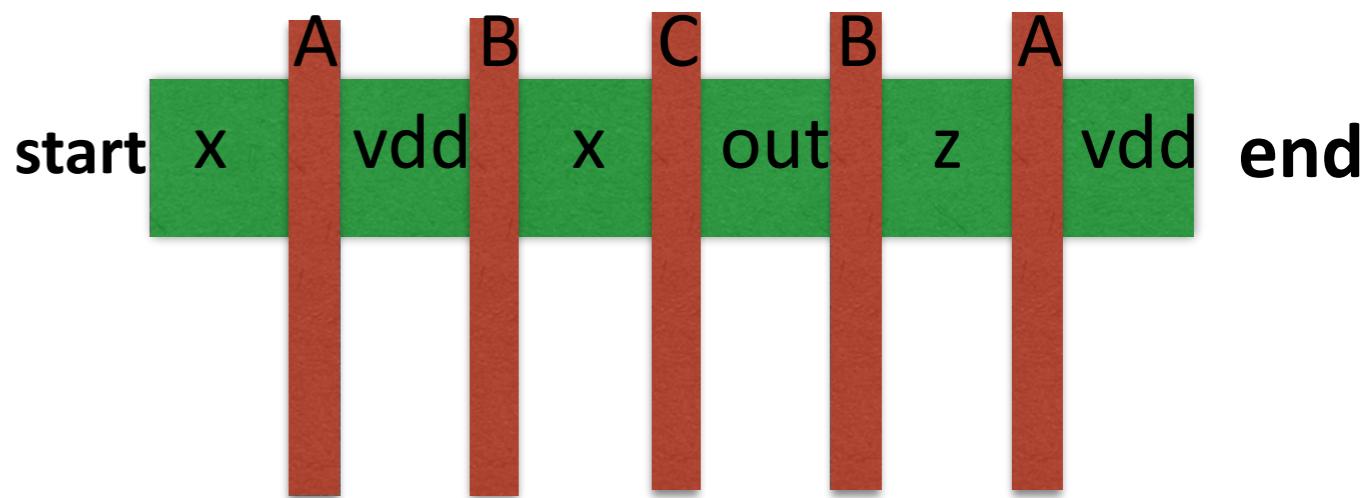Step 3: Label the circuit nodes along the path from start to end



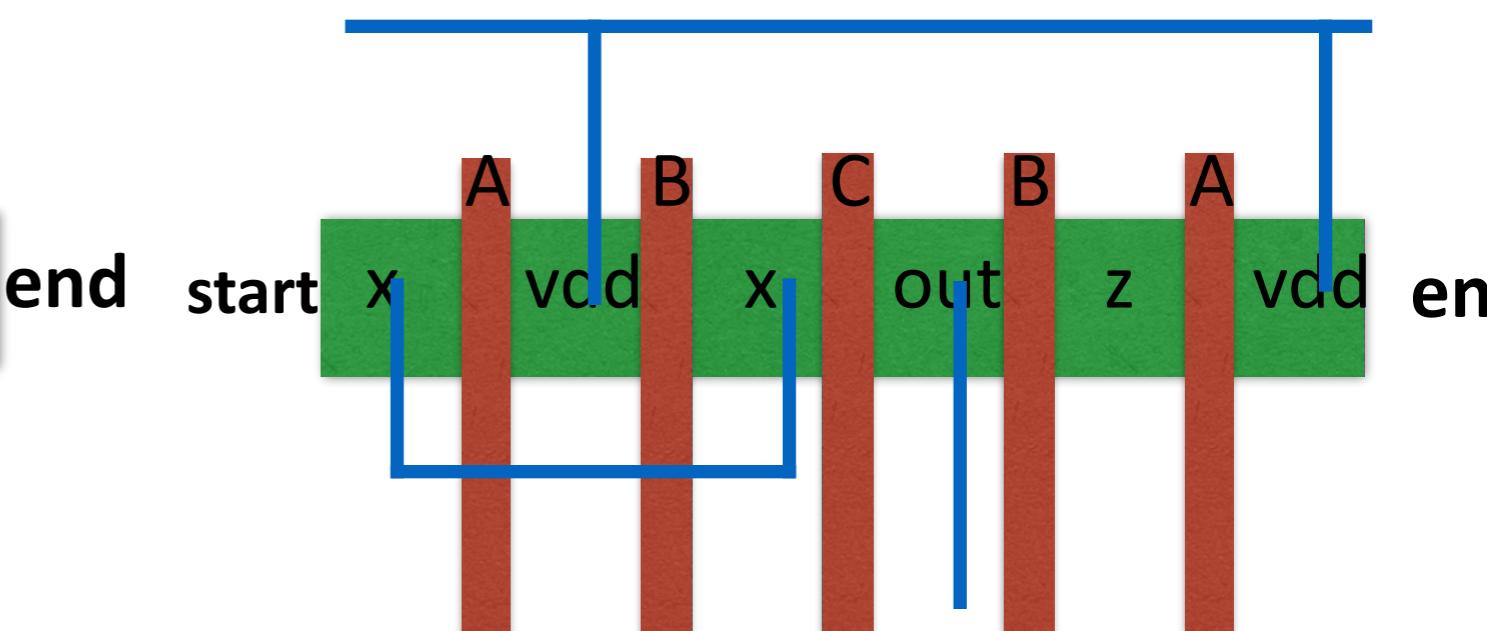
Step 4: Draw (stick) connections to connect areas that are the same ckt node



Layout quick questions

Alternatives:

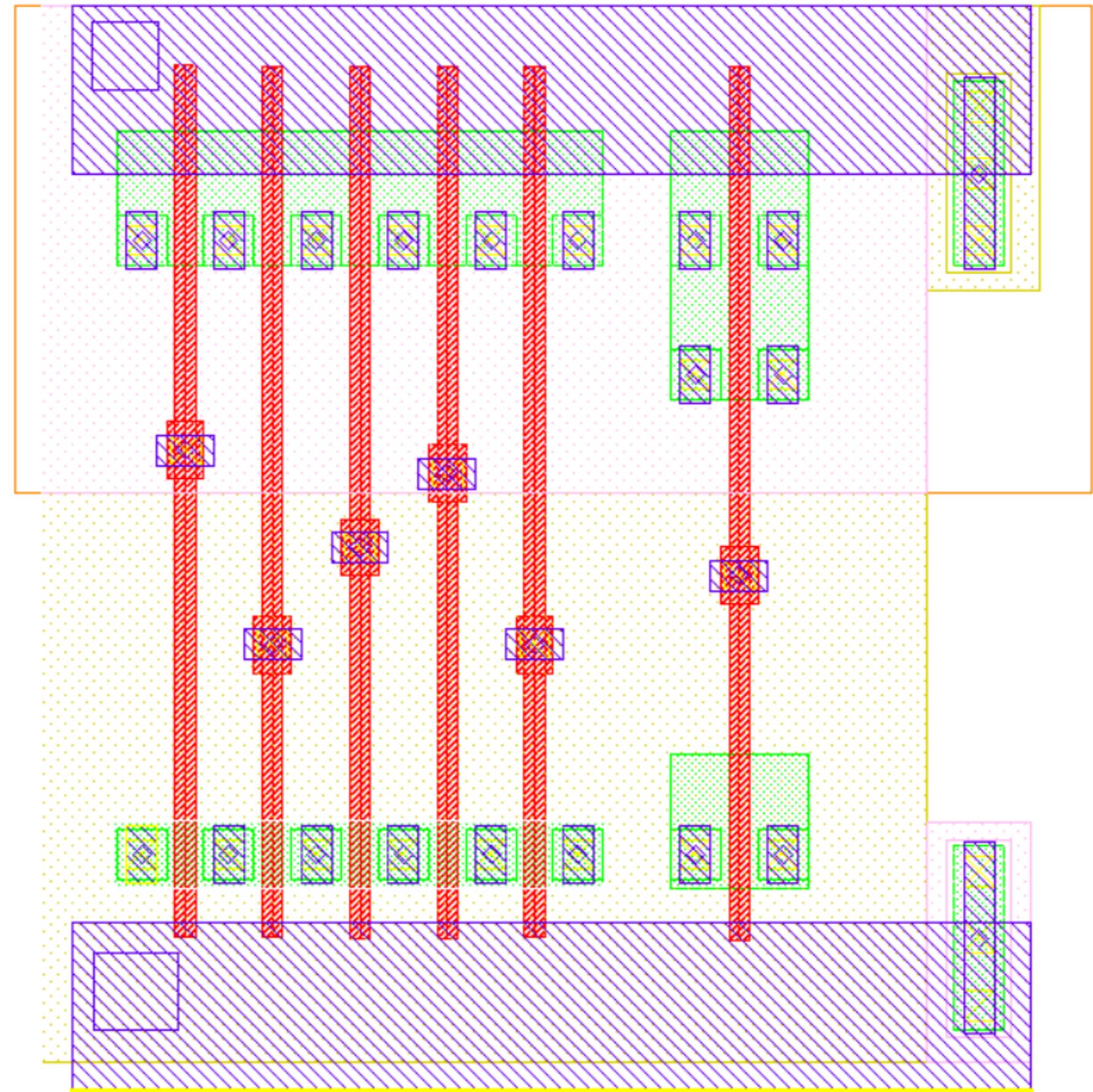
1. Diffusion
2. Pplus
3. Nplus
4. N-well
5. Poly



Layout quick questions

Alternatives:

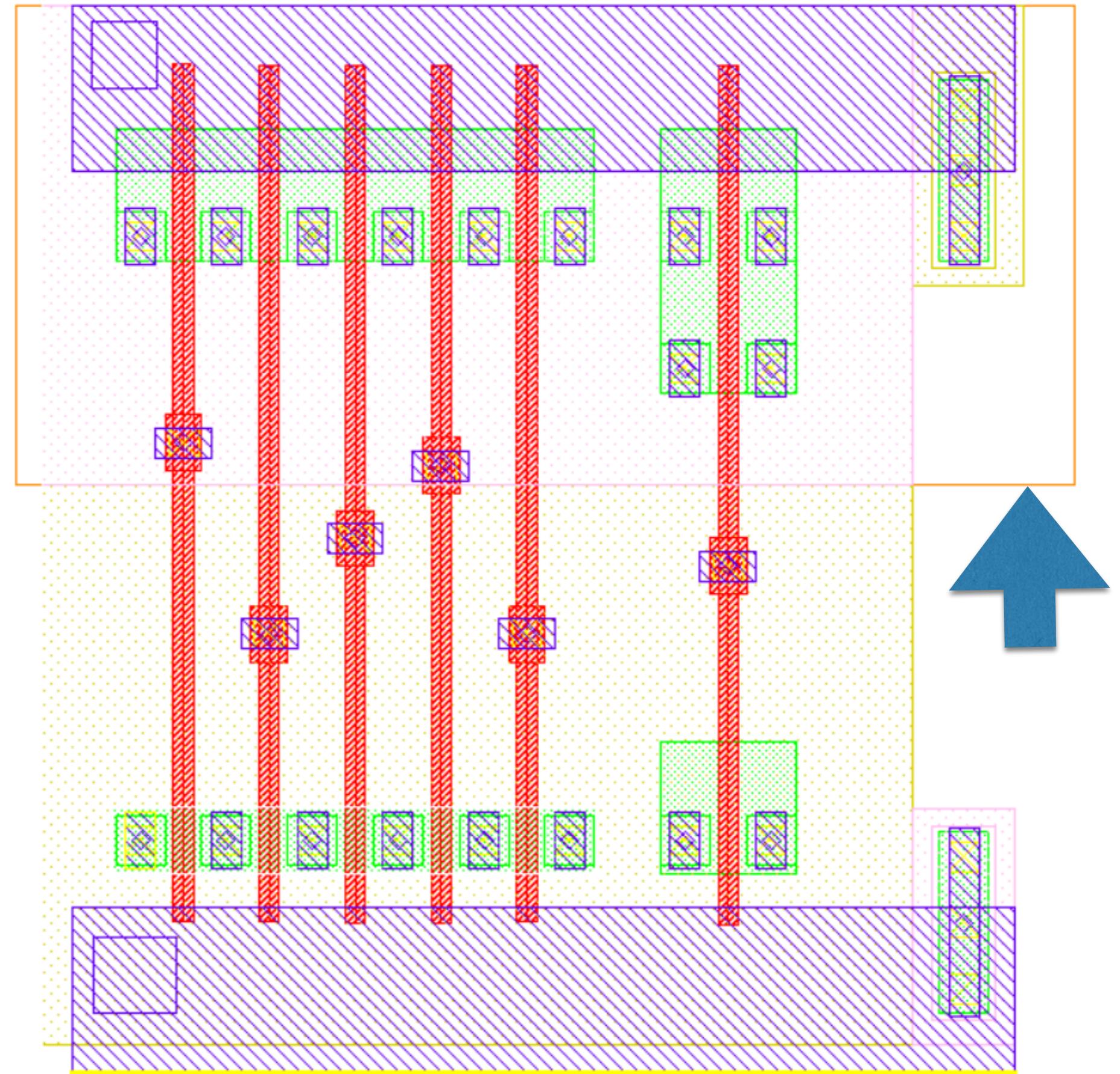
- A. Diffusion
- B. Pplus
- C. Nplus
- D. N-well
- E. Poly



Layout quick questions

Alternatives:

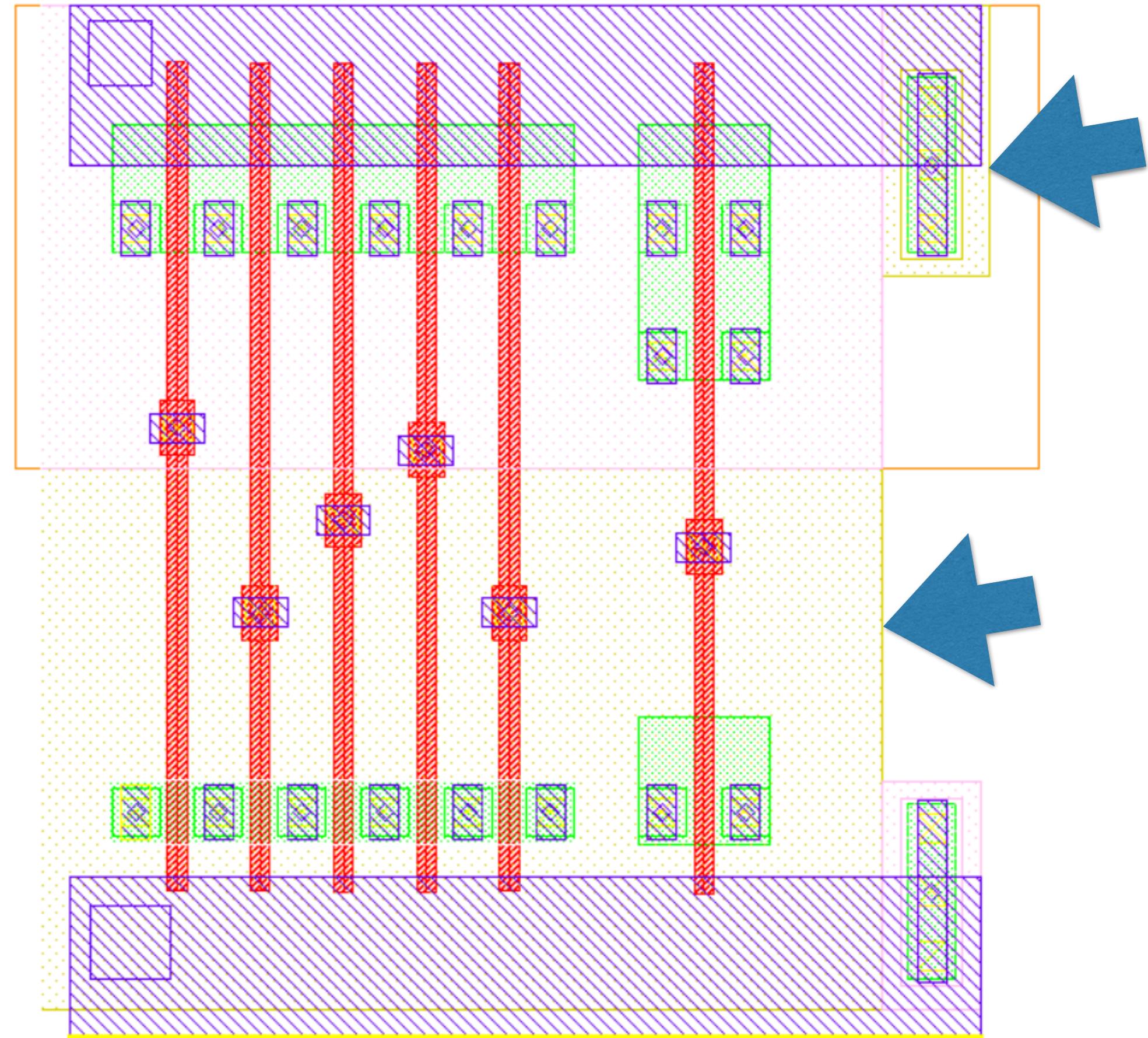
- A. Diffusion
- B. Pplus
- C. Nplus
- D. N-well
- E. Poly



Layout quick questions

Alternatives:


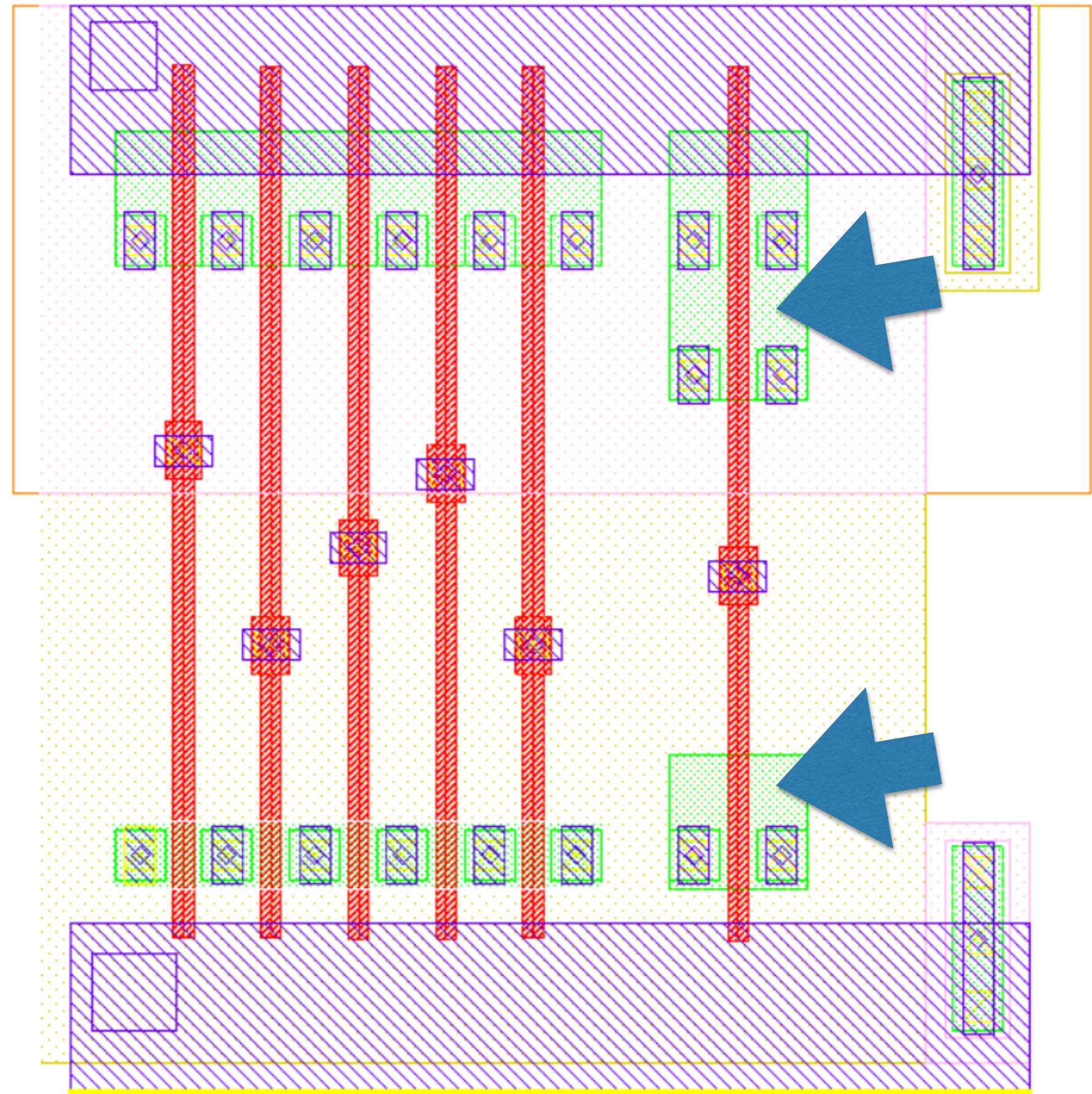
- A. Diffusion
- B. Pplus
- C. Nplus
- D. N-well
- E. Poly



Layout quick questions

Alternatives:

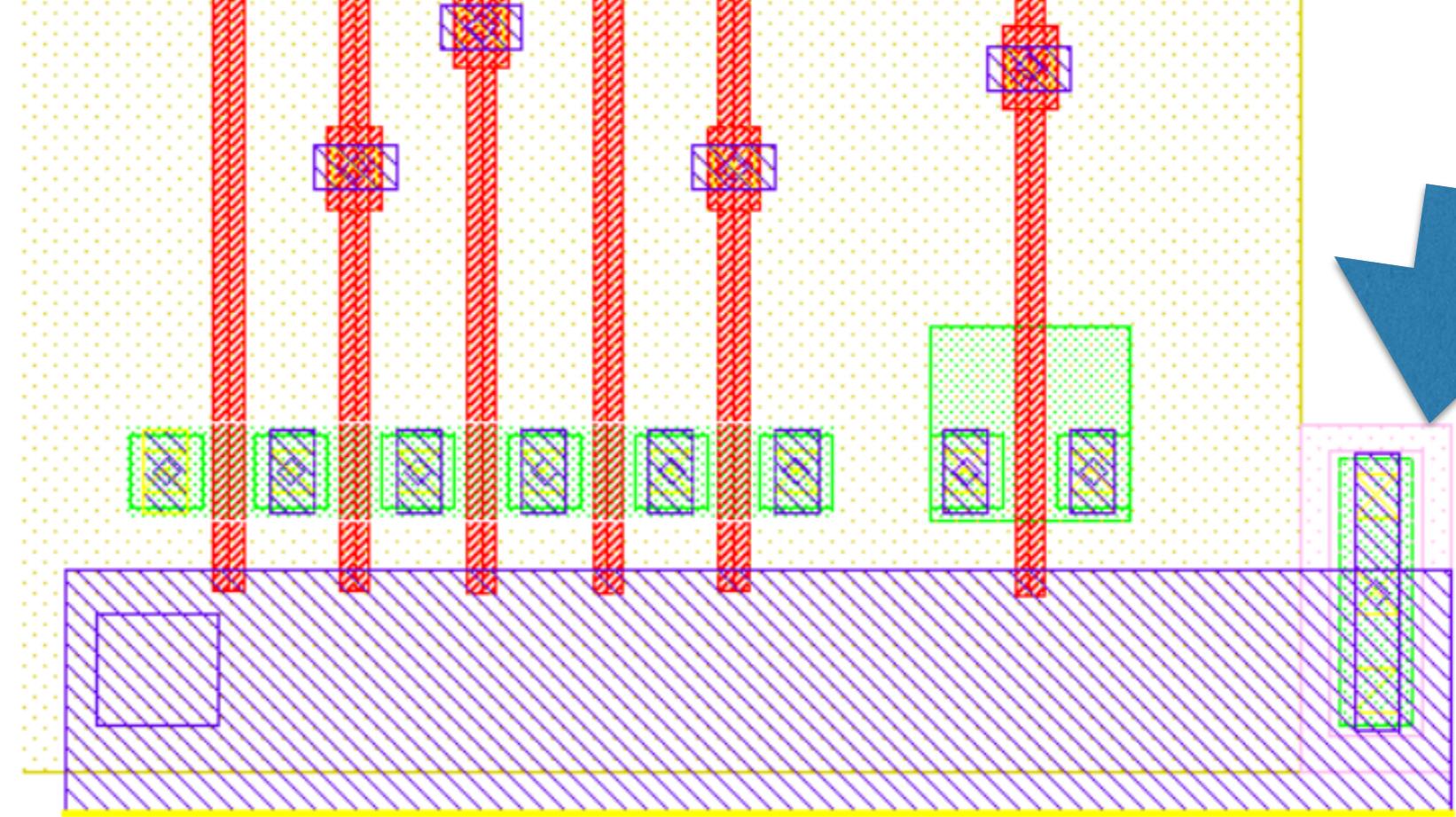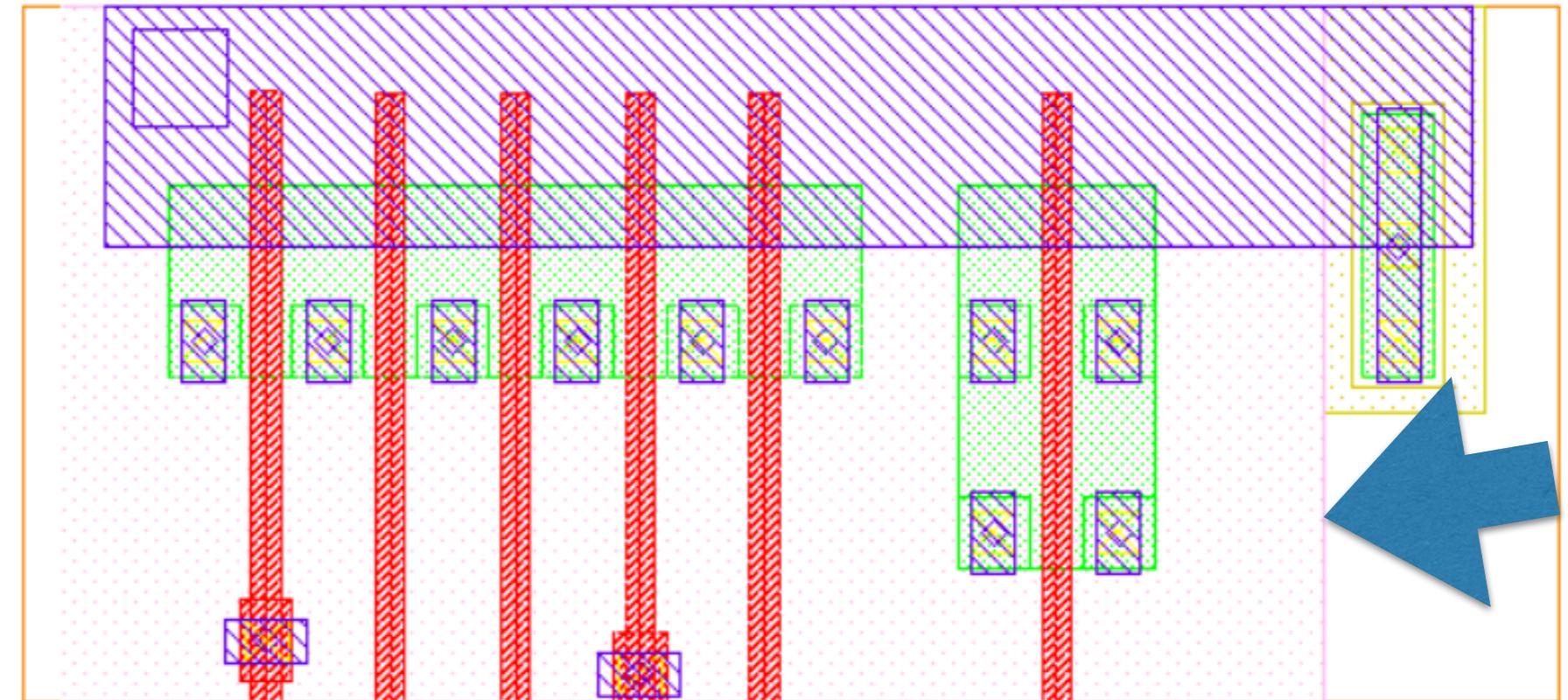
- A. Diffusion
- B. Pplus
- C. Nplus
- D. N-well
- E. Poly



Layout quick questions

Alternatives:

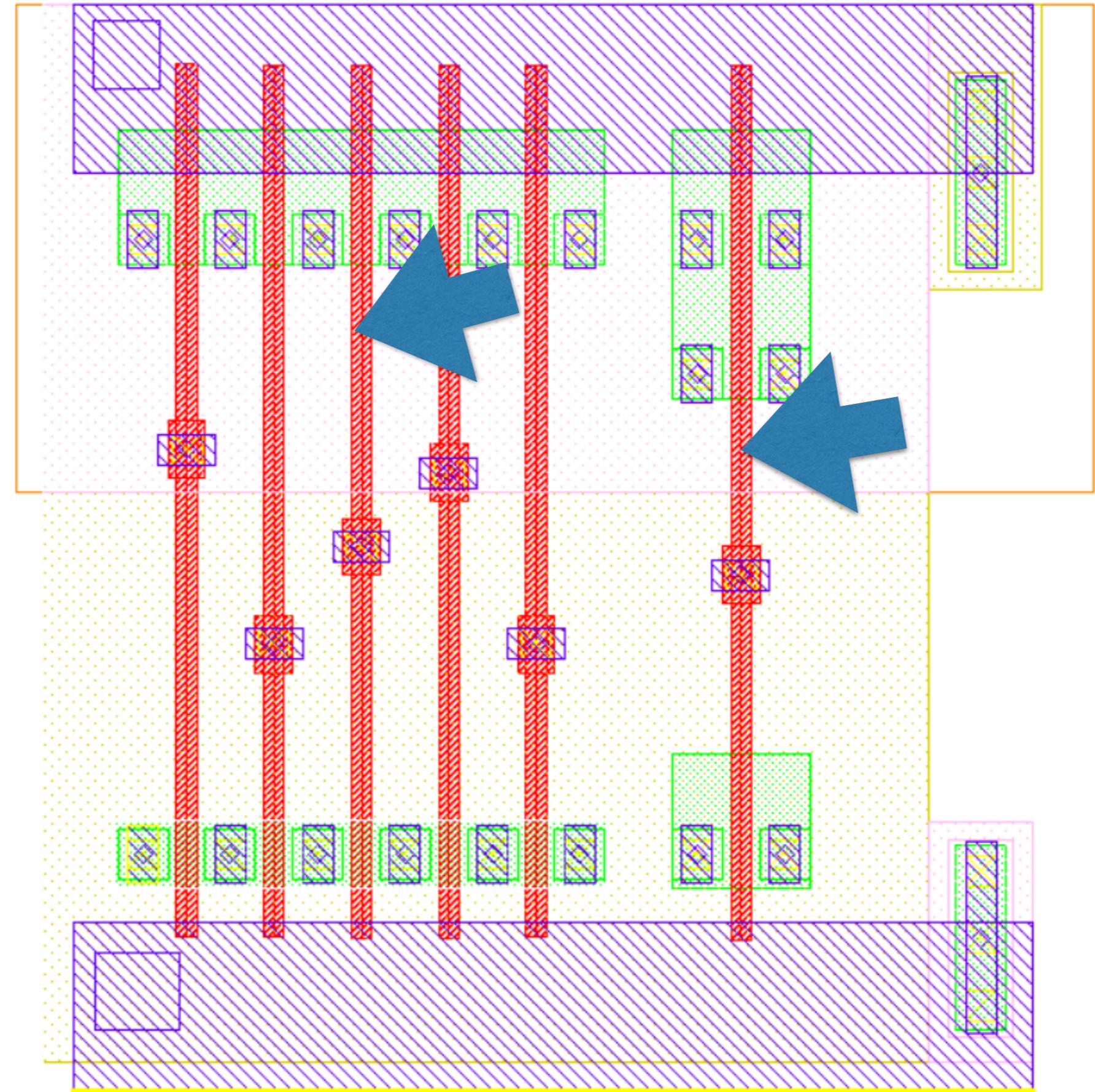- A. Diffusion
- B. Pplus
- C. Nplus
- D. N-well
- E. Poly




Rules

- Many rules!
- If you are to fabricate even more rules!
- Minimum area of metal 1: $0.042 \mu\text{m}^2$
- All poly has to be covered by nplus or pplus

Layout-versus-schematics

- The graphs have to match exactly:
 - Order of transistors matter
- If you have unconnected the NTAP from Vdd p-transistor bulks are not connected to Vdd.
- Labels have to be exactly the same (case matters)

Prelab 4

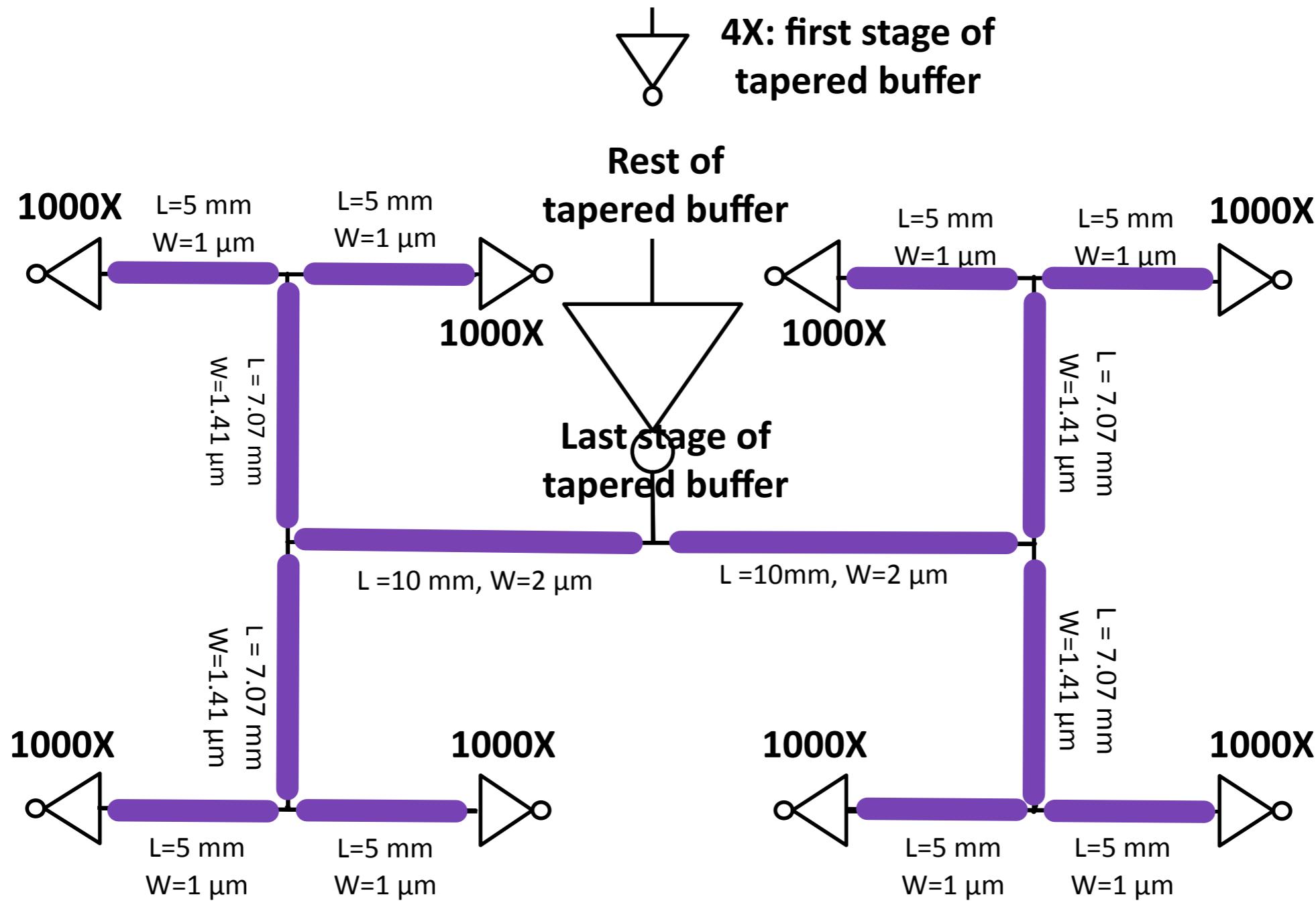

Lab 4

- All documents updated today!
- Clock H tree:
 - C only - design tapered buffer
 - C+R effect on delay
 - Repeaters in tree
 - Effect of skew in capacitive load of tree


Prelab 4, calculations part 1

- Each wire segment = one pi link
- First, $R_{SH}=0$, that is whole tree is one big capacitance
- Design a tapered buffer to drive this huge capacitance
- How many stages, N , to use? What is f_{opt} ?
 - Note that N has to be an integer, f_{opt} does not.


Prelab 4, calculations part 2

- Assume $R_{SH} \neq 0$
- Calculate delay to leaves using Elmore model
- Collapsed tree helps!

H-tree branching

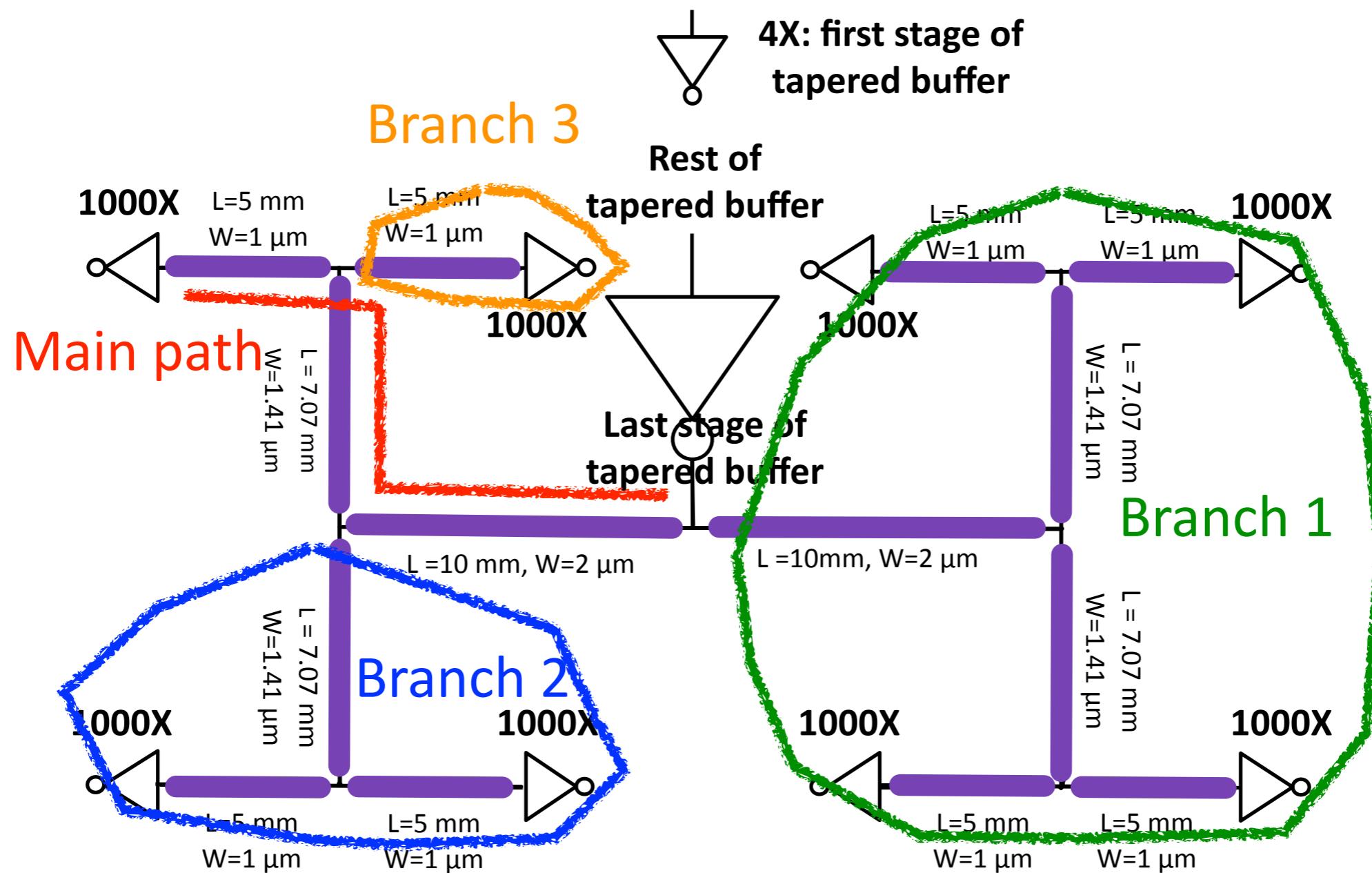


H-tree collapsing

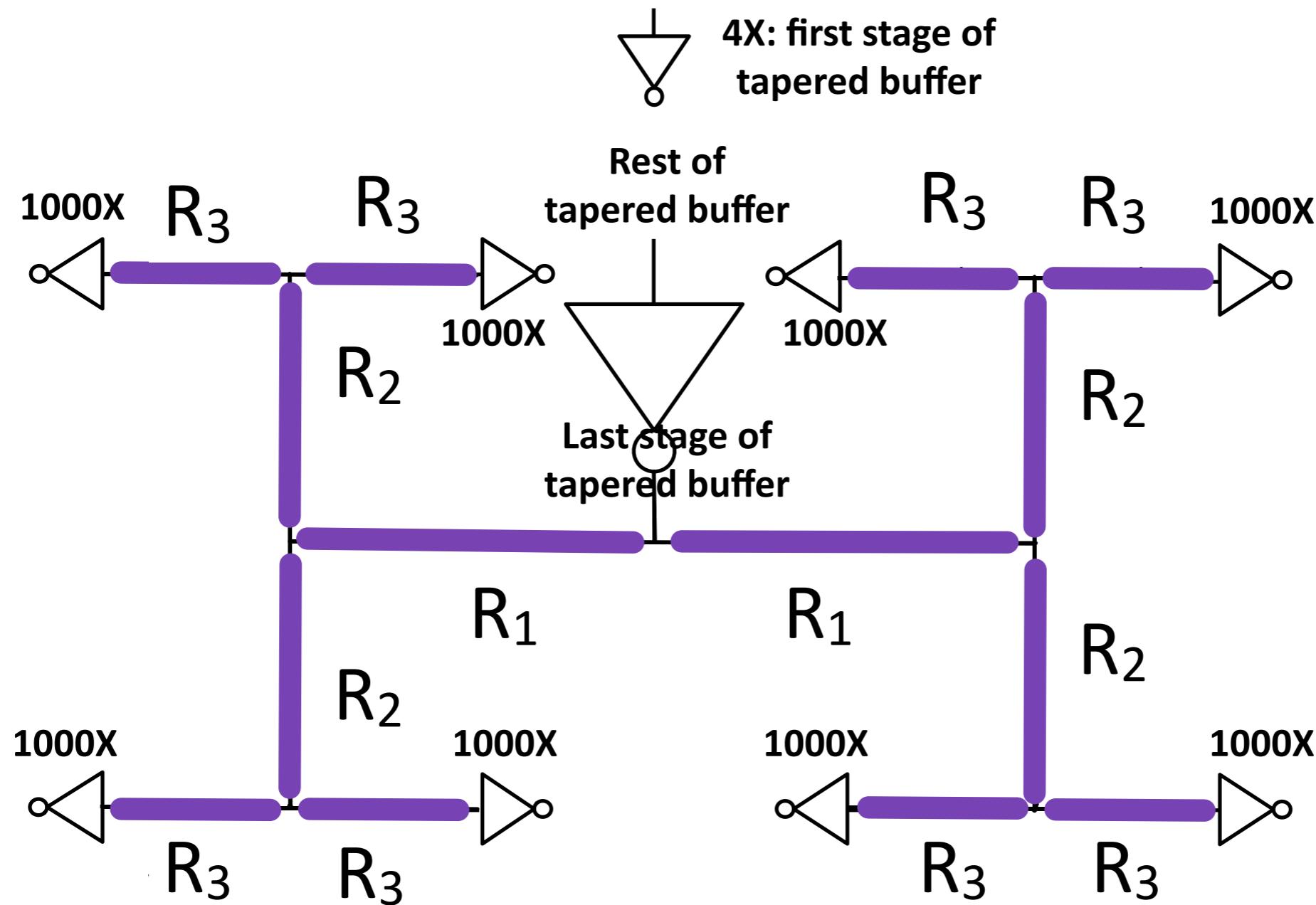

H-tree collapsing


Fold over once

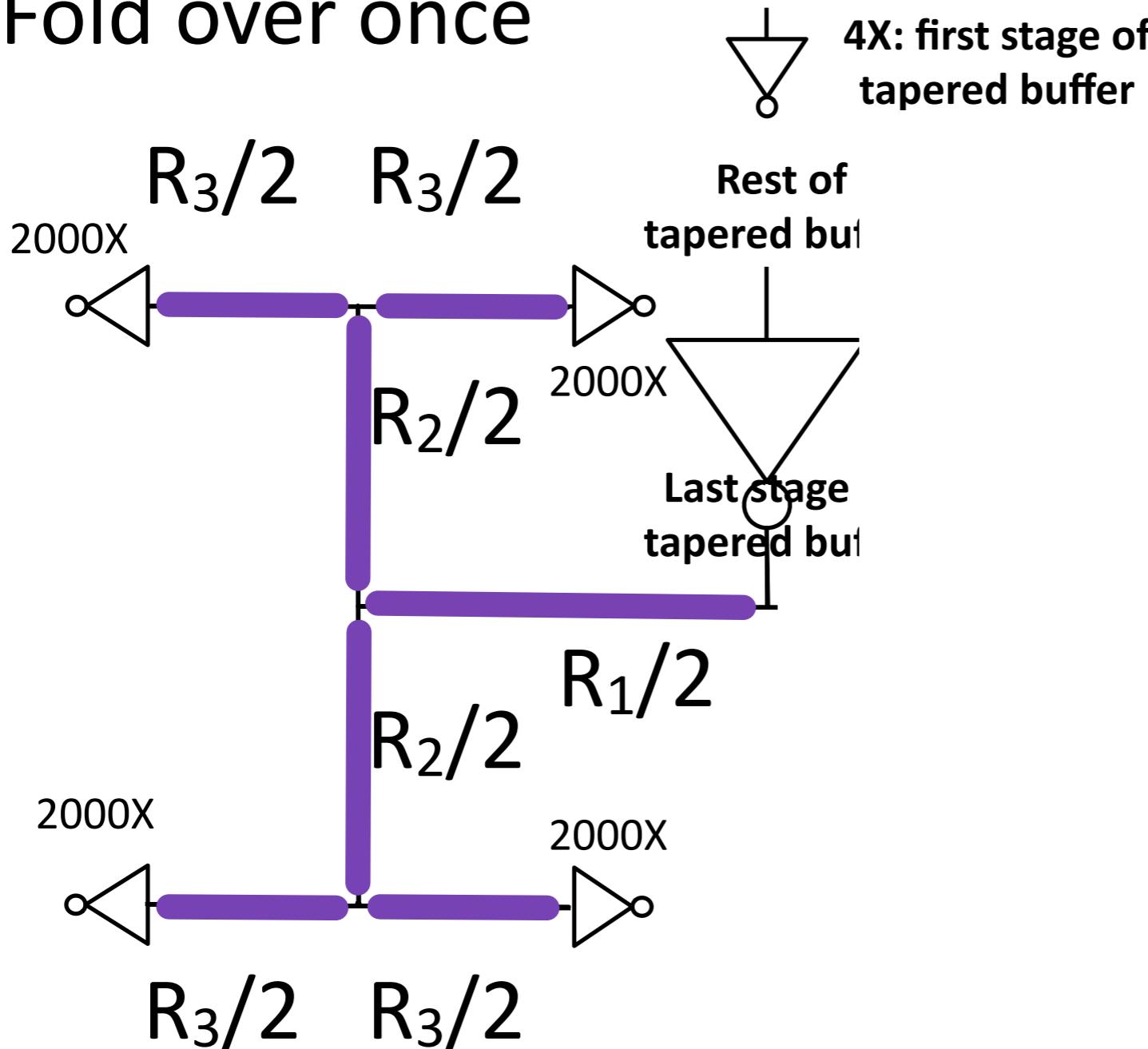

And wire
capacitances in
parallel are
added

H-tree collapsing


Fold over twice

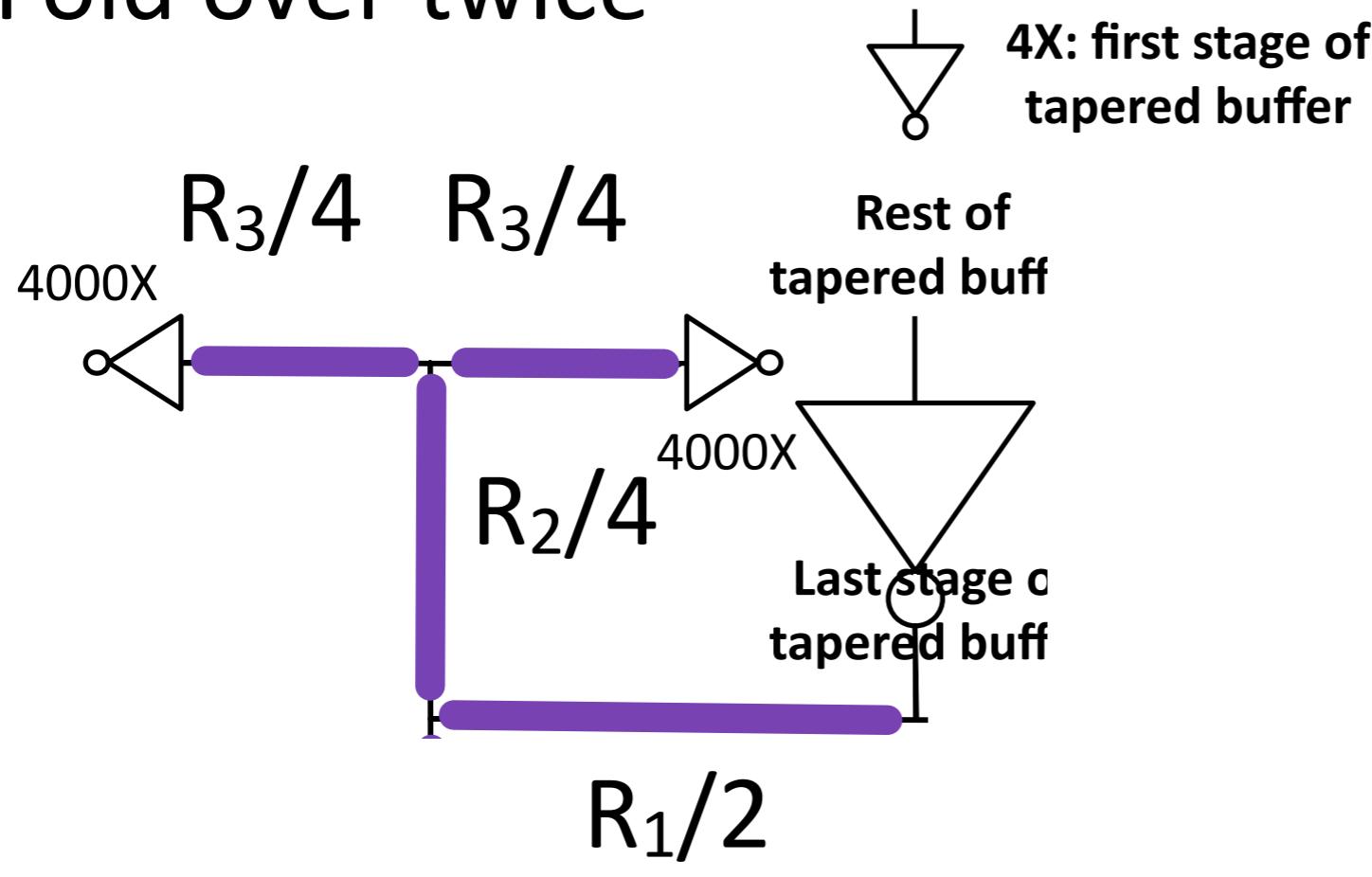

And wire
capacitances in
parallel are
again added


H-tree collapsing

Fold over thrice

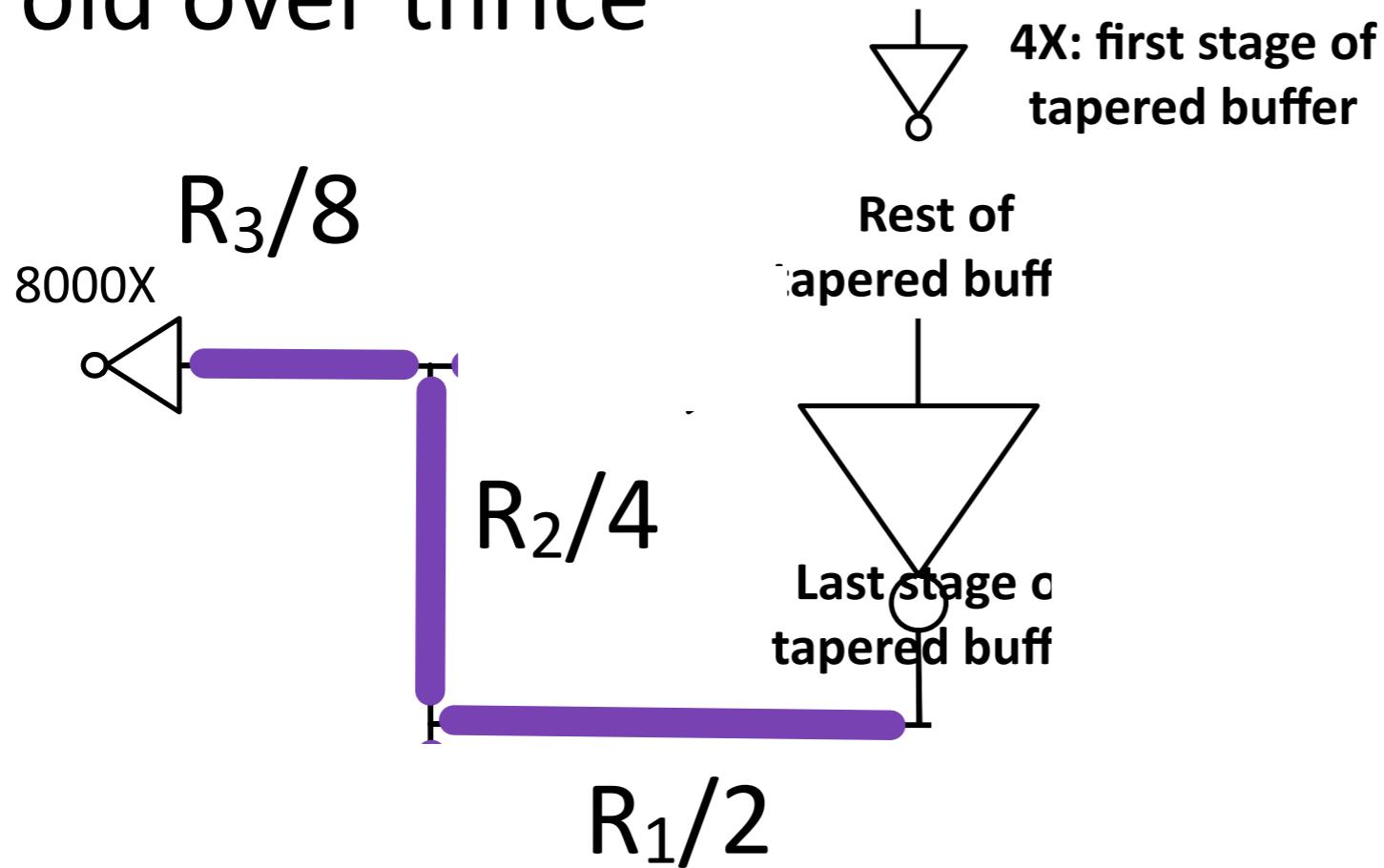

And wire
capacitances
are added again

Prelab 4, calculations part 3

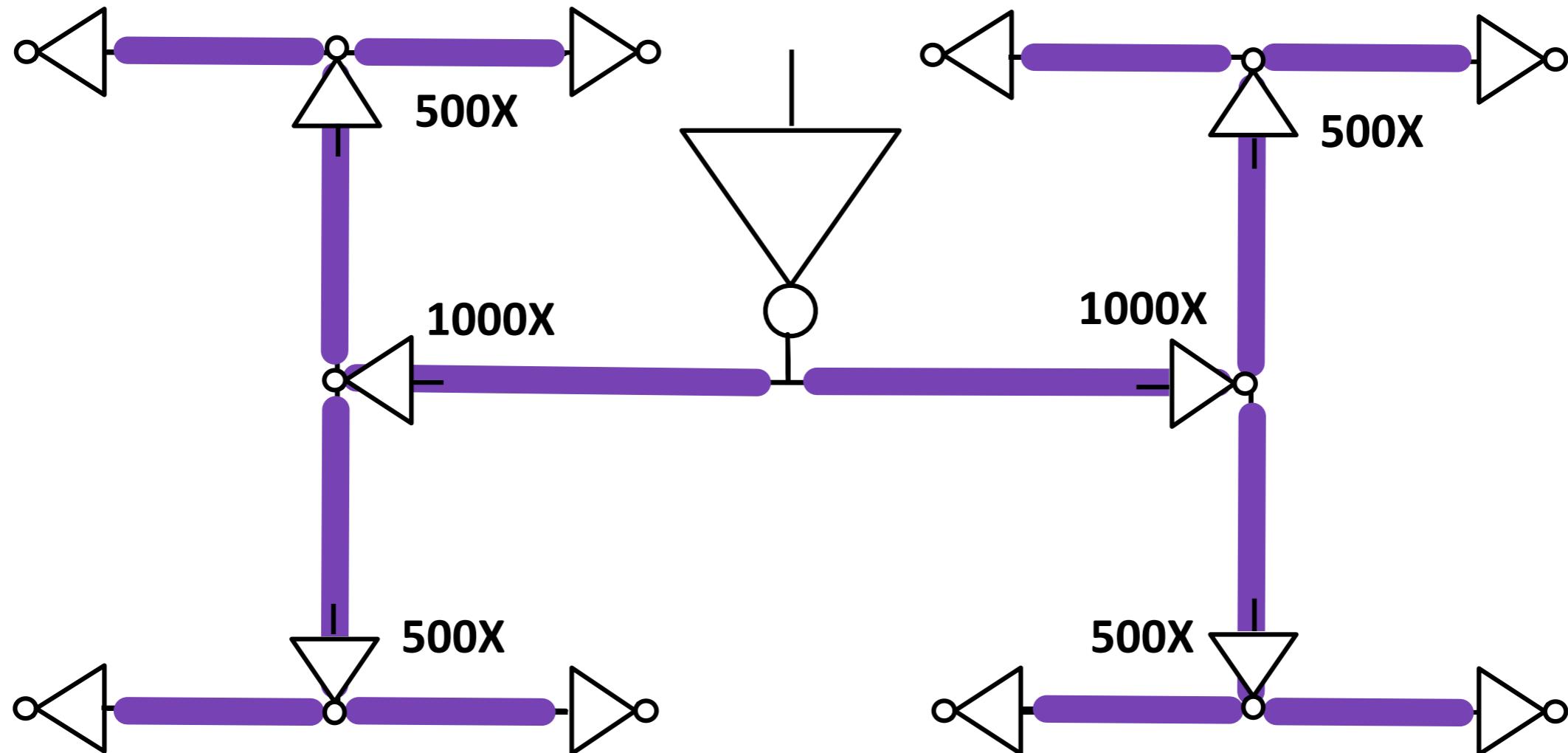

Prelab 4

- We will use Spectre with command-line input.
- Write the Spectre input file properly!
 - Otherwise you have to spend valuable lab time doing that.
 - File will be copied to `heffalump` before lab.
- Consultation times:
 - Thursday 9.15-10 w. Victor
 - Thursday 16.00-17.00 w. Lena
 - Friday 9-10 w. Lena