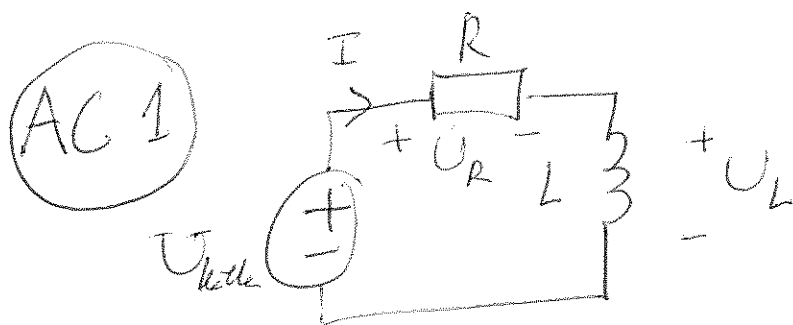




$$U_{källa} = 10 \text{ V}$$

$$R = 100 \text{ } \Omega$$

$$L = 0,050 \text{ H}$$

$$\omega = 2000 \text{ rad/s}$$

a) Komplexa spänningen över induktorn:

$$U_L = U_{källa} \frac{j\omega L}{j\omega L + R} = 10 \cdot \frac{j 2000 \cdot 50 \cdot 10^{-3}}{j 2000 \cdot 50 \cdot 10^{-3} + 100} = 10 \frac{j}{j+1}$$

$$= \frac{10 e^{j90^\circ}}{\sqrt{2} e^{j45^\circ}} = \underline{\underline{7,07 \cdot e^{j45^\circ} \text{ volt}}}$$

Tidsfunktion:

$$u_L(t) = \text{Im} \{ U_L \cdot e^{j\omega t} \} = 7,07 \cdot \sin(2000t + 45^\circ)$$

$$\approx \underline{\underline{7,1 \cdot \sin(2000t + 45^\circ) \text{ volt}}}$$

b) $P = \frac{1}{2} R |I|^2$ där $|I|^2 = \left| \frac{U_{källa}}{R + j\omega L} \right|^2 = \frac{U_{källa}^2}{R^2 + \omega^2 L^2}$

$$= 0,005 \text{ A}^2$$

$$\Rightarrow \underline{\underline{P = 0,125 \text{ W}}}$$

$$c) \quad U_R = U_{\text{eff}} \frac{R}{R + j\omega L} = \frac{10}{1+j} \approx 7,07 \cdot e^{-j45^\circ} \text{ volt}$$


$$\Rightarrow \hat{U}_R \approx 7,07 \text{ V} \text{ d.h. samma som } \hat{U}_L.$$

$$[\text{Alt. lös. } U_R = I \cdot R \dots]$$

$$\hat{U}_R^2 + \hat{U}_L^2 = \hat{U}_{\text{källa}}^2$$

d) —

AC 2

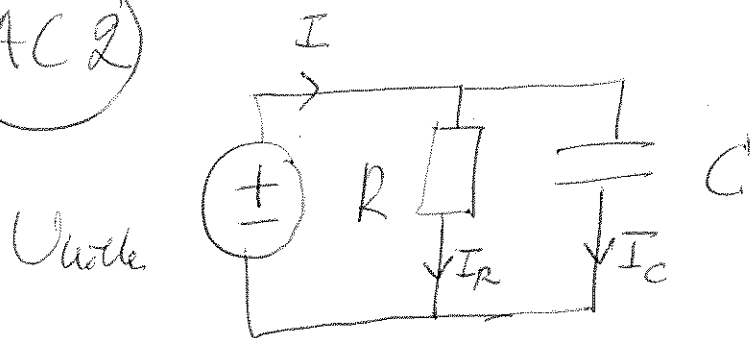

$$U_{\text{Kolle}} = 10 \text{ V}$$

$$R = 50 \Omega$$

$$C = 5,0 \mu\text{F}$$

$$\omega = 2000 \text{ rad/s}$$

$$a) \quad Y = \frac{1}{R} + j\omega C = \frac{1}{50} + j2 \cdot 10^3 \cdot 5 \cdot 10^{-6} = \frac{2+j}{100} \approx$$

$$I = U_{\text{Kolle}} \cdot Y \approx 0,0224 e^{j26,6^\circ} \text{ ampere} \quad \left(\approx 0,0224 \cdot e^{j26,6^\circ} \text{ S} \right)$$

$$i(t) = \text{Im}(I e^{j\omega t}) \approx 0,0224 \cdot \sin(2000t + 26,6^\circ) \text{ ampere}$$

$$\approx 0,022 \cdot \sin(2000t + 26,6^\circ) \text{ ampere}$$

$$b) \quad I_R = \frac{U_{\text{Kolle}}}{R} = 0,2 \text{ A} \Rightarrow \hat{I}_R = 0,2 \text{ A}$$


$$I_C = \frac{U_{\text{Kolle}}}{j\omega C} = j 10 \cdot 2 \cdot 10^3 \cdot 5 \cdot 10^{-6} = 0,1 e^{j90^\circ} \text{ A}$$

$$\Rightarrow \hat{I}_C = 0,1 \text{ A}$$

$$\hat{I}_R^2 + \hat{I}_C^2 = \hat{I}^2$$

c) —

AC4

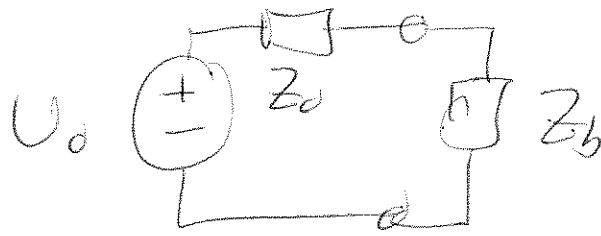

$$U_0 = 5,0 \text{ V}$$

$$\omega = 5000 \text{ rad/s}$$

$$Z_0 = 50 - j20 \Omega$$

$$a) \quad Z_b = \overline{Z_0} = 50 + j20 \Omega$$

Spannung last

$$\Rightarrow Z_{\text{tot}} = Z_0 + Z_b = 100 \Omega$$

$$P_b = \frac{1}{2} \operatorname{Re}\{\overbrace{Z_b}^d \overline{I} \cdot I\}$$

$$P = \frac{1}{2} \underset{\substack{\uparrow \\ \text{Realteil} \\ \text{von } Z_b}}{R_b} |I|^2 = \frac{1}{2} R_b \left| \frac{U_0}{Z_{\text{tot}}} \right|^2 = \frac{1}{2} 50 \left(\frac{5}{100} \right)^2$$

$$= \underline{\underline{0,0625 \text{ W}}}$$

$$b) \quad Z_b = |Z_0| = \sqrt{50^2 + (-20)^2} \approx 53,85 \approx \underline{\underline{54 \Omega}}$$

$$P_b = \frac{1}{2} \underset{\substack{\uparrow \\ \text{nu} = Z_b}}{R_b} |I|^2 = \frac{1}{2} R_b \left| \frac{U_0}{Z_0 + Z_b} \right|^2 = \frac{53,85}{2} \frac{5^2}{(50 + 53,85)^2 + (20)^2}$$

$$\approx 0,0602 \approx \underline{\underline{0,06 \text{ W}}}$$

$$c) \quad \left. \begin{array}{l} Z_b = |Z_b| e^{j45^\circ} \\ |Z_b| = |Z_0| \approx 53,85 \Omega \end{array} \right\} \Rightarrow Z_b \approx 53,85 e^{j45^\circ} = \frac{53,85 (1+j)}{\sqrt{2}} \Omega$$

$$\Rightarrow Z_b \approx 38,08 (1+j) \approx \underline{\underline{38 (1+j) \Omega}}$$

$$P_b = \frac{1}{2} R_b |I|^2 = \frac{38,08}{2} \cdot \frac{5^2}{(50+38,08)^2 + (-20+38,08)^2}$$

$$\approx 0,0589 \approx \underline{\underline{0,059 \text{ W}}}$$

d) $Z_b = R_b + j40 \Omega$ (ej fix fas $\Rightarrow |Z_b| = |Z_0|$
kan ej ändra)

Se $j40 \Omega$ som del av $Z_0 \Rightarrow$

$$R_b = |50 - j20 + j40| \approx 53,85 \Omega \approx \underline{\underline{54 \Omega}}$$

$$P_b = \frac{1}{2} R_b \left| \frac{U_{källa}}{Z_0 + Z_b} \right|^2 \approx 0,0602 \text{ W} \approx \underline{\underline{0,06 \text{ W}}}$$

e) $Z_b = 100 + jX_b \Omega$


P_b maximal om strömmen i kretsen maximal
dvs $Z_{\text{total}} = \text{reell i vårt fall}$

$$\Rightarrow \text{Välj } jX_b = -jX_0 = -(-j20) = \underline{\underline{j20 \Omega}}$$

$$P_b = \frac{1}{2} R_b \left(\frac{U_{källa}}{R_0 + R_b} \right)^2 \approx 0,0556 \approx \underline{\underline{0,056 \text{ W}}}$$

AC 15

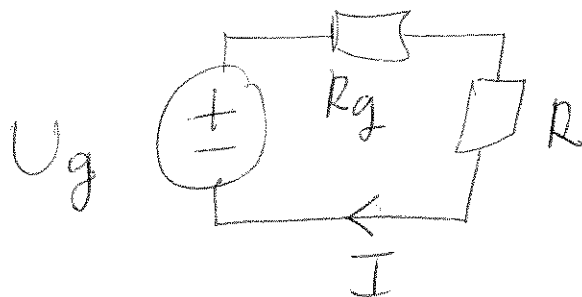
$\omega \rightarrow 0 \Rightarrow$ kretsen kan approximeras med:



("kondensator avbrutt")
("induktor kortslutt.")

$$\Rightarrow |I| = \frac{|U_g|}{R_g + R}$$

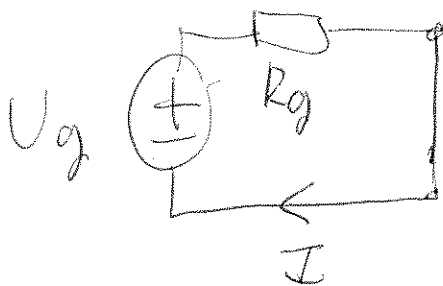$\omega \rightarrow \infty \Rightarrow$ kretsen kan approximeras med:




$$|I| = \frac{|U_g|}{R_g}$$

("kondensator kortsluttes")
("induktor avbrutt")

Med dessa uttryck kan deluppg. a, b, d, e lösas

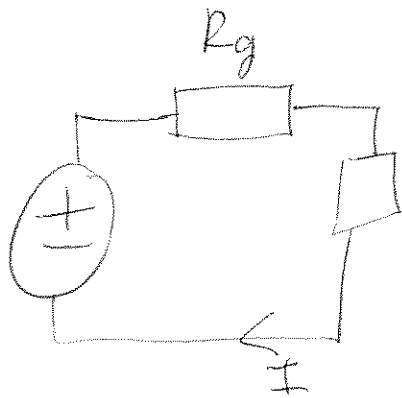Vid resonans ($Z_{\text{total}} = \text{reell}$) är kretsen



← realdelen av parallellkopplingen
av $\frac{1}{j\omega C}$ & $R + j\omega L$

$$Z_{\text{tot}} = R_g + \frac{(R + j\omega L) \frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} = \dots =$$

$$= R_g + \frac{R \cdot (1 - \omega^2 LC) + \omega^2 LCR + j[\omega L(1 - \omega^2 C) - \omega CR^2]}{(1 - \omega^2 LC)^2 + (\omega RC)^2}$$

$$\text{Im } Z_{\text{tot}} = 0 \Rightarrow \omega_r L(1 - \omega_r^2 LC) - \omega_r CR^2 = 0$$

$$\Rightarrow \begin{cases} \omega_r = 0 & (\text{ingen oscillation}) \\ L(1 - \omega_r^2 LC) = CR^2 \end{cases}$$

$$\Rightarrow \omega_r^2 = \frac{1}{LC} \left(1 - \frac{R^2 C}{L}\right) = \omega_0^2 \left(1 - \frac{R^2 C}{L}\right)$$

$$\Rightarrow \boxed{\omega_r = \omega_0 \sqrt{1 - \frac{R^2 C}{L}}}$$

[om $R > \sqrt{\frac{L}{C}}$ så blir ω_r imaginär $\Rightarrow$ damping, ingen oscillation]

Nu har vi fått fram resonansvinkel bet. ω_r

$$\omega = \omega_r \Rightarrow Z_{tot} = R_g + \frac{L}{C} \cdot \frac{1}{R}$$

$$\Rightarrow |I| = \frac{|U_g|}{R_g + \frac{L}{C} R} \Rightarrow \text{lösar deluppg. c, g, i}$$

Kvartan att bestämma strömmen då $\omega = \omega_0 = \frac{1}{\sqrt{LC}}$.

Ins. $\omega = \omega_0$ i Z_{tot} på föregående sida ger:

$$Z_{tot} = R_g + \frac{1 - j R \sqrt{\frac{C}{L}}}{\frac{RC}{L}}$$

$$\Rightarrow |I| = \frac{|U_g|}{\left| R_g + \frac{1 - j R \sqrt{\frac{C}{L}}}{\frac{RC}{L}} \right|} = \frac{|U_g|}{\sqrt{\left(R_g + \frac{L}{RC} \right)^2 + \left(-\sqrt{\frac{L}{C}} \right)^2}}$$

$\Rightarrow$ lös en deluppg. c, f, h.